

# Electronics Today



August 1984

\$2.95  
MM70924



Canada's Magazine for Electronics & Computing Enthusiasts

## Robots For Home and Education

R2D2 can be yours.

### Model Railway Switch Controller




### Computing Today

- 6502 Assembler
- Apple Listings
- Memotech 512

### Robot Servo Interface

Computer Control

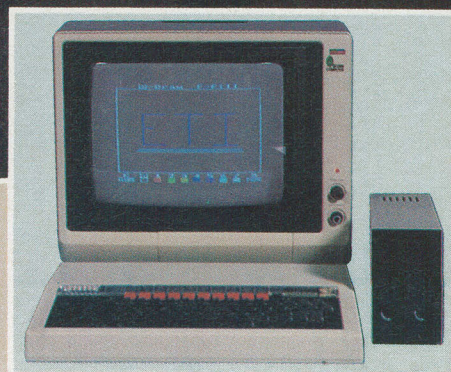

**Computer  
Review**  
Acorn BBC





# The **BEST** News All Day

The **BEST** personal computer is your best opportunity to own a really powerful, flexible personal computer at a really attractive price.

For less than the cost of other comparable systems, the **BEST** offers you a sixteen bit 8088 based computer compatible with most MS-DOS based software.



## The basic **BEST**

- 64K of RAM expandable to 256K on board, 512K in all.
- Shugart SA455 drive Double sided double density holds 340K.
- Colour video board
- Floppy controller

**Just \$1995.**

## The Loaded **BEST**

- The basic **BEST** with
- Two Shugart SA455 drives Shugart double sided double density drives.
  - 256K of RAM A quarter megabyte of memory on board.
  - RS-232C interface

**Just \$2595**

## The Executive **BEST**

- The loaded **BEST** with:
- A 10 megabyte hard drive.

**Just \$3995**

Does not include Microsoft BASIC or other proprietary software.

**Exceltronix 319 College Street, Toronto, Ontario M5T 1S2**

Other locations: 72 James Street N., Hamilton, Ontario 416-522-4124  
217 Bank Street, Ottawa, Ontario 613-230-9000

Phone: 1-416-921-8941 Toll free: 1-800-268-3798 Telex: 065-24218 Email: 1-416-293-1796



# SURPLUSTRONICS

**we will not be undersold**



Canadian Made

AS  
Reviewed  
in ETI  
May 1983:  
Send for a  
FREE Copy

**960-1350**

## OUR FAMOUS 6502 BOARD

**NOW NEW & IMPROVED VIDEO SECTION**



This 6502 board is a vast improvement on others available:

- 64K RAM (8-4164 chips)
- 80 x 24 video included on board
- Floppy Disk Controller included
- FIVE additional slots
- Z80 blank PCB included
- Powerful power supply (5V 5A, +12V 2 up to 3A peak, -5V 0.5A, -12V 0.5A)
- Hydro-approved whereas many others are not!
- Superb quality plastic case
- Excellent keyboard including numeric keypad
- EPROMS (blank) included
- Available preassembled by special order only.
- Ideal for educational applications.

**\$669**

Our prices are low due to our mass production assembly, which makes it hard for others to compete.

**NOW** you receive a **FREE** Z80 PC BOARD **AND** **FREE** 128K RAM DISK PC BOARD when you order the complete package (BLANK)

Our boards are professionally made, flow soldering & cleaned & use only high quality prime parts.

You can now get an IBM compatible without wasting your investment in a 6502 system. Talk to us about our generous trade-in scheme.


## BEST PRICE

**8088 System ..... \$1,989**

Best Prices in Canada

Complete System with 64K, expandable to 256K. Comes with Colour Graphics, Floppy Controller and one DS, DD 5 1/4" Disk Drive, Keyboard, Case and Extra Heavy-Duty, Fan Cooled Power Supply.

System comes with 5 peripheral slots. Optional 8087 arithmetic processor available. Floppy controller can handle up to 4 drives and as an option can a serial port and real-time clock. Completely built and tested and sold with a blank EPROM. Compatible with You-Know-Who. Systems are now in stock but due to extraordinary demand at time of going to press, order now to prevent delays. Please Note: We do not sell any proprietary software.

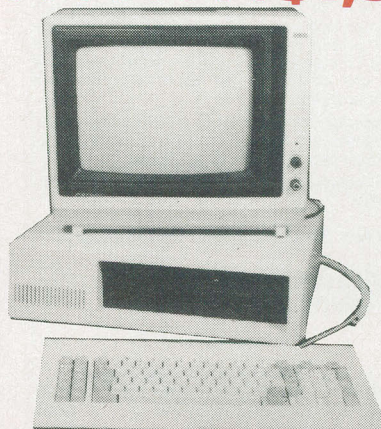

## Peripheral Boards for your IBM PC

Prototyping Card ..... \$33.00  
Floppy Controller Card ..... \$289.00  
Colour Video Card ..... \$299.00  
Parallel & Game Port Card . . . \$149.00  
EPROM Programmer. Starts at \$149.00  
Expansion Card  
with many options ..... \$Call

Attractive Case (as shown above) \$85.00  
Keyboard (as shown above) . . . \$187.00

**Super Power Supply, made to fit above case, with cooling fan. . . . . \$135.00**

8088 Board, with 64K on board (provision for 256K), as described in our 8088 System.

Assembled and tested \$499.00

**Form a Buyers Group. Buy in groups of 5 or more and you can save hundreds of dollars each.**

**Huge variety of Surplus stock at low, low prices. New shipments arriving. No reasonable offers refused. Prices subject to change without notice!**

Surplustronics, 310 College Street, Toronto, Ontario, M5T 1S3

## Monitors

ZVM-122 Amber ..... \$139.00  
ZVM-123 Green ..... \$129.00  
Roland Colour 1 ..... \$395.00  
Amdek Green ..... \$129.00

## EPS Keyboard \$399.00

Apple Compatible. IBM Module available. Distributor for Ogivar

## Apple Peripherals Assembled and Tested

Serial Card ..... \$ 85.00  
Z80 Card ..... \$ 58.00  
80 x 24 ..... \$ 84.00  
16K RAM ..... \$ 58.00  
Prototyping Board ..... \$ 14.50  
Parallel Printer Card ..... \$ 59.00  
... with cable & connector. . . . \$ 69.00  
128K Board (No IC's) ..... \$ 49.00  
...with IC's & 64K RAM. . . . . \$129.00  
...with IC's & 128K RAM. . . . . \$210.00  
Crazy Card ..... \$ 58.00  
Eprom Programmer ..... \$ 68.00

Apple Compatible ..... \$249.00  
Controller ..... \$ 59.00  
...w/software ..... \$119.00

**One year warranty**

**All prices subject to change**

A. Gemini 10x ..... \$359.00  
B. Special Multiflex parallel card with cable. Shop and compare . . . \$ 69.00  
Package price of A and B . . . . \$415.00  
Gemini 15x ..... \$598.00

## 5" Green Screen Monitors. \$59

**Telex No.  
065-24218**

Mail Orders add \$5.00 minimum for shipping & handling. Ontario residents add 7% P.S.T. Visa, Mastercard and American Express cards accepted: send card number, expiry data, name of bank and signature. Send certified cheque or money order, do not send cash.

Circle No. 29 on Reader Service Card  
More lines to serve you better  
**(416) 960-1350**



# GLADSTONE ELECTRONICS

## SUMMER SALE '84

SAVE \$105.00 on  
**TIMEX 2068**  
was \$325.00



**NOW  
\$229.95**  
72K Internal memory,  
Sound & Colour

- One Touch Keyword Entry • Brilliant Colour Display on TV or Monitor • Intermixed Text & Graphics • Includes 3 Programs on Cassette — Keyboard Tutorial, Turtle Graphics, Home Accounting • High Resolution Colour Graphics •

Other features include built-in upper and lower case, 42 keys with auto repeat, reset key, outputs for monitor and TV, 256 x 192 colour graphics resolution, two joystick ports, and expansion connector.

The new Timex 2068 computer is designed to fill all of your computing requirements for home and business. It loads and saves programs on ordinary cassette tape on a regular household cassette player — or use the new Timex data recorder listed below. New improved tape circuitry make loading and saving a breeze.

### 2068 Software and Hardware

#### HARDWARE

2068 Joystick .....	\$14.95
2050 Modem .....	\$219.95
2040 Printer .....	\$99.95
JT-1115 Data Recorder .....	\$54.95
Complete Technical Manual .....	\$34.95

#### SOFTWARE CARTRIDGES:


Budgeter .....	\$34.95
Flight Simulation .....	\$39.95

#### SOFTWARE ON CASSETTE:

Vu-Calc .....	\$24.95
Vu-File .....	\$24.95
Vu-3D .....	\$19.95
Personal Finance .....	\$24.95
Androids .....	\$19.95
Penetrator .....	\$19.95
Casino 1 .....	\$19.95
Dragmaster .....	\$19.95
Chess .....	\$36.95
Personal Accountant .....	\$36.95
Gulpman .....	\$29.95
Assembler .....	\$29.95
Disassembler .....	\$29.95
Cyberzone .....	\$29.95
2068 Beginners & Intermediate Guide "Book" .....	\$13.95

**TIMEX 1500  
PERSONAL COMPUTER**  
RUNS ALL TS-1000/ZX-81 SOFTWARE

**\$129.95**

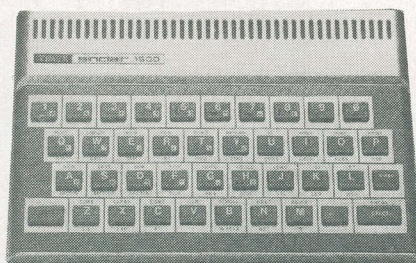

Includes 3 Software Programs! • Grimm's Fairy Trails  
• Bio Rhythms • Cassette Load Test Program

**RAISED  
TYPEWRITER  
KEYBOARD**

Simple...

Affordable

**EXPANDS TO 32K LISTED  
(WITH 16K RAM  
ELSEWHERE)**

Versatile...

**UNIQUE KEYWORDS  
AND SYNTAX CHECK  
MAKE LEARNING TO  
PROGRAM EASY**



\* Includes all hook-up accessories and manual

\* Directly connects to TV

Using the same basic language and operating system as the world's most popular computer — the ZX-81/TS-100 — the all new TS/1500 incorporates the best of two worlds. Compatibility with ZX-81 software allows present Sinclair owners to upgrade their equipment without obsolescing their software. First-time buyers will have access to one of the largest libraries of software available for any computer.

Improved tape loading and saving facilities make data storage and retrieval simple on ordinary cassette player, or on the Timex data recorder listed below.

Includes full-sized typewriter-style keyboard and 16K internal memory.

**The Timex Sinclair 1500. Order today!**

### SOFTWARE/HARDWARE FOR ZX-81/TS-1000/TS1500 SALE

ZX Printer .....	\$69.95	Software On Cassette	
3 rolls ZX paper .....	\$16.95	Flight Simulation .....	\$7.95
64K Bare Bones Kit .....	\$19.95	Backgammon .....	\$7.95
Edge Connector .....	\$9.95	VU-File .....	\$7.95
16K Memotech RAM .....	\$49.95	VU-Calc .....	\$7.95
64K Gladstone RAM .....	\$69.95	Munchy-Man .....	\$7.95
Keyboard/case .....	\$79.95	ZX Assembler .....	\$5.95
Memotech .....		ZX-Aid .....	\$5.95
keyboard .....	\$119.95	ZX Bug .....	\$5.95

#### Books

Basic Course .....	\$18.95
ZX-81 Pocket Book .....	\$9.95
Mastering Machine Code .....	\$16.95

### VIDEO-TEX SOFTWARE FROM COMPUSERVE

**VIDTEX** — Complete communications software, terminal emulator, provides colour graphics, auto log on, full printer support, RAM buffer, user defined function keys, cursor positioning, and more. Specify Apple or C64. .... \$59.95

**EXECUTIVE INFORMATION SERVICE** (for I.B.M. PC) - VALUE LINE, STANDARD AND POORS, up-to-date stock information, executive news service, and more. .... \$129.95  
Above with Software ..... \$199.95

**IBM PROFESSIONAL  
CONNECTION** ..... \$129.95

### ROBOT KITS

(as advertised in July ETI)

\* DO IT YOURSELF

\* EASY TO BUILD

### LINE TRACER

**\$64.95**

- \* Follow any black line
- \* Kit contains 2 motors



Guided by an infra-red light sensor, this robot will automatically follow any black line drawn on white paper.

**Movement:** 3 wheels driven by 2 DC motors

**Control:** Infra-red sensor including infra-red diode/photo diode/IC

**How to play:** Draw a black line on white paper board. Line width should be 10mm minimum wide. Narrowest turning radius must be at least 15 cm.

### AVOIDER

**\$69.95**

- \* Detects and avoids objects in its path
- \* Walks on 6 legs



An intelligent robot which knows how to avoid hitting walls. This robot emits an infra-red beam which detects an obstacle in front.

**Movement:** 3 legs on each side by crank motion.

**Control:** Infra-red sensor including infra-red diode/photo diode/IC

### TSUN. MONKEY

**\$39.95**

- \* Climbs rope on command
- \* 2 movable climbing arms



Order your MONKEY to "Move" with a loud voice or clap of your hands, and the robot starts romping along a rope and stops after a while by himself.

**Movement:** Two alternatively moving gripper arms driven by crank motion.

**Control:** Sound sensor, including condenser microphone/transistor.

### COMMODORE 64 HOME/BUSINESS SOFTWARE DISKS

CALC-PRO Financial Spreadsheet .....	\$29.95
Personal Money Management .....	\$29.95
Real Estate Management .....	\$29.95

### COMPUSERVE STARTER PACKAGE \$59.95



Takes the mystery out of computer communications  
• FULL VIDEO-TEX INFORMATION

#### WHAT IS COMPUSERVE?

CompuServe is a versatile easy to use interactive communications system designed for the computer user — and simply connected through the phone lines. Among the over 1000 services supplied are magazines, news and weather, movie reviews, electronic banking and shopping, financial information, bulletin boards for selling & swapping, CB simulator, electronic mail, medical information, access to mainframe computers, encyclopedias, a wide variety of games, and much more.

**STARTER PACKAGE:** The CompuServe Starter package provides step by step instructions for the beginner on how to operate your computer to access this system. Also provides free CompuServe time, subscription to TODAY magazine, and instructions on how to sign up for this service. Now you can enter the exciting world of computer telecommunications! Order today.

**GLADSTONE ELECTRONICS**

1736 Avenue Road  
Toronto, Ont. M5M 3Y7

**ORDER TOLL FREE  
1-800-268-3640**

Have your credit card ready; Orders only.

**Product Information  
416-787-1448**

Circle Reader Service Card No. 36  
For FREE Catalogue



# Electronics Today





Audit Bureau  
of Circulation

August 1984

INTERNATIONAL

Vol. 8, No. 8 ISSN 07038984

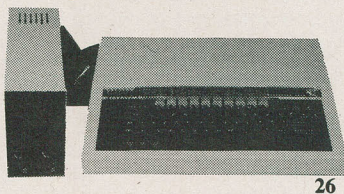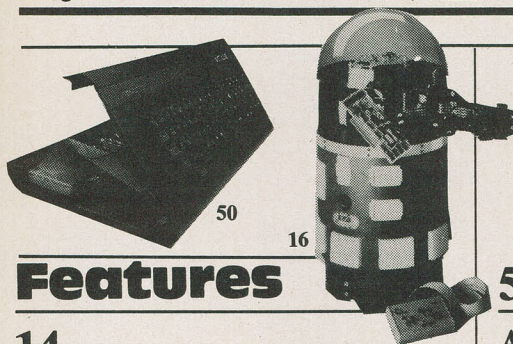

## Features

14

### Alignment by Test Pattern

James Essex explains TV Ontario's nifty gift to TV tinkers.

16

### Robotics: Home and Educational

Roger Allan's lineup of the New Robotics: affordable home units.

26

### Computer Review

Anthony DeBoer examines the Acorn BBC, a powerful UK micro.

31

### Electronics In Action

Roger Allan reports on a heat scanner, an intelligent phone, and a tiny VCR camera.

40

### Machine Language, Part III

Addressing techniques for various CPUs.

42

### Advanced 6502 Programming

Some unusual approaches to 6502 assembler, by Yin Pun.

45

### Circuit Ideas

Technical tips on a tone control and other circuits.

50

### A Look at the Memotech 512

Another UK computer, recently available in Canada.

56

### Computing Today

Some Applesoft listings related to timekeeping.

## Projects

22

### Model Railway Switch Controller

Capacitive discharge and an indicator for deluxe switching.

58

### Servo Interface

A robotics project: run a servo arm with your computer.

## Columns, News and Information

For Your Information .....	7
ETI Bookshelf .....	47
Order Form .....	53
Binders .....	53
Book of the Month .....	54
Subscriptions .....	54
Next Month .....	53
Product Mart .....	70

## Our Cover

The Heath HERO robot symbolizes what may be a new era in home robotics, page 16. The Acorn BBC computer is reviewed on page 26.

### Electronics Today is Published by:

Moorshead Publications  
Editorial and Advertising Offices  
Suite 601, 25 Overlea Boulevard,  
Toronto, Ontario, M4H 1B1  
Telephone (416) 423-3262

Editor:  
Editorial Assistant:  
Director of Production:  
Creative Manager:  
Production:

William Markwick  
Edward Zapletal  
Erik Blomkwist  
Ann Rodrigues  
Douglas Goddard  
Neville Willams  
Naznin Sunderji  
Lisa Salvatori  
Omar Vogt  
Rick May  
Claire Zvyvitski  
John McGowan & Associates  
(514)735-5191

Circulation Manager:  
Advertising:

Advertising (Que.):

Publisher: H.W. Moorshead; Executive Vice-President: V.K. Marskell; General Manager: S. Harrison; Controller: B. Shankman; Accounts: P. Dunphy; Reader Service: C. Wyatt, S. Halladay, H. Brooks, K. Adams; Advertising Services: D. Whitehead; Dealer Services: A. Nagels.

Newsstand Distribution:  
Master Media, Oakville, Ontario

Subscriptions  
\$19.95 (one year), \$34.95 (two years). For US add \$3.00 per year, other countries add \$5.00 per year. Please specify if subscription is new or a renewal.

Postal Information  
Second Class Mail Registration No. 3955. Mailing address for subscription orders, undeliverable copies and change of address notice is:  
Electronics Today International, Suite 601, 25 Overlea Blvd., Toronto, Ontario, M4H 1B1.

## Advertiser's Index

ABBA Computer Systems .....	67
Active Components Sales Corp. ....	10
Atlas Electronics Ltd. ....	61
Allan Crawford and Associates. ....	68,69
Audiovision .....	30
BCS Electronics Ltd. ....	33,64,66
Budgetron .....	12
Brunelle Instruments Inc. ....	34,65
Circuitronics .....	66
Computer Mail Order .....	6
Computer Parts Galore .....	8,9
Computronics .....	33
Cyprus Products Inc. ....	72
Daetron .....	65
Electronic Control Systems .....	34,65
Exceltronix .....	2
Gladstone Electronics .....	4
Heath Company .....	39
H. Rogers Electronic Instruments Ltd. ....	11
H.T. Watt and Associates Ltd. ....	67
Infinite Canada Inc. ....	67
Kaientai Electronics Merchants Ltd. ....	33
Kitstronic International Ltd. ....	11
Mark Gee Enterprises .....	67
McGraw Hill .....	29
Metermaster .....	43
Orion Electronic Supplies Inc. ....	41
T.W. Wilson Sales .....	65



# = COMPUTER MAIL ORDER =

= CANADA =

**ONTARIO/QUEBEC**  
**1-800-268-3974**

**TORONTO**  
**828-0866**

**OTHER PROVINCES**  
**1-800-268-4559**

**We Carry a Wide Selection of Software From:**

Artworx, Broderbund, Commercial Data, Creative Software, Epyx, Atarisoft, Hes, Sirus, Microspec, Synapse, Thorn, Spinnaker, Timeworks + Many More. Call us for prices!

(All equipment under full warranty in Canada.)

Price subject to change without notice.

(All orders Shipped within 48 hrs, upon payment.)

## COMPUTERS

APPLE	CALL
COLUMBIA	CALL
COMPAQ	CALL
EAGLE	CALL
FRANKLIN	CALL
HEWLETT PACKARD	CALL
IBM	CALL
SANYO	CALL

## DISK DRIVES

CDC (for IBM)	\$339.00
INDUS	
GT ATARI Drive	549.00
MSD	
MSD-1 C64 Drive	519.00
MSD-2 C64 Drive	855.00
PERCOM	CALL
RANA	
1000 (Atari)	479.00
Elite 1	389.00
Elite 2	579.00
Elite 3	799.00
SANTA CLARA	CALL
TALLGRASS	CALL
TANDON	
TM-100-2 DS/DD	339.00
TM-50-2 DS/DD	349.00
TRAK	
ATD-2	565.00

## MODEMS

ANCHOR	
Mark I (RS232)	129.00
Mark II (Atari)	129.00
Mark III (TI-99)	179.00
Mark IV (CBM/PET)	199.00
Mark V (Osborne)	159.00
Mark VI (IBM)	279.00
Mark VII (AA/AD)	193.00
Mark XII (1200 Bd.)	489.00
HAYES	
Smartmodem 300	356.00
Smartmodem 1200	799.00
Smartmodem 1200B	749.00
Micromodem II	432.00
Micromodem II +	489.00
Micromodem II e	439.00
NOVATION	
J-Cat	163.00
Smartcat 103	289.00
Smartcat 103/212	649.00
Autocat	356.00
212 Apple Cat	929.00
PC-Cat	549.00

## MONITORS

AMDEK	
Video 300	\$229.00
Video 300 A	239.00
Video 310A IBM	249.00
Colour 1 +	429.00
Others	CALL
BMC	
12" Green	125.00
12" Amber	135.00
GORILLA	
12" Green	139.00
12" Amber	149.00
NEC	CALL
PANASONIC	CALL
PRINCETON GRAPHICS	
HX-12	819.00
QUADRAM	
Quadcolor RGB	809.00
SAKATA	CALL
TAXAN	CALL
USI	CALL
ZENITH	
Amber	159.00
Green	149.00
Colour	699.00

## CARDS

AST RESEARCH	CALL
QUADRAM	CALL
HERCULES	
Graphic card	598.00
PLANTRONICS	
Colorplus	699.00

## ACCESSORIES

KEYTRONIC	
KEYBOARDS	CALL
KOALA PAD	
All Computers	CALL

## INTERFACES

Batteries Included	
Bus Card	CALL
80 Col. Card	CALL
CARDCO	
Par Printer Inter	75.00
Int/Graphics	119.00
TYMAC	
C64 to EPSON OKI	148.00
MPC	
Apple Dumping GX.	CALL
PKASO	
Universal Card	225.00

## PRINTERS

BMC	
401 Letter Quality	\$923.00
BX-80 Dot Matrix	399.00
C. ITOH	
Gorilla Banana	299.00
Prowriter 8510P	550.00
Prowriter 1550P	899.00
F10-40	1529.00
F10-55	1999.00
DAISYWRITER	
2000	1499.00
COMWRITER	
CW2. LQ 12CPS	749.00
EPSON	
RX80	449.00
RX80FT	525.00
FX80	749.00
FX100	1049.00
JUKI	
6100	769.00
OKIDATA	
82	475.00
83	899.00
84 Par	1499.00
84 Ser	1650.00
92	695.00
93	1159.00
MANNESMANN TALLY	
Spirit 80	469.00
160L	895.00
180L	1229.00
SMITH CORONA	
L1000	589.00
STAR	
Gemini 10X	CALL
Gemini 15X	CALL
BROTHER	
HR 15	CALL
TTX	CALL
DISKETTES	
BASF	
BA1D SS/DD W/Case	28.99
BA2D DS/DD W/Case	35.99
ELEPHANT	
EL1 SS/DD	27.99
EL2 SS/DD	29.99
EL3 DS/DD	39.99
MAXELL	
MXD1 SS/DD	37.99
MXD2 DS/DD	54.99
NASHUA	
ND1D SS/DD W/Case	26.99
ND2D DS/DD W/Case	38.99
VERBATIM	
VE1 SS/DD	31.99
VE2 DS/DD	43.99
VE1C SS/DD W/Case	34.99
VE2C DS/DD W/Case	46.99

**Dealer Enquiries Invited**

Write or telephone for our FREE catalog

To order: Send money order, certified cheque, personal cheques must clear our bank, VISA or MASTERCARD. (Include card # and expiry date & signature) Add 5% for shipping and handling. Minimum \$5.00 per order.

**Ontario residents add 7% P.S.T.**

Computer Mail Order Canada 2505 Dunwin Drive, Unit 3 • Mississauga, Ontario L5L 1T1





# for your information

## Copyright

All material is subject to worldwide copyright protection. All PCB patterns are copyright and no company can sell boards to our design without our permission.

## Liability

While every effort has been made to ensure that all constructional projects referred to in this magazine will operate as indicated efficiently and properly and that all necessary components are available, no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate efficiently or at all whether due to any fault in the design or otherwise and no responsibility is accepted for the failure to obtain component parts in respect of any such project. Further no responsibility is accepted in respect of any injury or damage caused by any fault in design of any such project as aforesaid.

## Editorial Queries

Written queries can only be answered when accompanied by a self-addressed, stamped envelope. These must relate to recent articles and not involve the staff in any research. Mark such letter ETI Query. *We cannot answer telephone queries.*

## Binders

Binders made especially for ETI are available for \$9.25 including postage and handling. Ontario residents please add provincial sales tax.

## Back Issues and Photocopies

Previous issues of ETI Canada are available direct from our office for \$4.00 each; please specify by month, not by feature you require. See order card for issue available.

We can supply photocopies of any article published in ETI Canada; the charge is \$2.00 per article, regardless of length. Please specify both issue and article.

## Component Notation and Units

We normally specify components using an international standard. Many readers will be unfamiliar with this but it's simple, less likely to lead to error and will be widely used everywhere sooner or later. ETI has opted for sooner!

Firstly decimal points are dropped and substituted with the multiplier; thus 4.7uF is written 4u7. Capacitors also use the multiplier nano (one nanofarad is 1000pF). Thus 0.1 uF is 100nF, 5600pF is 5n6. Other examples are 5.6pF = 5p6 and 0.5pF = 0p5.

Resistors are treated similarly: 1.8Mohms is 1M8, 56kohms is the same, 4.7kohms is 4k7, 100ohms is 100R and 5.6ohms is 5R6.

## PCB Suppliers

ETI magazine does NOT supply PCBs or kits but we do issue manufacturing permits for companies to manufacture boards and kits to our designs. Contact the following companies when ordering boards.

Please note we do not keep track of what is available from who so please don't contact us for information on PCBs and kits. Similarly do not ask PCB suppliers for help with projects.

K.S.K. Associates, P.O. Box 266, Milton, Ont. L9T 4N9.

B—C—D Electronics, P.O. Box 6326, Stn. F, Hamilton, Ont. L9C 6L9.

Wentworth Electronics, R.R. No. 1 Waterdown, Ont. L0R 2H0.

Danocinths Inc., P.O. Box 261, Westland MI 48185, USA.

Arkon Electronics Ltd., 409 Queen Street W., Toronto, Ont., M5V 2A5.

Beyer & Martin Electronic Ltd., 2 Jodi Ave., Unit C, Downsview, Ontario M3N 1H1.

Spectrum Electronics, 14 Knightswood Crescent, Brantford, Ontario N3R 7E6.


## Rugged TSE Cases

TSE Inc. announced the introduction of a patented line of exceptionally rugged cases for shipping or carrying tools, components, and sensitive equipment. Molded of Lexan® resin, the virtually indestructible cases protect their contents from shock, dirt, moisture, and theft. TSE cases are ideal for shipment and storage — both in-plant and between-plant.

The water-resistant cases are remarkably lightweight yet considerably stronger than formed metal cases. They have the added advantage of being nonconductive and far more resistant to denting and cracking. Cutting tools, measuring devices, chucks, dies, and collets are among the objects protected in transit by polycarbonate TSE cases.

For further information on TS protective cases and TSE Custom-Pack system, contact TSE, Inc., 541 East Hector St., Conshohocken, PA 19428; phone (215) 825-8202.

Circle No.60 on Reader Service Card

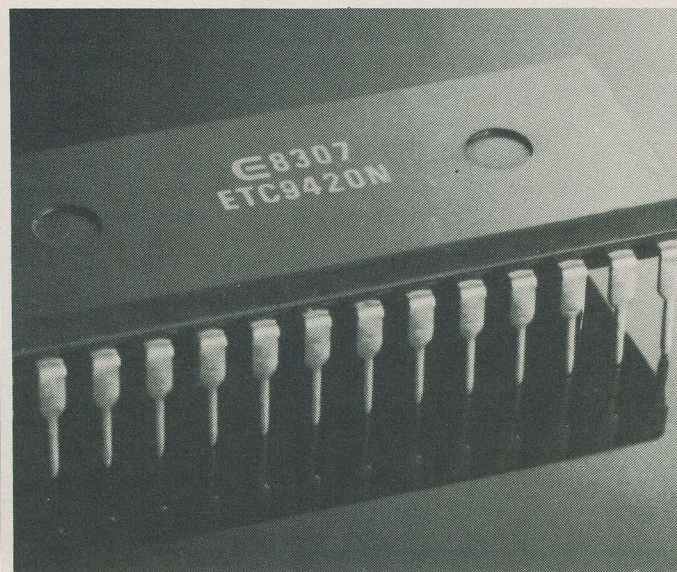

## National's COP-420C

Thomson Semiconductor recently announced availability of its ETC-9420, a fully compatible equivalent of National Semiconductor's (Controller-Oriented Processor) COP-420C — a semi-custom, 4-bit microcontroller.


Thomson's P<sup>2</sup> CMOS device contains all system timing, internal logic, ROM, RAM, and I/O for a wide variety of applications including telephone sets, automobiles, toys and other dedicated control functions. Prices and technical information are available from Thomson Semiconductor's MOS marketing group, 6660 Variel Ave., Canoga Park, CA 91303, (818) 887-1010.

Circle No.59 on Reader Service Card
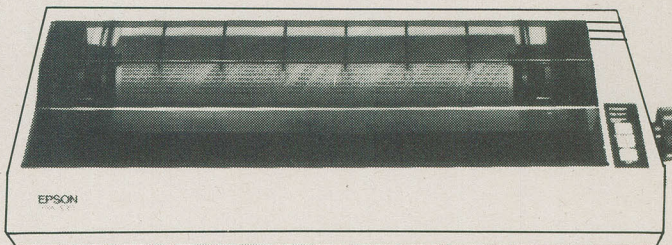
## New Epson RX-100 Printer

Epson Canada recently introduced the RX-100 upgraded printer based upon the proven technology of the MX series. The upper-compatible RX-100 offers many features of the MX-100 such as a 9 x 9 print matrix structure and bidirectional with logic-seeking printhead motion. Both friction and tractor feed are provided for maximum paper handling convenience.

Two full 96 ASCII character sets plus 11 international characters sets offer a versatile printing capability. A total of 128 typesets are offered including emphasized, doublestrike, pica, elite, italics, subscript and superscript.



In addition to the RX-series, Epson Canada markets the FX-LQ-series dot matrix printers, HX-20 Notebook Computer and the QX-10 Personal Business Computer. All products carry a one year warranty under contract with

E.S.S.N.A. Services Limited. For more information contact: Epson Canada Ltd., 21 Progress Court, Unit 18, Scarborough, Ont., M1G 3V4. Phone (416)431-5588 Telex 065-25415.

Circle No.58 on Reader Service Card



# COMPUTER


# PARTS GALORE INC.

316 College St.  
Toronto, Ontario M5T 1S3
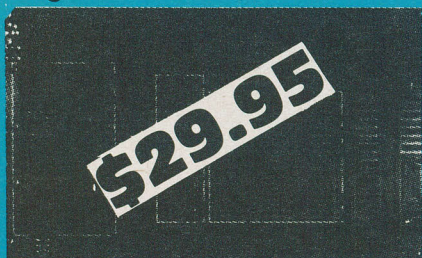
## SOLID ABS CASE NUMERIC \$59.95



**OUR 6502 BOARD**  
Now only \$29.95 still with  
all the versatility of the  
original and a full 8 slots.



## ASCII KEYBOARDS



Now, we have a new keyboard, micro  
controlled with 3 levels of pre-coded  
functions for Basic, CPM etc. and at the  
same old price as before

Function Keyboard, Numeric . . . \$99.00  
Function Keyboard, Standard . . . \$89.00

**Toll Free Orders Only**  
**1-800-387-1385**

Order Checking (416)925-8291  
Technical Data (416)925-1105

## MODEM

At last, an affordable Modem, we  
have cloned a board similar to the  
SSM Modem that features:

- APPLE II & APPLE IIe  
COMPATIBLE
- 40/80 COLUMN SUPPORTED
- FULL/HALF DUPLEX
- AUTO ANSWER/AUTO DIAL
- TOUCH TONE OR PULSE  
DIALING
- AUDIO MONITOR CHANNEL
- IN PLACE FIRMWARE
- HAYES MICRO MODEM II  
COMPATIBLE
- RUNS ASCII EXPRESS AND  
MOST OTHER PROGRAMS
- DIRECT LINE CONNECTION

We have tried it out and it is very  
good and very reasonably priced  
for it's quality . . . . . \$229.00  
Bare PCB only . . . . . \$ 24.95

## POWER SUPPLY



Our Famous "BLACK BEAUTY" power supply, now  
reduced in price but not in quality. Our ratings are  
5V-5A; 12V-2.5A; 5A-1/2A; 12V-1/2A for real . . . . . \$79.95

## GREAT DEAL



THE GREAT DEAL  
CARRIES ON FOREVER AND GETS BETTER

Our proven 6502 motherboard plus a numeric case plus  
a black beauty powersupply plus a numeric keyboard  
plus any 4 bare pcb for \$225.00




## SYSTEM SAVIOUR

2 grounded 3 wire switched sockets, pilot light, surge  
protector and on-off switch to turn off your system and  
two plugged in items . . . . . \$45.00
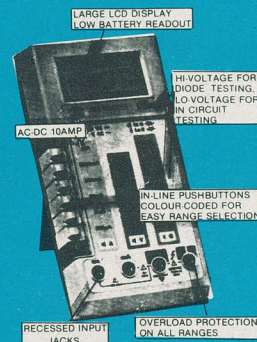
## DIGITAL MULTI-METER

AMAZINE QUALITY AT LOW COST  
**\$69.96**



## EXTRA FEATURE

- Diode test circuit • Lo voltage ohms, 0.5v • Lo bat-  
tery indicator • Auto-Zero • Auto polarity • Overload  
protection, all ranges • ABS case (will not crack) •  
One hand push buttons.

### HARD TO GET PARTS

14.318 MHZ XTAL . . . . .	\$ 2.95
17.43 MHZ XTAL . . . . .	\$ 4.95
1.8432 MHZ XTAL . . . . .	\$ 4.95
MPSA13 TRANSISTOR . . . . .	\$ 0.75
2N3904 . . . . .	\$ 0.35
2N3906 . . . . .	\$ 0.45
2N4258 . . . . .	\$ 0.75
MPSU51 . . . . .	\$ 1.00
1K, 9 PIN SIP . . . . .	\$ 0.75
1K, 8 PIN SIP . . . . .	\$ 0.75
10K, 10 PIN SIP . . . . .	\$ 0.75
4 POS DIP SWITCH . . . . .	\$ 1.75
20 PIN MALE RT ANGLE . . . . .	\$ 2.95
20 PIN FEMALE, FOR ABVS. . . . .	\$ 2.00
6 PIN POWER CONNECTOR . . . . .	\$ 1.00
RCA JACK, PCB MOUNT . . . . .	\$ 0.75
50 PI TRIMCAP . . . . .	\$ 1.00
220 OHM TRIMPOT . . . . .	\$ 0.75
68A45, VIDEX IC . . . . .	\$ 16.00
MC3242, 128K IC . . . . .	\$ 16.00

### 6502 STUFF

BB POWER SUPPLY . . . . .	\$ 79.95
ABS NUMERIC CASE . . . . .	\$ 59.95
ASCII NUM KEYBOARD . . . . .	\$ 99.00
SYSTEM SAVIOUR FAN . . . . .	\$ 45.00
GREAT DEAL . . . . .	\$225.00
Z-80 WIRED . . . . .	\$ 55.00
80 COLUMN WIRED . . . . .	\$ 75.00
16K WIRED . . . . .	\$ 59.95
WILDCARD WIRED . . . . .	\$ 45.00
SAM TALKER WIRED . . . . .	\$ 45.00
128K WIRED, NO IC'S . . . . .	\$ 39.95
128K WIRED, 64K . . . . .	\$119.00
128K WIRED, 128K . . . . .	\$199.00
DISK(3) FOR 128K . . . . .	\$ 20.00


### BARE PCB

(A) REAL TIME CLOCK PCB . . . . .	\$14.95
(B) QUAD DRIVE CARD (RANA) . . . . .	\$24.95
(C) 9 VOICE MUSIC PCB . . . . .	\$14.95
(D) BUFFER PRINTER PCB . . . . .	\$19.95
(E) GRAPPLER PCB . . . . .	\$19.95
(F) CABLE FOR D, E, SPECIFY . . . . .	\$24.95
(G) 80 COLUMN, SOFTSWITCH . . . . .	\$14.95
(H) DISC CONTROLLER PCB . . . . .	\$12.95
(I) Z-80 PCB . . . . .	\$12.95
(J) SSM MODEM PCB . . . . .	\$24.95
(K) MOUNTAIN MULTIFUNCTION . . . . .	\$24.95
(L) 128K (SATURN) PCB . . . . .	\$19.95
(M) RGB COLOR PCB . . . . .	\$24.95
(N) EPROM PROGRAMMER PCB . . . . .	\$12.95
(O) PIA PCB . . . . .	\$14.95
(P) WILD CARD PCB . . . . .	\$12.95
(Q) SAM TALKING CARD . . . . .	\$12.95
(R) RS-232 PRINTER PCB . . . . .	\$12.95
(S) RS-232 MODEM (COMM) PCB . . . . .	\$12.95
(T) RS-232 ASYNCHRONOUS PCB . . . . .	\$14.95
(U) SPRITE GRAPHICS PCB . . . . .	\$17.95

### BARE PCB FIRMWARE ETC.

(A) REAL TIME CLOCK DISK . . . . .	\$ 8.00
(B) 9 VOICE MUSIC, 2 DISKS . . . . .	\$16.00
(C) GRAPPLER EPROM . . . . .	\$ 8.00
(D) 80 COLUMN, 3 EPROMS . . . . .	\$24.00
(E) SSM MODEM EPROM . . . . .	\$ 8.00
(F) MULTIFUNCTION EPROM . . . . .	\$ 8.00
(G) 128K, 3 DISKS . . . . .	\$20.00
(H) RGB CARD PROM . . . . .	\$ 9.00
(I) RGB CARD DISK . . . . .	\$ 8.00
(J) EPROM PROG. EPROM . . . . .	\$ 8.00
(K) WILD CARD EPROM . . . . .	\$ 8.00
(L) WILD CARD DISK . . . . .	\$ 8.00
(M) SAM TALKER DISK . . . . .	\$ 8.00
(N) SPRITE DISK . . . . .	\$ 8.00

## IBM PC™ LOOK-A-LIKE CASE

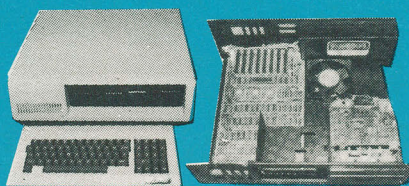

Make your Apple™ or 6502 machine look like an IBM  
PC™. This attractive metal case with ABS front bezel  
looks just like you-know-who, but is punched internally  
to take all the 6502 Mother boards, power supplies etc  
that are now sold. . . . . \$69.95  
• Keyboard Case . . . . . \$ 19.95

## MAIL ORDERS

We accept: Personal Cheques, Postal Money Orders,  
Certified Cheques, Travelers Cheques, Visa, American  
Express, Mastercard, Bank Draft. We ship C.O.D. only  
by CANPAR and Truck. We do not use Canada Post  
C.O.D. We will send your goods via CANPAR or Canada  
Post unless you say otherwise. You will be charged a  
min. \$3.00 for delivery and handling or more if your  
goods are heavier than the \$3.00 weight or if you spec-  
ify another delivery service that charges more. All  
Ont. res + 7% sales tax. We sell wholesale to any  
retail store or other reseller with a sales tax exemption  
no. as long as a realistic quantity is bought. We ship  
within a week if in stock and we will cancel any back-  
orders over 4 weeks unless otherwise instructed. 20%  
Restocking Charge.

### MEGA BOARD PARTS


(A) MAXI SWITCH KB . . . . .	\$179.95
(B) IBM CASE . . . . .	\$ 89.95
(C) ALL THE 82 IC's & 8088 . . . . .	\$159.00
(D) 8253-5 . . . . .	\$ 11.95
(E) 8259A . . . . .	\$ 11.50
(F) 8237A-5 . . . . .	\$ 34.95
(G) 8255A-5 . . . . .	\$ 7.95
(H) 8288 . . . . .	\$ 37.50
(I) 8284 . . . . .	\$ 7.95
(J) 8088 . . . . .	\$ 34.95
(K) 100 NS DELAY . . . . .	\$ 14.95
(L) 7 NS DELAY . . . . .	\$ 14.95
(M) BUS, BARS, SET OF 2 . . . . .	\$ 4.95
(N) 6-35 pf trimcap . . . . .	\$ 1.50
(O) 62 PIN EDGE CONNECTORS . . . . .	\$ 4.95
(P) 5 PIN DIN CONN, KB . . . . .	\$ 3.50
(Q) POWER CONNECTOR, M/F . . . . .	\$ 2.50
(R) 4.7K x6 SIP . . . . .	\$ 0.75
(S) 4.7K, 16 PIN RES NTWK . . . . .	\$ 1.50
(T) 8.2K, 16 PIN RES NTWK . . . . .	\$ 1.50
(U) 33 OHM, 16 PIN RES NTWK . . . . .	\$ 2.50
(V) TBP 24s10 PROM . . . . .	\$ 8.95



COMPUTER

**PARTS GALORE** INC.316 College St.  
Toronto, Ontario M5T 1S3

Toll Free Orders Only

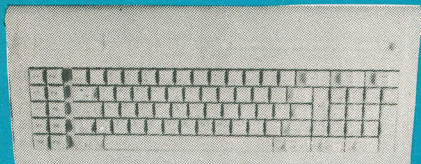**1-800-387-1385**Order Checking (416)925-8291  
Technical Data (416)925-1105**DTC**™ DISPLAY  
TELECOMMUNICATIONS  
CORPORATION**NEW FROM  
MAXISWITCH™**

The finest most cost effective keyboard for the IBM™ PC or the APPLE™ that we have ever seen. The IBM model has all of the standard features of the IBM KB plus an improved return key for true typewriter emulation (For word-processing) Full N key roll-over, auto-repeat and more. The APPLE version has a lot more than the run of the mill APPLE keyboard, 10 function keys, cursor pad, numeric pad, and 21 preprogrammed commands to save a lot of typing. Just like the picture and just as pretty.

**ONLY \$179.95**

Please specify APPLE, or IBM PC, XT  
NOTE: Complements our IBM look-alike case exactly.

**DEALERS AND OEM MANUFACTURERS  
QUANTITY DISCOUNTS AVAILABLE**

**Ideal for**

- COMPUTERISTS
- OEM MANUFACTURERS
- DEVELOPMENT LABS
- UNIVERSITIES
- INDUSTRIAL APPLICATIONS

**THE ULTIMATE OEM/PC  
COMPATIBLE SINGLE  
BOARD COMPUTER**

- ☐ **MEGA-BOARD™** with full assembly instructions ..... \$99.95
- ☐ **USERS MANUAL** with theory of operation, schematics, block diagram, application notes ..... \$19.95
- ☐ **MEGA-BIOS™** fully compatible MS-DOS/PC-DOS BIOS \$29.95

**ORDER NOW!!!**


**ONLY!**  
**\$99.95**  
**Evaluation Board Kit**

**MEGA-BOARD™ Evaluation Board Kit!**  
(Blank board with full assembly instructions and parts list.)

Includes highest quality PC board with gold plating, silk screen, solder mask

**new!****MEGA-BOARD™**

IBM is a registered trademark of  
International Business Machines

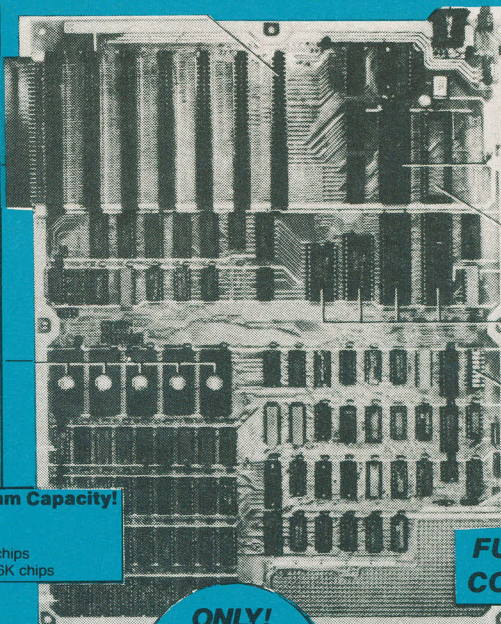**Eight Compatible  
I/O Interface  
Connectors**

(Full PC compatible)  
(compatible with all  
IBM-PC\* plug-in cards)

**Special J1  
Interface**

(Allows horizontal mounting of compatible expansion cards for easy bus expansion and custom configuring) (Board has 62 pin gold plated compatible connector)

**Extended ROM  
Capability**

(Runs all compatible PC ROMS) (Jumper programmable to accommodate all popular 8K, 16K, 32K and 64K ROM chips and NEW EE ROMS! VPP power pin available for EP ROM burning!) (External VPP voltage required)

**Full Mega-Byte Ram Capacity!  
On board!**

- (With parity)
- ☐ 256K Bytes using 64K chips
- ☐ 1 Mega Bytes using 256K chips

**Standard Key-board Interface**

(Full PC compatible)

**Hardware Reset**

(Overcomes reset flaw in PC)

**Power Connector**

(Full IBM\* pinout compatible)

**8088 Processor**

(Same as PC)

**8087 Numeric Processor**

(Same as PC)

**Peripheral Support Circuits**

(Same as PC)

**Configuration Switches**

(Same as PC)


**Speaker/Audio Port**

(Same as PC)

**Wire Wrap Area**

To facilitate special custom applications!

**FULL IBM - PC\*  
COMPATIBILITY!**

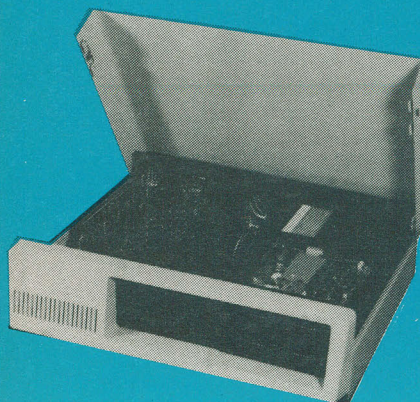**NEW****IBM CASE**

At last, a nice new case for the IBM look-a-like boards. Not cut for 6502. Fits the power supply types listed on this page and has cutouts for PC or XT (specify) card spacing, with card-guides and plastic Drive inserts and all mounting hardware, and with the greatest feature ever, a hinged lid that allows rapid and easy access to the insides. Spring clips hold it on at front so no screws need to be undone \$89.95

**WIRED N TESTED  
MEGA-BOARD™**

- Fully wave soldered and tested with all IC's and 64K of Ram on board, complete with bios, full manual, and schematic \$595.00
- Fully wave soldered and socketed with all discrete and non-plug-in parts in place. Pre-tested on a bed-of-nails tester for any shorts and other faults. All you need are the plug-in parts and you are away \$319.00

**POWER SUPPLIES  
FOR IBM PCB'S**


- 100 Watts ..... \$135.00  
Has 2 drive connectors and plug to fit all IBM Clones.  
+5V @ 10A +12V @ 3.5A  
-5V @ 0.5A -12V @ 0.5A
- 130 Watts ..... \$179.00  
Has 3 drive connectors and plug for all IBM Clones  
+5V @ 14A +12V @ 4.5A  
-5V @ 0.5A -12V @ 0.5A

**WE'VE GOT EM!  
5-1/4"  
HALF SIZE DRIVES**

- 40 Track per side
- Double-sided, double density
- Same as SA455
- Latest head & drive technology
- Fast access time



Two of These Half Size Drives will  
Fit in the Same Space as 1 Full Size Drive! \$269.00

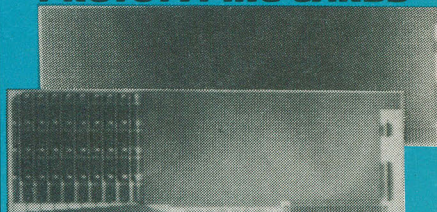**PROTOTYPING CARDS**

- WIRE WRAP ONLY CARD.** An ideal card for high density wire wrap work. There are WW holes everywhere with a DB-25 and a DB-9 Footprint at one end ..... \$29.95
- MEMORY AND WIRE WRAP.** A very good prototyping card for those doing video, memory, etc. cards. This card has the pads for a 256K 9 bit memory already laid out. All power and grounds run are in, pads for 0.1uf bypass caps on each 4164 are in, all control functions are gridded and brought out to WW pads, upward compatible to 41256, 256K memory chips. The rest of the PCB is WW on 1 centres with a DB-25 and a DB-9 footprint at one end for I/O ..... \$34.95

Circle No. 8 on Reader Service Card



## for your information

### New GRiDS

GRiD Systems Canada Inc. has announced a major expansion of its COMPASS Computer family with the introduction of three new portable computers, enhancements to its networking system, and several new software products. GRiD's networking system now integrates both IBM PCs and GRiD products in a remote area network. The GRiD COMPASS family now includes seven computer models, starting in price at \$5,195 for the GRiD Server Workstation. GRiD introduced two models of its new COMPASS II

computer. Both models offer plug-in software modules for operating systems and applications programs. Each COMPASS II will accommodate up to 512 kilobytes of read only memory (ROM) in the form of easily exchanged pre-programmed ROM packs which allow users to conveniently load different programs into the computer. Contact GRiD Systems Canada Inc., 2 Park Centre, 110-895 Don Mills Road, Don Mills, Ont. M3C 1W3 (416) 446-1555.

Circle No.53 on Reader Service Card

If you've ever considered turning your technical expertise into money through consulting, Michael A. Neighbours has recently published "How To Become A Consultant In Your Own Technical Field". The author believes that any engineer or technologist with about six years experience or more is probably qualified to work full- or part-time as a consultant; the book offers advice on marketing your services to the technical public. The book is priced at \$25 U.S. from ATC Books, Rt. 2, Box 448, Estill Springs, TN 37330.

Circle No.52 on Reader Service Card

Computer bits: IBM Canada has lowered the prices of the PC and XT micros by 15 to 18 per cent; they have also followed the US firm's lead in lowering the price of the PCjr. Commodore has introduced the 8296 business computer with two drives and 128K for about \$4,000, and Radio Shack in the US plans to start a door-to-door sales campaign for their colour computer.

Microtel Limited is now the official name of the company formerly known as AEL Microtel Limited. The amendment to the company's name, dropping the designation "AEL", became effective on June 1, 1984.

### Selected Addresses:

Robotics Age, The Journal of Intelligent Machines, Box 358, Peterborough, New Hampshire, 03458, USA

(also Robotics Age Product Guide)

Designatronics Inc., Stock Drive Products Division, 54 South Denton Ave, New Hyde Park, New York 11040 USA

Feedback Inc., 620 Springfield Ave, Box 247, Berkely Heights, New Jersey, 07922, USA

RB Robots:  
R.A. Hubbell and Assoc.,  
298 Dundas St.,  
London, Ont. N6B 1T6

Cybernetic Micro Systems,  
PO Box 3000, San Gregorio,  
California, 94074, USA

HHS Microcontrollers, 5876 Old State Road, Edonboro,  
Pennsylvania, 16412, USA

Votrax, Inc., 1394 Rankin, Troy,  
Michigan, 48083, USA,


Votan, 4487 Technolgy Drive,  
Fremont, California, 94538, USA

Ezra C. Lundahl, Inc., 710 N.  
600 West, PO Box 268, Logan,  
Utah, 84321, USA

Hobby Robot Co. Inc., P.O. Box  
887, Hazelhurst, Georgia, 31359,  
USA

MACK Corporation, 3695 E.  
Industrial Drive, Flagstaff,  
Arizona, 86001, USA.

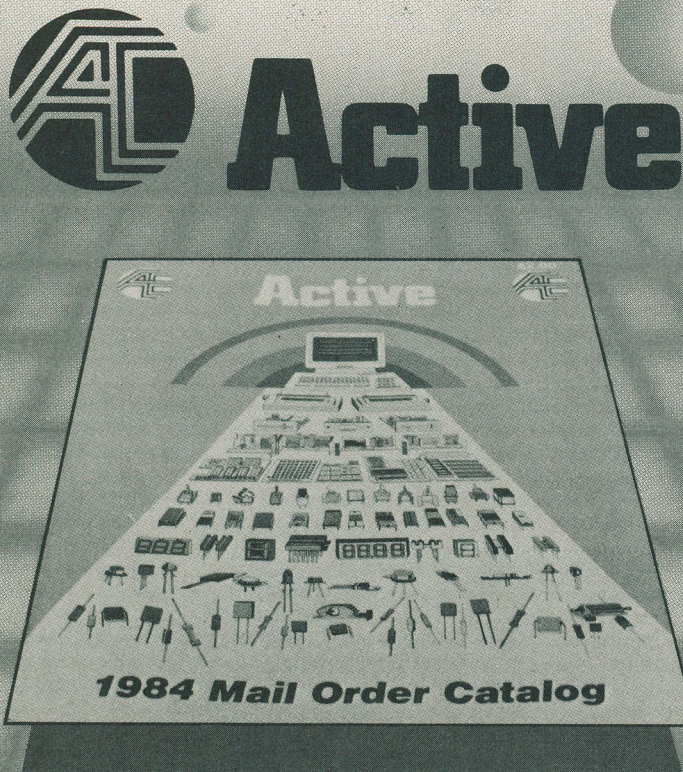Valinco Automation Ltd.,  
Custom Production Equipment,  
Unit 4, 2465 Dunwin Dr.,  
Mississauga, Ont. L5L 1J9 (416)  
828-7411



## The One Stop Shop For All Your Electronic Needs!

Conveniently located across Canada

**Montréal**  
5651 Rue Ferrier  
Montréal, Québec  
H4P 1N1  
(514) 731-7441

**Ottawa**  
1023 Merivale Road  
Ottawa, Ontario  
K1Z 6A6  
(613) 728-7900

**Toronto**  
14 Carlton Street  
Toronto, Ontario  
M5B 1K5  
(416) 977-7692

**Calgary**  
3220-5th Ave. N.E.  
Bay 2  
Calgary, Alberta  
T2A 5N1  
(403) 235-5300

**Downsview**  
86 St. Regis Cr. N.  
Downsview, Ontario  
M3J 1Y8  
(416) 630-0400

**Vancouver**  
3070 Kingsway  
Vancouver, B.C.  
V5R 5J7  
(604) 438-3321

\* Mail Orders to Montreal Address.

Visit your nearest Active store, call, write or circle  
the Reader Service Card for your copy of Active's new catalog.



## MEMORY SPECIAL

4116 150nS NEC	\$ 1.99
4864 1x64K Hitachi 150NS	\$ 7.75
4164 C-3 150NS NEC	\$ 8.50
2716 2Kx8 HITACHI, NEC	\$ 4.99
2732A 4Kx8 TI	\$ 9.00
2764 8Kx8	
Mitsubishi 250NS	\$12.25
2764 8Kx8	
Mitsubishi 300NS	\$11.75
2532 Hitachi	\$ 7.65
2114 200nS (Hitachi)	\$ 2.25
2128-2, 2116, 4016	\$ 8.25
6116LP 150NS Hitachi	\$10.50
TMS 4416 120NS 4Kx16	\$ 9.50
Mc3470	\$ 5.99
2003A	\$ 1.59

Call for quantity price  
OEM Enquiries Invited.


## Japanese Parts Specialists PARTS 100% GUARANTEED

### CPU

Z80	\$ 5.99
Z80A NEC	\$ 6.75
6502A 2MHz	6.99
6502	\$ 6.50
6845 CRT Controller (Hitachi)	\$10.99
6522	\$ 6.99
6850	\$ 4.99
8088	\$32.95
8035	\$11.00
8039	\$12.50
8279	\$ 9.00
8155	\$11.50

### 800 Series for IBM

8088D NEC	\$29.50
8237A-5 NEC	\$29.95
8253A-5	\$16.00
8259A-2	\$10.99
8255A-5	\$15.95
8284A	\$13.50
8288D	\$19.00
UPD 765A	\$45.00
82C43C	\$11.00
82C53-5	\$10.75
8243C	\$12.00

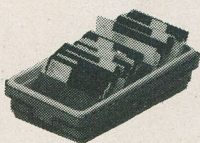

5 1/4 Floppy Disk Case (storage up to 150 diskettes) Lock included

- 1. YJE High Res non-glare Amber Monitor \$169.00
- 2. 52 function numeric keyboard (electronic touch) upper/lower case \$119.00

1. 40-80 Column Switch	\$ 5.00
2. Colour R.F. Modulator	\$15.00
3. Joystick (Self-centering) two adjustable controls	\$39.00

a) 128K RAM Card	\$225.00
b) 16K RAM Card	\$ 59.00
c) 80 Column Card	\$ 79.00
d) Disk Controller Card	\$ 59.00
e) Z80 Card	\$ 60.00
f) Communication Card	\$ 79.00
g) 40/80 Col. soft switch	\$ 19.95

### Diskettes

Maxell MDI	\$ 33.50
Verbatim	\$ 33.50
SKC S/D	\$ 27.00
IBM Compatible	
5-1/4 Slimline double sided double density disk drive.	
MODEL: Matsushita	
JA551-2	\$249.00
Mounting Hardware	\$ 6.99
Full Height Front Panel (to above drive)	\$ 12.50
5-1/4 dd for Apple TM	\$299.00
Model JA550-2 Panasonic Super 5 TEAC Drive or Apple	\$289.00

Service Centre and Retail Outlet, 4051 Sheppard Avenue East (at Kennedy), Agincourt, Ontario M1S 1S8 (416) 298-3280

# Kitstronic

INTERNATIONAL LTD.

(416) 298-3280  
Telex - 065-26150

Mail Orders: Send a certified cheque or money order plus \$3.00 for shipping and handling. For Special Delivery, please add \$1.00 extra. Ontario residents add 7% P.S.T. Visa & Mastercard accepted.

Circle No. 18 on Reader Service Card

## HICKOK MX SERIES DMM's World's Fastest Troubleshooters



**MX333 \$380.00**  
**MX331 \$273.00**

Compact size, unique shape and easy-to-read-from-almost-any-angle sloped display facilitates use as a hand held, bench top or belt mounted instrument.

VARI-PITCH, audible signal on MX333 provides instant indication of the resistance, voltage or current measured for quick and easy troubleshooting. The audible response is instantaneous and proportional to the reading.

- 0.1% Basic Accuracy
- LCD Display In Unique Wide View Case
- Uses Single 9V Battery
- Compact Size. Rugged Construction
- Superior Overload Protection
- Exclusive VARI-PITCH Audible Output (MX333)
- Fast LOGI-TRAK Logic Function (MX333)
- 20Ω Range (MX333)

LOGI-TRAK function on MX333 combines the features of a high performance logic probe and voltmeter in one convenient function. Use any 10:1 high frequency scope probe to measure all logic signals and DC voltages from 10mV to 20V. Audible tone output identifies logic Hi's, Lo's, pulses as narrow as 5 nsec as well as marginal and faulty logic states and pulse trains.

Duty and FST included. Charge (Visa) accepted. Ont. res. add 7% sales tax. Shipping Extra.

**ZAGERS** electronic instruments Ltd.

P.O. Box 310, 595 Mackenzie Avenue Units 1 & 2.  
Ajax, Ontario L1S 3C5. Tel. (416) 683-4211

### CONDENSED SPECIFICATIONS: MX331 and MX333

**DC VOLTS (5 RANGES):** 200mV to 1000V full scale. **RESOLUTION:** 0.1mV. **ACCURACY:**  $\pm 0.1\% + 1$  digit. **INPUT IMPEDANCE:** 10MΩ. **OVERLOAD PROTECTION:** 1000V DC or peak AC + up to 6kV transients all ranges.

**AC VOLTS (5 RANGES):** 200mV to 1000V full scale. **RESOLUTION:** 0.1mV. **ACCURACY:**  $\pm 1\% + 2$  digits. 45 Hz to 1kHz,  $\pm 5\% + 5$  digits to 5 kHz. **INPUT IMPEDANCE:** 10MΩ. **OVERLOAD PROTECTION:** 1000V DC/750 RMS.

**RESISTANCE (7 RANGES):** 20Ω to 20MΩ full scale except no 20Ω range on MX331. **RESOLUTION:** 0.01Ω on MX333, 0.1Ω on MX331. **ACCURACY:** 0.1% + 1 digit except 0.2% on 200Ω, 1% on 20MΩ, and 3% on 20Ω ranges. **OVERLOAD PROTECTION:** 500V DC on RMS all ranges plus 2A fuse on 20Ω range. **TEST VOLTAGE:** Low power, 0.25V max of full scale.

**DIODE TEST (1 RANGE):** Measures forward voltage drop across diode and transistor junctions at 2mA nominal current.

**AC/DC CURRENT (5 RANGES):** 2mA to 10A full scale. **RESOLUTION:** 1μA. **ACCURACY:**  $\pm 1.2\% + 1$  digit DC,  $\pm 2.5\% + 1$  digit AC. **OVERLOAD PROTECTION:** 250V @ 2A all ranges except 10A, max 15A on 10A range.

**VARI-PITCH (MX333 ONLY):** Variable pitch proportionate to reading, off at open circuit. Increasing frequency as resistance approaches "0" on ohms function. Increasing frequency as input increases on volts and current functions. **RESPONSE:** Instantaneous (less than 100 msec.)

**LOGI-TRAK (MX333 ONLY):** 0-20V range using Hickok SP-7 (not incl.) or other 10:1 scope probe. **HI/LO INDICATION:** High or low audible tone. **PULSE INDICATION:** Audible "chirp" plus lighted colon on display. **MIN PULSE WIDTH:** 5 nsec typical. **MAX FREQUENCY:** 80 MHz. **ACCURACY:**  $\pm 0.25\% + 1$  digit + probe accuracy. **INPUT IMPEDANCE:** 10MΩ. **INPUT PROTECTION:** 300V DC or RMS.

**GENERAL: Dimensions:** 2.2x6.7x6 in. (5.6x17x15.2 cm); **Weight:** 22 oz. (.7kg); **Power:** 9V battery (incl.) or Hickok AC adapter. **Battery Life:** 200 Hrs. typical; **Temperature:** 0-50°C operating, -35 to +60°C storage. **INCLUDES:** Deluxe safety test leads, battery, manual and belt clip.

### ACCESSORIES

SP-7 10:1 Divider Probe for Logi-Trak Input	\$66.00
TP-20 (C or F) Temperature Probe	\$96.00
VP-40 40KV DC Probe (0 to 40K VDC)	\$85.00
CC-6 Deluxe Vinyl Carrying Case	\$26.50
RC-3 AC Adapter	\$16.50

Circle No. 19 on Reader Service Card


ETI—AUGUST—1984—11



# ATTENTION OEM / DEALERS PROFIT MAKERS NOW IN STOCK


## Budgetron Inc.

IMPORTER / DISTRIBUTOR / MANUFACTURER

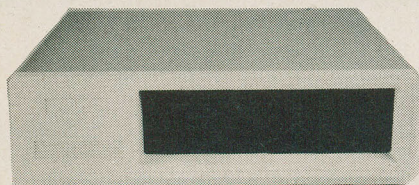
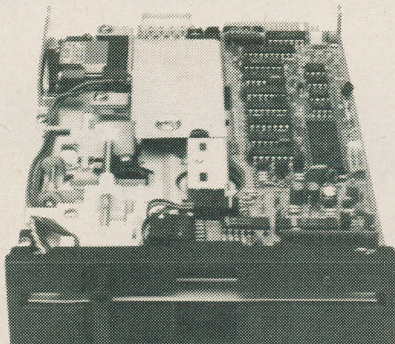
### PC / XT CASE


- 6 expansion slots for PC (8 FOR XT)
  - Cut-outs for I/O and keyboard connectors
  - Full set of hardware includes board mounting plates, card guides, stand-offs and drive plates.
  - Power supply cut-outs with fan hole.
- Exact fit to our 100/130W power supply


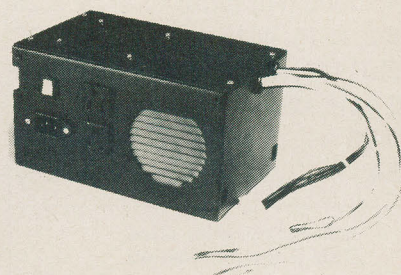
### DOUBLE SIDED DISK DRIVE

**MASUSHITA JA-551-2**  
(same as Shugart SA455)


- Fully compatible with IBM PC/XT
- 500K unformatted, 320K/360K formatted
- Direct drive motor
- 10,000 hours MTBF



### SWITCHING POWER SUPPLY


Exact fit to our PC/XT case

MODEL	RATING	OUTPUT			
		+5V	+12V	-12V	-5V
SPS-I100	100 W	10A	3.5A	0.5A	0.5A
SPS-I130	130 W	15A	4.5A	0.5A	0.5A

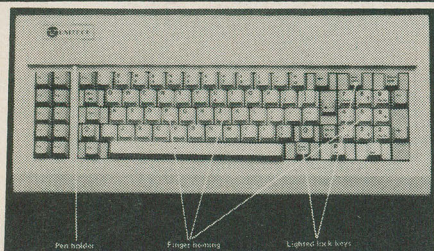
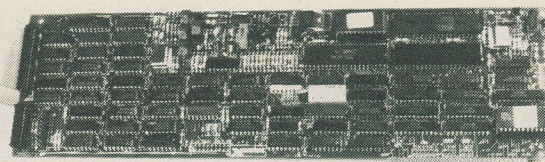
### FINGER FRIENDLY KEYBOARD


- Uses German made cherry keyswitches
- Life time > 20 million operations
- Lighted indicators - Cap lock and No. keys
- Finger homing



### 10 MB HARD DISK SUB SYSTEM

- 100% software compatible
- 10 MB formatted capacity
- Controller plug directly on mother board
- BIOS on board is self-booting
- Cables & manual
- Disk formatted for and accessed by DOS 2-0

Turn IBM pc or compatibles into an XT

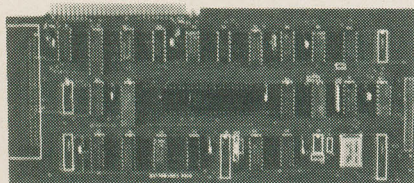

### FLOPPY DISK CONTROLLER

- Controls up to 4 5 1/4 floppy drives
- Software and hardware compatible

### 8 Slots XT Compatible Mother Board

- Fully IBM PC/XT Compatible
- Supports PC DOS, MS DOS, and CP/M 86
- 256K of parity checked RAM
- 8 expansion slots
- Double sided board 8-1/2" x 12" exact fit to our case.

We can supply you BARE PC BOARD, KITS AND FULLY FINISHED A&T BOARD.

### OTHER ITEMS

- Complete PC / XT unit
- Bare circuit boards (mother board, monochrome graphics, controller)
- 4164 ram chips
- NEC UPD 765 AC

IBM is a Registered trademark of IBM Canada Ltd.

### OEM / DEALERS CALL US TODAY

#### Budgetron Inc.

1601 Matheson Blvd., Unit 3  
Mississauga, Ontario L4W 1H9  
Tel. (416) 624-7323

Telex 06-960172 BUDGETRON MSGA




# ETI READER OFFER

## The Movit Memocon Crawler Robot

Price after September 7th: \$119.95

ETI  
Reader  
Price

**\$99.00**

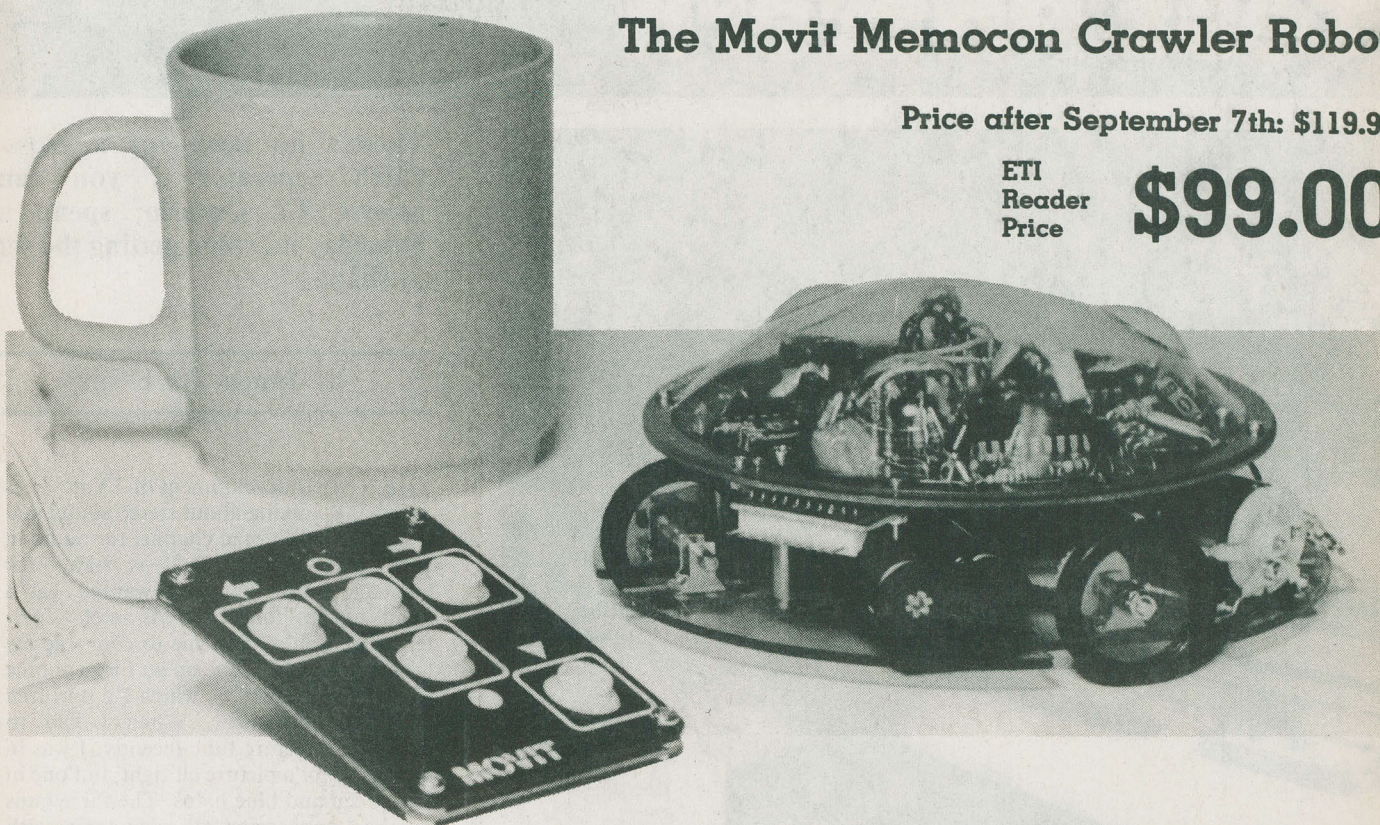

In researching our article on non-industrial robotics in this issue of **ETI**, we came across the **Movit Memocon Crawler MV-918 Kit** which will shortly become available in Canada through dealers – at the moment it is not on sale.

We had a lot of fun with it and have made special arrangements with the distributor to supply it directly to readers at a **special introductory price** prior to its launch in early September. The price will be \$119.00, but we have arranged a strictly-limited-time offer at **\$99.00 only for ETI readers using this offer.**

Fill out the coupon to get your kit now. The kit portion is purely mechanical – the electronics on the circuit board are already built; it takes from one to two hours to complete.

The Robot is controlled through a keyboard during the input stage; you then disconnect the keyboard and the **Memocon Crawler** duplicates the programmed instructions.

There are five modes: forward, left, right, sound a "beeper", and light an LED; a pause step can also be built into the program. The robot uses a sequence function static RAM 256 X 4 bit memory. The inputted program repeats itself once it has completed its routine. Up to 256 steps can be put in, each step representing a preset motion forward or a segment of a turn.

There are three wheels and two

motors. The robot needs a 9V battery and two AA alkaline cells.

No instructions are given for connection to a larger computer but the operation and connections should present few difficulties.

This special ETI Reader Offer must close on September 7th and will not be extended. **Order now and save yourself a genuine \$23.**



**Yes, I'd like a Memocon Crawler and enclose payment of \$99.00 plus \$3.00 for shipping. Ontario Residents please add 7% PST.**

☐ **Cheque or Money Order.**

☐ **Bill my Charge card: Visa, Mastercard, American Express.**

**Card No.** ..... **Expiry date** .....

**Name** .....

**Address** .....

**City** ..... **Province** ..... **Post Code** .....

**Mail to: Robot Offer, Moorshead Publications, 25 Overlea Blvd., Suite 601, Toronto, Ontario M4H 1B1**

**Please allow four weeks for delivery.**

**Offer Expires September 7th, 1984.**



# Alignment by Test Pattern



The Toronto control room at TV Ontario. Photos courtesy of Gord Kent, TV Ontario.



There's no need for a cross-hatch generator if you can receive TV Ontario; spend a Saturday morning getting the set in shape.

---

by James W. Essex

---

THE RAPID development of TV now has authorities talking about stereo sound and a separate additional channel for audio in another language. This is okay for language buffs, but all I wanted was a good old-fashioned "cross-hatch" pattern that would allow me to converge my triad-type picture tube on an Electrohome Chassis, vintage 1977, which I'd nurtured since my retirement. When I had to replace the picture tube recently, I was in trouble. I got a picture all right, but one in red, green and blue halos. The three guns required converging all over again with the new tube.

When I was with Electrohome, of course they had their own "in-house" convergence signal which included a "cross-hatch" pattern alternating with a "colour-bar" pattern. But they also had their own "in-house" rules and only bona fide repairs were allowed entrance. Even when employed there, you couldn't have taken a test generator home, although most technicians would have liked to have kept their own sets "up to snuff". I recall one foreman who attempted to get around this by asking the local TV station outlet to broadcast a "cross-hatch" to facilitate his technicians' checking out of their own sets at home. But all we received from the TV station was a big yawn. After all, to get good "whites" and no "halos", the three guns have to cover off — exactly. But without a "cross-hatch" pattern, it's virtually impossible to get a good picture. I valiantly tried "lining-up" the three guns for the brief spell when a Tide commercial was on, but all I got was T-I-D-E in red, green and blue. I never did get my washing white. What to do?

Then I remembered TV Ontario — the Ontario Educational Authority. Why, only recently they ran a complete course in computers. Would they offer the same help with TV?



As it turned out, Gord Kent, Supervisor of Master Control for TVO, was already thinking the same thing. Kent wrote the following:

"For a long time, I have felt that there might exist the need among our viewers for this type of test signal, or at least something other than colour bars. It was your original letter forwarded to me that gave me the needed 'push' to do something about it.

Following the first transmission on Saturday, January 14th, I arbitrarily decided to continue the transmission on a trial basis on Saturday mornings for an indefinite period awaiting any feedback, positive or negative, that might be forthcoming. I assume that Saturday (and possibly Sunday) would be the best day for most handymen and part-time technicians."


Kent of course, was referring to the help TVO already had given me when Doug Hanley of the same genial TVO staff, had already phoned me to "stand-by" that first Saturday morning in now distant January, in response to my call for help. This was followed by another from Dennis Roy, also with Master Control of TVO, that a "cross-hatch" was being transmitted for a half-hour beginning at 8 a.m., January 14th, 1984. I'm sure the pattern has been helping hundreds like

myself since. This has been reinforced by Kent's subsequent comments:

"As indicated above, I recognize that the colour bar has limited usefulness to a viewer or anyone not having a vectorscope at his disposal. It certainly cannot be used for convergence adjustment or linearity. The colour bar has another disadvantage too. If left on for an extended period, the white chip will burn in, leaving a permanent dark square on the screen. For that reason, we transmit a 50% grey signal during non-program hours since we have a number of low power transmitters scattered across the province which operate 24-hours per day."

All of which means I don't get a "burn" on my picture tube and I can now converge to my heart's content. And while it's true that those with TVs having Trinitron picture tubes don't have to worry (the convergence is integral with each picture tube), there are many, many triad picture tubes extant which need convergence checks and/or converging. Without TVO's test signal, you might never have the opportunity to correct this.

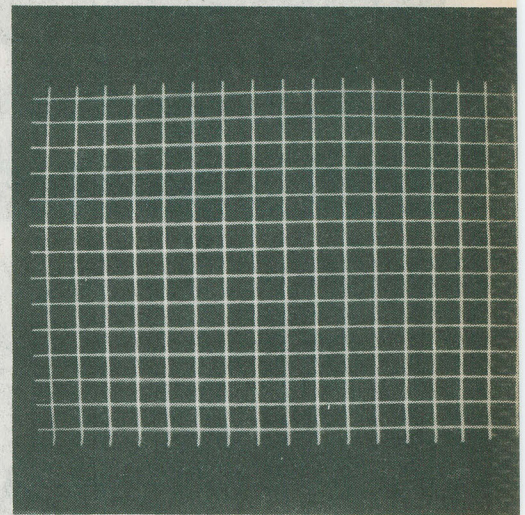Now, if you have any qualms about why JR's cowboy hat has peculiar red, green, or blue lines outlined on his otherwise picture-white hat, you have only to tune to TVO any Saturday morning at 8 a.m. to check it out. With judicious set-



The alignment cross-hatch test pattern.

tings of three knurled knobs on the convergence board surrounding the picture tube, you too can make it all come out right, and those big, bold "T-I-D-E" letters in that ubiquitous commercial will once more be "picture white".

ETI

## CATCH UP WITH ELECTRONICS TODAY

COMPLETE YOUR COLLECTION  
OF ELECTRONICS TODAY  
NOW. FILL OUT THE HANDY  
COUPON AND MAIL WITH  
YOUR PAYMENT TODAY.

See order form in this issue for  
full complete list of available  
back issues.

### ELECTRONICS TODAY

Back Issues

Moorshead Publications,  
Suite 601, 25 Overlea Blvd.,  
Toronto, Ontario M4H 1B1.  
List desired issues below.

☐ Cheque or ☐ Money Order  
for \$4.00 per issue. (Postage  
and handling included.) Pay-  
ment must accompany order.


Total amount enclosed

\$ \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

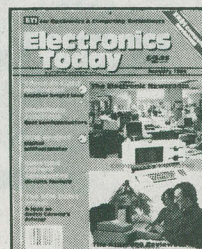City \_\_\_\_\_ Province \_\_\_\_\_ Postal Code \_\_\_\_\_



JANUARY '83




FEBRUARY '83



MARCH '83



APRIL '83

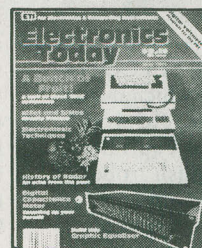

MAY '83



JUNE '83



JULY '83



AUGUST '83



SEPTEMBER '83



OCTOBER '83




NOVEMBER '83



DECEMBER '83



# Robotics: Home and Educational

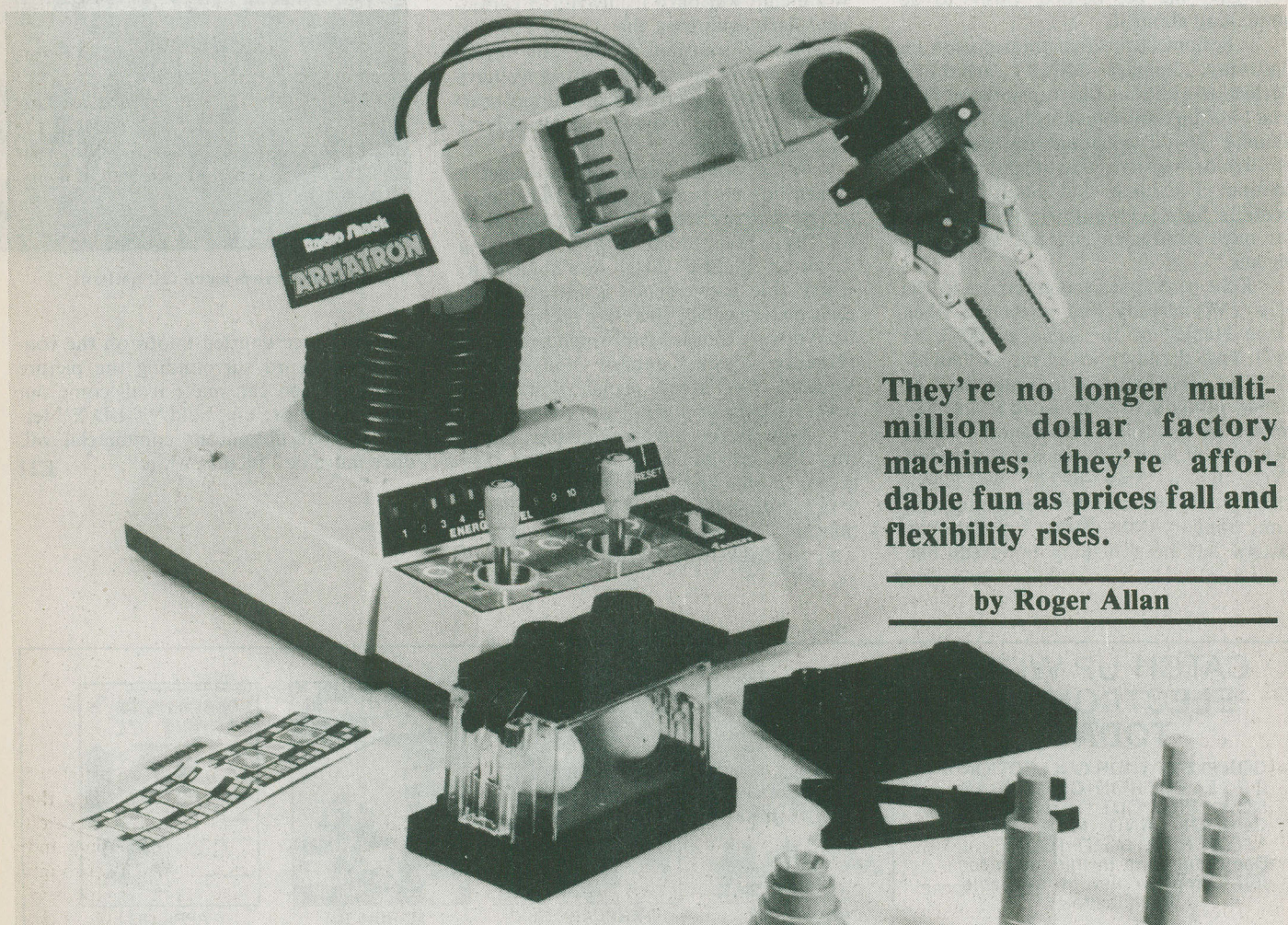

**They're no longer multi-million dollar factory machines; they're affordable fun as prices fall and flexibility rises.**

---

**by Roger Allan**

---

THE DEVELOPMENT of robots has its roots in the Middle Ages, and is concurrent with the increase in man's ability to manipulate things mechanically. The greatest degree of sophistication, and the area in which the greatest amount of work and thought was placed, occurred in the development of clocks — the intricacy of their internal structures stretching engineering abilities to their limits. After all, to pick something up requires a high degree of mechanical sophistication (unless one is prepared to have it alternately crushed by too much force or dropped on one's toe from too little), an engineering ability derived from a knowledge of gears, torques and smooth movements — knowledge predicated, at least until recently, in the construction of clocks.

## **Bits of History**

But what actually is a 'robot'? In Gothic, there is a word akin to robot which means 'inheritance', and in German, 'to work'. An old Slavic word, and near equivalent, is 'rabota'. In Czech and Polish 'robota' means 'servitude' or 'forced labour'. It was first used in its contemporary context in 1921, in the title for the stage play *R.U.R.* (Rossom's Universal Robots) by the Czech playwright Karel Capek; the play was a self-styled 'fantastic melodrama' in which robots, constructed without any feelings or soul ("God hasn't the slightest notion of modern engineering") do all the world's work, wage all the world's wars and finally rebel and destroy their makers. After all, as the leader of the robot rebels tells the General Manager of the factory that produced him (it?), "You

are neither as strong nor as skillful as we robots. I want to be master."

But despite the mere 60-year age of the word 'robot', and their technical basis in watch and clock making, robots have been cropping up in history for quite some time. In about 375 BC Archytas of Tarentum built a robot bird which flew (or so he records). *De Automattis* written by Hero of Alexandria in the 2nd century BC, tells of a theatre in which robot figures danced at temple ceremonies. In the 1490s, Leonardo da Vinci constructed a robotic duck which walked and flapped its wings (powered by a coiled spring — shades of clocks). In 1750, Jacques de Vaucanson constructed another duck robot. It stretched, took grain from the hand, swallowed and seemingly digested its food, leaving deposits behind. Johan Nepomuk Mael-



zel, in the early 1800s, built a robot orchestra of some seven instruments, for which he commissioned Beethoven to compose his *Vittoria Symphony*. Regretfully, Maelzel's other robot, this one a robotic chess player, was taken on a grand tour through Europe and North America and turned out to be more circus carney than robot. It was actually operated from the inside by a hunchbacked Alsatian dwarf named Schlumberger. But giving credit where credit is due, Maelzel's Panharmonium did work. There are many other examples of descriptions of robots in history. In the realm of mythology, the first humans were robots formed out of clay by the Titan Prometheus. In the realm of literature, perhaps the most noted example, courtesy of the fertile mind of Mary Shelley, is Dr. Victor Frankenstein's triumph in creating The Monster.


## Definitions

Technically therefore, a home robot can be any one of a number of things: a device to play music, flap its wings, pour drinks, whatever. However, with the rise of automated industry and a concomitant rise in logic circuitry capabilities, robots 'took off' as it were, and in all sorts of directions, so much so that it is difficult to find a definition that can be agreed upon (see 'Industrial Robots,' ETI, Feb. 1982). Its taking off was no longer dependent upon the abilities of watch makers, but upon the rise of the nuclear industry (requiring sophisticated manipulators to work in hazardous environments), war casualties (and the research into artificial limbs), and the rise of the computer industry (logic processing). Putting them all together, robots today are in a state of "expectant euphoria" according to one industry source, somewhat akin to the first microcomputer introduced in 1976 — a development without a stated purpose. By this, one doesn't mean that the massive robots employed in industry do not have a purpose: spray painting car bodies, lifting heavy objects out of furnaces, or even as at the Fujitsu Farroke plant in Japan, manufacturing other robots — quite obviously they do. But rather, the smaller robots, the ones one can find around the home or schools or light industry, have a purpose which is ill-defined and in a state of flux.

Perhaps the best coalescence of the problem (if it is a problem) is to repeat the quote by Douglas Bonham, U.S. director of educational applications for the Heath Company during the introduction of the HERO I robot. He stated that what they are good for, other than to teach people what robots can do, isn't really apparent, but that, "we hope the backyard tinkerers and inventors will come up with applications for it." In other words, it's similar

to the introduction of the home computer offered to the electronic hobbyist market without any definite use, but computers have blossomed into a billion-dollar a year industry with applications cropping up in some of the unlikely places.

Such is the industry feeling about the home robot. At the moment, it's really only just 'fun', but the backyard tinkerers and the industry as a whole are beginning to find applications for it. Whether the industry takes off as did the microcomputer, remains to be seen, but the indications are that it very well may. The oft repeated question, "But will they do windows?" is rapidly becoming a question that can be answered in the affirmative.

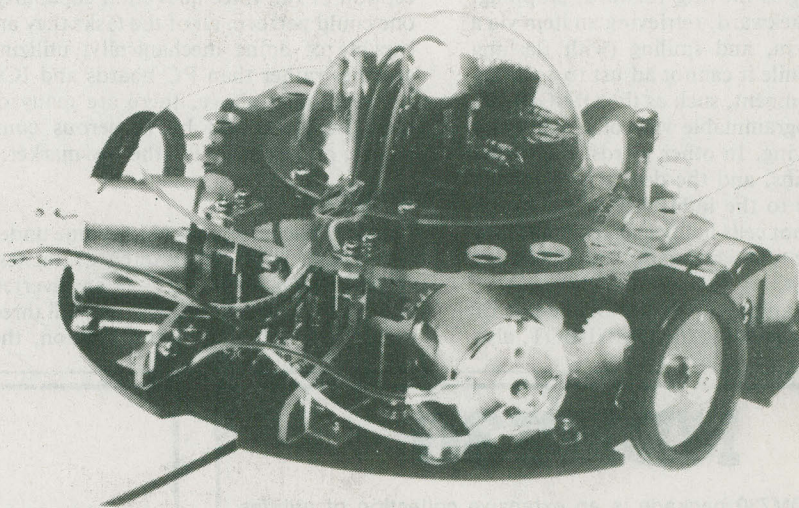

The MOVIT Line Tracer is similar in design to the crawler, but its main function in life is to follow a black line with its infra-red sensing device.

The groundwork is in place. While this author has been unable to locate any true home robot manufacturers in Canada, there are more than 100 companies in the U.S. manufacturing complete robots, robot kits, peripherals, vision systems, software languages and addendums (and they *can* do the vacuuming — more later). There is a national magazine (glossy, subscriptions high) entitled *Robotics Age*, which recently published a sourcebook for educators and experimentalists in robotics. The first International Personal Robotics Conference was held in Albuquerque, New Mexico, two months ago, and had delegates from around the world.

## State Of The Industry

But what actually is the state of the industry, ranging from the minor to just shy of the industrial grade machines? Is the potential for a \$2 billion a year industry in home robots by 1990 fact or fiction? After all, home computer companies, such as Atari, Coleco, etc., have almost fallen flat on their faces with the home microcomputers (Atari lost \$560 million U.S. last

year), though it was only a year ago that their industry spokespersons were projecting that their manufacturers would not be able to keep up with demand. And what of the experimentalists of the backyard variety, upon whose shoulders rest the development of robotics applications around the house? Will they rise to the occasion as did the microcomputer hackers? One cannot say, other than that the potential is there.

Lets' start at the bottom-of-the-line machines, those just a fraction ahead of wind-up clockwork toys. There are any number of manufacturers, all extolling the virtues and humour derived from their machines. There are all sorts of models,

far too many to catalogue in an article of this length. A few examples: perhaps the best to start with are those manufactured by the MOVIT company of Japan and widely sold in Canada, primarily through toy shops. They have eleven inexpensive models all in kit form. An example is the MOVIT Monkey MV-919 (assembled and ready to run) or the MV-929K (in kit form); Essentially cylindrical in shape, with what looks like a miniature elephant's trunk sticking up and out from the front of the body (containing a microphone at its end), with two plastic arms reaching up and in. One ties a piece of rope across the room and hangs the device from it. Loudly crying "Move!" or clapping one's hands results in the robot beginning to swing itself along the line hand over hand, just like a monkey. After a while it stops. Its movements are via two alternately moving gripper arms driven by crank motions, while its control is via a sound sensor which includes a condenser microphone. Its power is via two 1.5 volt "N" type batteries. Sophisticated? Not really; it's more of a novelty than anything else.



## Robotics

Slightly up the line is one manufactured by the TOMY company, marketed in Canada, which sells for about \$20. Called DING-BOT, it looks like a little robot and is battery powered. It's a bit more complex than the Monkey, in that it moves forward until it encounters and object. It then stops, turns it head from side to side, chatters away with a chirping sound, then turns right and goes off. Battery powered, it comes with its own 'map' that only it can follow. A somewhat up-market robot, also sold by TOMY is the VER-BOT. Looking a bit like R2D2, it possesses a memory with eight separate functions. It is voice activated and can, when activated this way, perform simple tasks such as moving forward, stopping, moving backward, retrieving an item via a gripper arm, and smiling (with flashing lights). While it cannot adjust to a changing environment, such as the DING-BOT, it is reprogrammable via voice activation while moving. In other words, the owner is the brains, and the device is the slave, analogous to the industrial robots which enter the hot cells in nuclear reactors; they have to be told what to do and when they are to do it.

An example of the top-of-the-line of this sort of robot is the OMNI-BOT, also

manufactured by TOMY. Looking like a largish version of the VER-BOT, it is radio controlled, as well as being able to repeat a series of commands. It can repeat these programmed functions at a later time through an on-board clock/tape memory. It can speak or deliver messages via an on-board computer and a tape cassette, enabling it to carry on a dialogue with humans and to carry items like slippers, drinks and snacks. Real time programming is possible via the radio control hand held device. It retails for about \$300 Canadian.

Essentially therefore, the first category of home robots are really nothing more than novelties. With the exception of the voice activation capability, one could perform all of the tasks they are capable of doing mechanically, utilizing switches rather than PC boards and ICs. As mentioned above, there are many of them manufactured by numerous companies, all primarily for the toy market.

### Turtles

The next level of home robots come under the general umbrella heading of turtles. Generically, a turtle is simply an inverted bowl shaped plexiglass housing, with three wheels in a triangular configuration, the

two on either side being power driven, usually by battery operated DC motors. Again, there are a number of manufacturers and types (even MOVIT, mentioned above, markets several versions), but they are a distinct progression towards what is customarily considered a true robot. Three examples:

The Line Tracer II, manufactured by Stock Model Parts and part of the MOVIT series, utilizes an infrared light sensor to guide it along any drawn black line pathway. A black felt-tipped marker or cap, can be used to create the straight or curved pathway, providing that the line is at least 3/8 of an inch wide and is on white paper or a white floor area. Sold in kit form (retail \$44.95 U.S) and taking about 2 hours to build, the Line Tracer II is primarily designed for school science projects and introductory robotics courses which teach how infrared sensors work.

A second example, also sold by Stock Model Parts, is a programmable robot controlled through a seven function teaching pendant (one disconnects the pendants after having entered the program) or via a microcomputer having a parallel interface. Called the Memocon Crawler, and sold as a kit, the robot includes an on-board CMOS static RAM

## MDM730

The MDM730 package is an extensive collection of utilities and patches for this unspeakably powerful code. It includes MDM730 itself, DOC files, M7LIB to change the phone numbers, M7FNK to meddle with the macro function keys and all the overlays we've been able to collect.

If you are interested in hacking yourself a version of this program... and are familiar with the nuances of 8080 code... here's a quick and easy way to get the code and the overlay source.

Just  
**\$19.95\***

Available for Apple CP/M, Access Matrix, Kaypro II, Lobo max 80, Morrow Micro Decision, Olympia single and double, Superbrain, Systel/Olympia, DEC VT-180, Nelma Persona, Xerox/Cromemco, 3R Avatar, Casio FP-1000, Epson QX-10VD, Attache, Micromate, Sanyo MBC 1000, Televideo, Zorba and on eight inch single sided single density disks.

Please note the following things

Thing 1. This code is all in the public domain. The charges for this package defer the cost of handling and postage.

Thing 2. If you are into hacking code you will freak when you see this. We are unable to answer questions about how to get this thing running... you're on your own.

Thing 3. Apple users are urged to check out the Apple MDM730 package offered elsewhere in this issue.

\*Thing 4. \$24.95 for Osborne, Olympia Single, Apple, Lobo, Xerox/Chromemco and eight inch versions.

**Moorshead Publications**  
Suite 601, 25 Overlea Blvd.,  
Toronto, Ontario M4H 1B1.

## Apple Wordstar Fixer

Apples and Wordstar are not entirely friendly. Apple compatible systems equipped with Videx type eighty-column cards do a number of unpleasant things to this popular word processor. While there are simple cures for this... they all involve some delicate code hacking.

The Fixer solves this problem. Place it on the same disk as your copy of WS.COM, type FIXER and after a suitable amount of disk noise, you will have APWS.COM on there too. This version of Wordstar includes special patching and unhooking code which runs each time you boot Wordstar, and makes your fruit behave as it should. It releases the control K's, translates the left arrow key to a delete character, and patches Unitron keyboards.

In addition all of this, the fixer allows you to set some of the defaults of Wordstar which the MicroPro INSTALL Package doesn't really get to. All of these features are menu driven in English for absolute non-technical operation.

Fixed Wordstar will run in either 44K or 56K CP/M.

Only  
**\$19.95**

*Ontario residents please add seven percent*

**Electronics Today Software**  
**25 Overlea Boulevard, Suite 601**  
**Toronto, Ontario**  
**M4H 1B1**



256X4 sequencer. If the teaching pendant alone is used, a program can be entered to the robot's memory for it to go forward, right, left, pause, sound a buzzer, or light up an LED lamp. It repeats the program continuously.

A third example of a turtle is the ARMADILLO model EMR 1020 manufactured by the Feedback Company. It represents the middle ground between robots as toys (above) and robots as educational devices (though most manufacturers insist that their robots, no matter how simple in construction, represent an educational tool). This device requires connection to a computer, either a ZX81 (Timex Sinclair 1000), and AIM 65, or similar. The ARMADILLO has LED eyes that blink, and a beeper in two tones. When directed by the computer, it will press down a pen and 'draw' or chart its programmed progress on paper. Under computer control, it will run around forward, backward and to the right or left. Each of its three wheels is independently controlled. The difference between this turtle and those mentioned above is that it's 'environmentally sensitive', that is, touch sensors attached to the ARMADILLO's shell send data back to the computer whenever the robot encounters an object. The reprogrammed computer then directs either evasive or exploratory

action. Its interface with the computer consists of four circuit blocks. The first is address and address decoder operating on the top ten address lines to produce an output only for a certain bit-pattern corresponding to a particular address (specifically, the ARMADILLO itself). The control circuitry determines, in conjunction with the output from the address decoder, whether the computer is writing data to the robot, or reading data from it. The latch accepts data from the computer at specific times and stores it until the next time data is sent to the machine. The buffer transmits data from the robot when the computer is ready to accept it. As such, the circuitry enable the robot to be treated as a memory-mapped I/O device; in other words, data can be sent to and from the robot as if it were another memory location in RAM or ROM.

Essentially, then, in the realm of turtles there is a spectrum of capabilities, ranging from glorified toys to devices that are capable of interfacing with the environment and reacting to it. The major drawback of this type of robot is that they just move around the floor.

### Adding Grippers

The next generic classification of home robots runs the spectrum from near toys to light industrial grade devices under the

umbrella title of 'grippers'. Grippers are essentially arms which are analogous to the human arm and hand; they can extend, twist, roll and grip through a variety of axes and motions. There are at least a dozen manufacturers of such devices in North America, each manufacturer having a variety of models. Only three will be discussed here, along with an addendum.

An example of a bottom-of-the-line device is a \$44.95 item manufactured by the Tandy Corporation (Radio Shack) and called the Armatron Robot Arm. All command functions are via two joysticks that guide all of the robot arm motions. The arm can be controlled to rotate left or right, move up or down, and bend at the elbow. The hand assembly can also be raised or lowered. Turning the joystick levers, opens the grippers up to two inches for gripping, picking up, moving and releasing objects. It is provided with rubber-coated pinchers for gripping. Essentially, as a toy it can be used to play games (placing it alongside a chess set and having it move the pieces, for instance) or as an educational device to teach robotic arm movements, what they entail and how to think through motions.

Two examples of up-scale grippers, from the many available, are taken from the Feedback Company's product line. The first is the ARMSORT Model PPR



The Armovert SSA 1040, an instructional robotic arm designed for control by an external computer.



## Robotics

1030. It was designed to illustrate the method of controlling stepper motors, solenoids and other robotic functions by using a properly programmed microcomputer. It comes with a magazine and a variety of resistors. Under computer control, this device moves its end of arm tool to the magazine and extracts a resistor. The value of the resistor is measured, converted to digital data and presented to the computer. The control program allows the the computer to search for up to 10 resistance values in preset tolerance bands. Each specified value of a resistor can be automatically placed in a predetermined storage location. Out-of-range resistors are rejected. When the magazine is empty, the robot halts and requests further instructions. It can continue to sort a refilled magazine or print out a summary of resistor sorts to date. Its 'personality pack' contains a software cassette or diskette, printout program (BASIC), flowchart program, and interface card and an interconnection lead to be placed between the robot and the microcomputer. Linear and rotary movement are provided through stepper motors, with resolution of 48 steps per revolution. They are geared to permit accurate positioning of the gripper. The two-fingered gripper is solenoid operated. When it picks up a resistor out of the magazine, a constant current circuit is completed. The voltage drop across the resistor is measured. The analogue value is converted to digital form and presented to the external computer.

The BASIC program attached to this device is quite straightforward. The ARMSORT introduces itself to the computer screen with, "Hi! I am an intelligent robot! I can perform a useful function by sorting mixed resistors into a number of stations in accordance with your instructions. My working resistance range has been set to 0-750 ohms. Above 750 ohms I make mistakes. First, drive my arm to the magazine, using the keyboard."

The device then asks the operator to select up to 10 stations, to select a choice of resistor values, and to give the resistor value and drive it to each station in turn. Then when the robot fails to pick up a resistor, it will request further instructions and/or give a summary of those selected.

Another example of a gripper is also taken from the FEEDBACK line, specifically the ARMOVER. It simulates full-scale industrial robots via interfaces with an Apple II (or clone). They simulate the actual production situations through waist rotation, shoulder bend, elbow bend, wrist pitch and wrist roll. The 'intelligent' gripper senses if it is holding an object or not, and can judge the size of an object to within 1/6 of an inch. Through parallel fingers, the versatility of the robot is increased over that of pincer-grip

models lower down the model line. Low force levels forgive operator error, unlike full-scale industrial robots with which accidents can result in product damage. Its movements are via tendon technology, that is, the type of cable control used in aircraft. It is an educational device, or for the serious hobbyist. Another gripper arm is the device Armdroid 1, from Valinco Automation. It can be controlled by an apple computer, and includes software.

In the range of grippers, one now starts to bump into industrial production devices, such as those manufactured by the MACK Corporation in their B.A.S.E. line of robots, and as such are beyond the scope of this article.

Essentially, then, grippers are "set in place" devices reminiscent of industrial robots. They cannot move. Turtles move, but cannot grip. It is in the combination of these two generic types of capabilities that the true home robot emerges. There are not many such devices on the market as yet, but two give a good indication of what's available: Heathkit's HERO I and RB Robot Corporation's RB5X.

### HERO

HERO I has been around for a while, and is perhaps the best known of such devices. It comes either in a kit (\$1779) or assembled (\$3395). It is an intelligent, mobile robot, incorporating the generic qualities of the turtles with those of the grippers. Reminiscent of R2D2, it stands about 20 inches tall, weighing in at 39 pounds. It is self-contained, operating on an electromechanical control foundation. It is controlled by its own on-board programmable computer and carries electronic sensors to detect and qualify light (1 part in 256, 30° angle), sound (resolution 1 part in 256, approximately omnidirectional), range (pulsed ultrasonics, resolution 0.42 inches at maximum range of 8 feet, horizontal and vertical beam width approximately 30°), motion (continuous wave ultrasonics, sensitivity resolution of a human at 15 feet), speech (synthesized phoneme-based system, 64 phonemes and time measurement). It moves on three wheels, has a head that rotates, and an arm with a gripper on the end which can pick up an object weighing a maximum of 225 grams. Its microprocessor (4K memory) is a 6808 which interfaces with all sensors, on-board real-time clock, experimental circuit board and drive motor. It is programmable through a hexadecimal multi-function keyboard mounted in its head, an external teaching pendant, or through directions carried on a standard cassette tape recorder pre-programmed via a computer. The microprocessor has seven operating modes: executive, utility, program, repeat, manual, learn and sleep. It therefore incorporates all the basic systems found in contemporary industrial


robots, with the added ability of mobility. While classed as an 'intelligent' robot, it cannot in fact learn from its environment.

The top of the line device currently being massed-manufactured is RB Robots' RB5X which comes as close to the lay persons' idea of what a home robot can do.
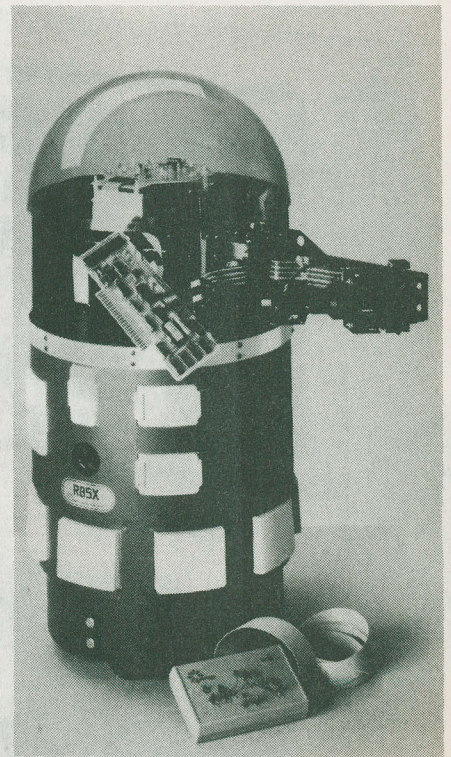
### RB5X

The RB5X stands about 23 inches high and weighs in at 25 pounds. It can do everything that the HERO I can do, and then some. The 'then some' is 'quite some'.

Its biggest difference (in part due to it having a later design than the HERO I and having a 64 K memory on-board as opposed to HERO's 4 K) is that it is the first of the truly intelligent home robots. It learns from its own experience, progressing from simple random responses to an ability to generalize about the features of its environment and to make predictions about its environment. For example, when the RB5X, equipped with its standard sonar and tactile sensors, encounters an object in its path for the first time, it chooses from a table of random responses — turn left, turn right, whatever. When one of these responses proves successful in allowing the RB5X to continue moving, the robot stores that information in memory (either in RAM,



**RB Robot Corporation's RB5X.** This one will vacuum your rug, put out your fire, fetch your paper, and walk your dog, not to mention countless other possibilities. It doesn't do windows, though.







# Model Railway Switch Controller



This project employs a capacitive discharge type power supply to drive the solenoid actuators in model railway turnout switchers. An add-on indicator unit can be used in conjunction with it to show which way turnouts are switched at any time.


by Jonathan Scott

THE IDEA of using a capacitive discharge supply to drive the solenoids in model railway turnout switchers is not new. Indeed, you can buy these at hobby shops for \$20 or so, if you are not inclined to build one for yourself. However, this project incorporates refinements you may not have seen, along with a system of indicating the state of turnouts modelled after the fashion of the 'professional' signal box lighted map.

The capacitive discharge supplies bought 'over the counter', generally charge a capacitor of one to two thousand microfarads via a current limiting resistor from a rectifier and an AC source. This is quite adequate, but can be refined. If you charge the capacitor from a constant current source, it charges somewhat faster and one can provide an 'unready' indication while it's charging. The little extra speed one gains in charging is handy as several switches often need to be changed in a short space of time and one's fingers dance from button to button when doing so.

With either system, the current limiting arrangement protects the solenoids against burnout if the supply happens to be accidentally connected indefinitely. The simpler system almost invariably incinerates something if you get a short somewhere.

The idea behind the capacitive discharge method is simply that the switch changes in the first hundred milliseconds or so; any other power delivered is wasted. The high momentary current capability of a capacitor means that the solenoid always moves quickly. When you connect the charged capacitor to the switch solenoid, it will deliver a very high current which rapidly subsides to nothing or, at worst, the charge current which can

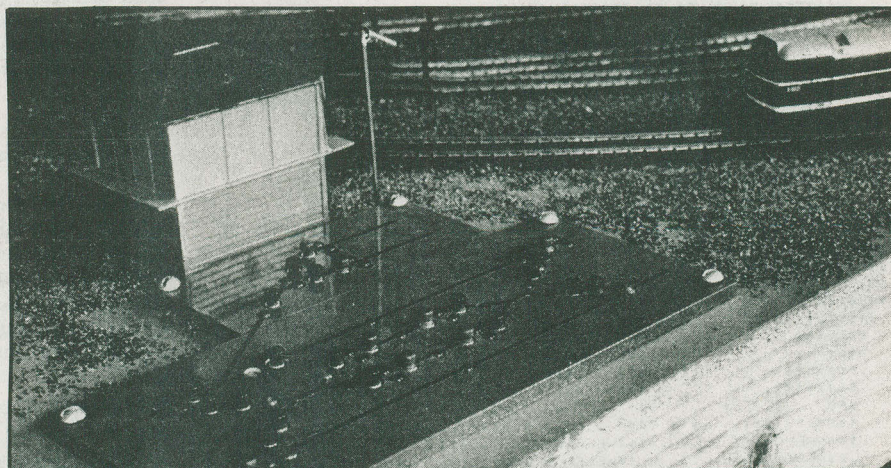

Signal map. This shows a view of one of my signal maps with the switch pushbuttons and indicator LEDs installed.

be much less than the current required to actuate the solenoid. Thus, the solenoid remains cool even if connected (by some accident or other) indefinitely, avoiding burnout of the solenoid.

The outline of a capacitive discharge supply is shown in Figure 1, along with the outline of a 'remote point indicator', or 'remoter'.

The remoter is simply a 'memory' circuit which records which way the switch was last changed. I used a simple flip-flop for this. Two LEDs or lamps are used to indicate the switch's condition. These may be built into a signal map panel. This is basically just a line diagram of a track layout, or part thereof, with lights and switches in the symbolic positions of the actual switches on the track layout. Train signal lights are also usually included on the map along with train position sensors, if used.

There is, of course, no need to have remoters. They are purely conveniences, rather than necessary functional items. Remoters are primarily important if you wish to have a layout which is as much like

the 'real' thing as possible. However, for the few dollars or so extra cost each, they add a very pleasing touch of realism.

You can have any number of turnouts in your layout and you'll only need one capacitive discharge supply unit. The one described can easily drive three turnouts simultaneously if you need to operate some of them together. One remoter is needed for each set of turnouts.

## Construction

Construction is relatively brief. The only part we can really cover here is the assembly of the pc boards and with the usual exhortation "assemble the boards according to the overlays," it's nearly all over!

There are two pc boards: the capacitive discharge supply, and the other is for remoters. Let us take the supply board first. It is easiest to mount the diodes and resistors first, then Q1 and IC1, followed by the capacitors. Take care with the orientation of the diodes and transistors as well as C1 and C2. Note that Q1 and IC1 should have heatsinks attached. You can make these from a scrap of aluminum; each heatsink should be at least 25 sq. cm in area. They can be bolted straight to the face of each device, but don't forget to smear on thermal compound first.

You may or may not wish to mount the 'charging' LED (LED1) off the board; such as on the front panel of your controller, for example. This is a good idea if other people are using your layout, as it helps them allow for the necessary delay


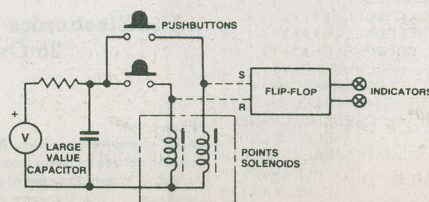


Fig. 1 The controller indicators scheme.

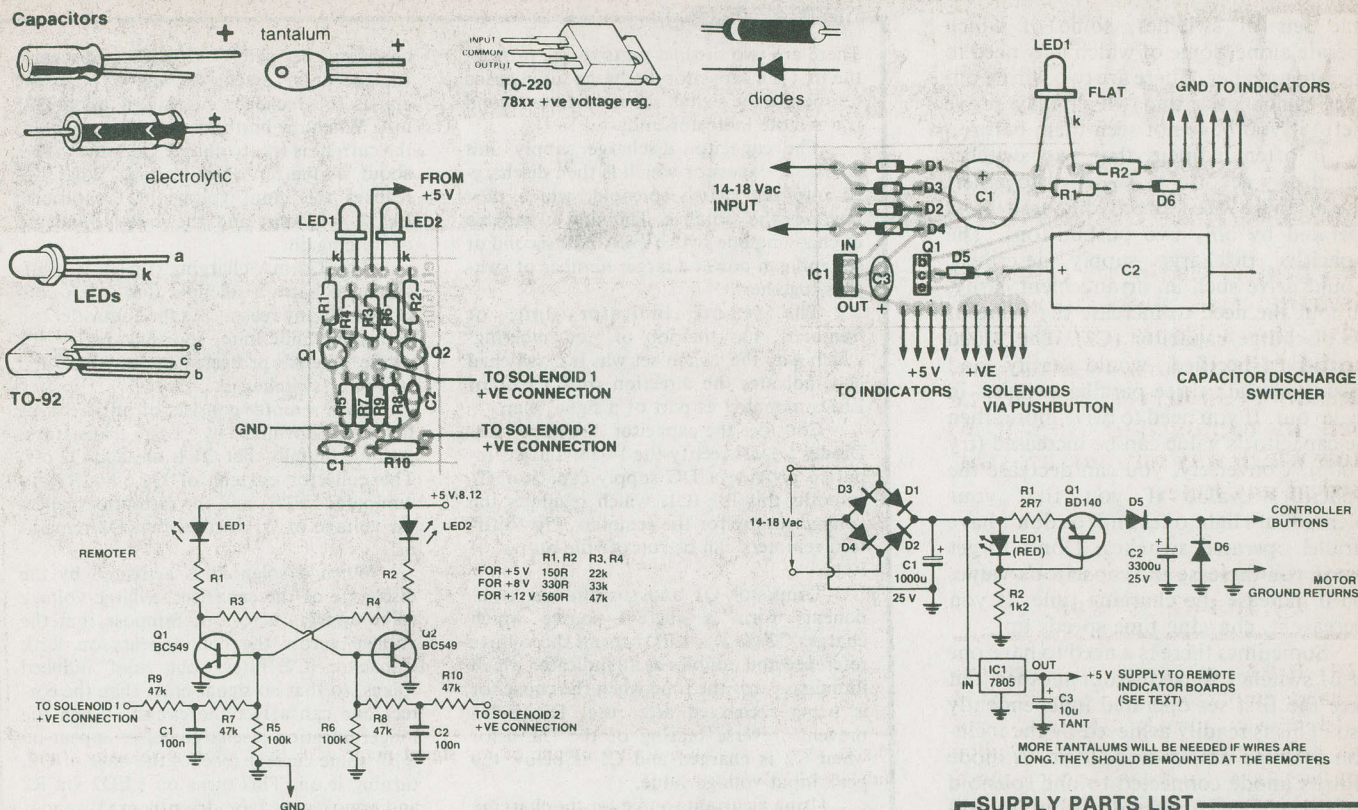



#### REMOTERS PARTS LIST

##### Resistors

R1, R2	see text, circuit
R3, R4	see text, circuit
R5, R6	100k
R7, R8, R9, R10	47k

##### Capacitors


C1, C2	100n
--------	------

##### Semiconductors

LED1	TIL220Y yellow LED
LED2	TIL220G green LED
Q1, Q2	2N3904 or equiv.

##### Miscellaneous

pc board; hookup wire, etc.

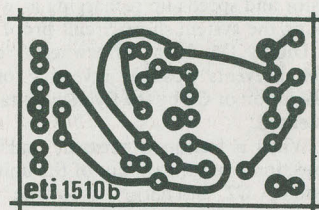

close to the pc board. This arrangement has proved entirely satisfactory.

#### Trying Out

The supply board can be tried out first. Hook up the input to an AC source of between 14 and 18 volts. On switch-on, LED1 should light, then extinguish about a second later. If not, check that it's connected the right way around. If that's OK, check that you're getting about 1½ times the AC input voltage across C1 (between 20 and 25 V DC or so should appear across it). If not, switch off and check the diodes D1 to D4 are all correctly oriented. Correct any faults as you go. When you've got LED1 to light on switch-on, then check that the output of IC1 is +5 V. Measure the voltage across C2. It should be equal, or nearly so, to the voltage on Q1. If LED1 won't go out, or there's less than one volt across C2, odds are you've got D6 the wrong way round.

Temporarily hook up the supply to a switch solenoid and see that it operates as expected.

You can check out the remoter(s) by temporarily connecting it to the +5 V

#### SUPPLY PARTS LIST

##### Resistors (all ½ W, 5%)

R1	2R7
R2	1k2

##### Capacitors

C1	1000u/25 V electro.
C2	3300u/25 V axial electro.
C3	10u/6 V tant.

##### Semiconductors

D1-D6	1N4001/2/3/4 etc.
LED1	TIL220R red LED or equiv.
IC1	7805
Q1	1A 50 V PNP, 2N4920 or equiv.

##### Miscellaneous

pc board; hookup wire, etc.

between switching operation of about half a second or so. Make sure you wire in LED1 the right way around.

The remoter board is quite straightforward. Best way to tackle this one is to mount the resistors and capacitors first. Then mount the two transistors making sure you get them the right way around. Finally, mount the two LEDs. Leave their leads long as the board can actually 'hang' from them. Alternatively, the LEDs may be mounted off the board and the board mounted somewhere conveniently nearby.

I secured my board to the underside of the model railway baseboard with staples from a staple gun holding down the wires to and from the units. The capacitive discharge supply was actually mounted at right angles to the baseboard. The remoters were held flat on the baseboard by stapling the wires fairly

from the supply board. One or other of the LEDs will light. Say, LED2 on the remoter lights. Connect the 'SOLENOID 1' input momentarily to the positive terminal of C2 on the supply, LED1 should light and LED2 should extinguish. If not, check transistor and LED orientations. If this works, then temporarily connect the 'SOLENOID 2' input to the positive terminal of C2 and the LEDs should swap over.

When wiring in the remoters, it may be necessary to add some extra supply bypassing to prevent random toggling of the LED indicators. Add a tantalum with a value between 4u7 and 10u. You'll need one of these per extra metre of cable length if the cable is a metre long or more.

#### Wiring Multiple Switches

Invariably, you will want to install mul-



# Model Railway Switch Controller

multiple sets of switches, some of which operate alone, some of which may need to operate together. There are two wiring options which exist and which may prove useful if you have not seen them before.

It often happens that two switches will always need to be switched together. These can be wired directly in parallel and operated by only two pushbuttons. The capacitive discharge supply described, should drive such an arrangement easily, without the need to increase the value of the discharge capacitor (C2). The 3300u capacitor specified would easily and reliably operate three parallel switches in my layout. If you need to drive more, then the capacitor's value can be increased (try 4700u). Conversely, you can decrease the capacitor's value if you find your solenoids are light ones and/or don't have parallel operated switches. Don't forget that if you increase the capacitor's value, you'll increase the charging time. If you decrease it, charging time speeds up.

Sometimes there is a need to have one set of switches 'slaved' from another, but have the first set operated independently also. This is readily achieved by the inclusion of some simple diode logic. A diode with its anode connected to one solenoid and its cathode connected to another, will leave the first turnout unaffected by the

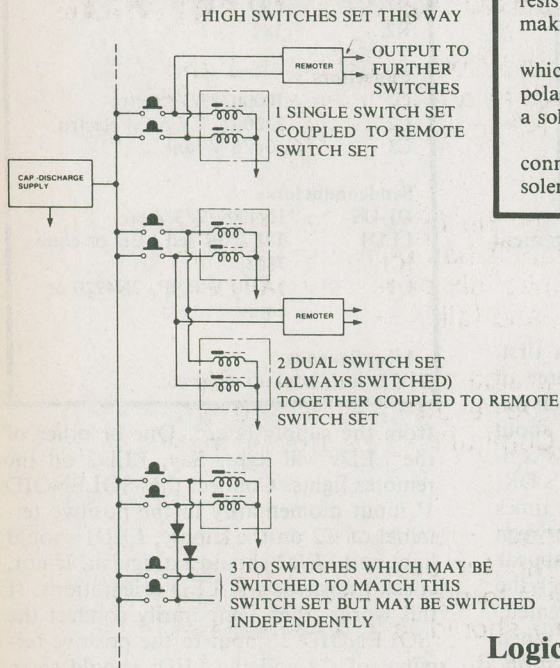


Fig. 2. Showing the three fundamental schemes for wiring switches.

second when switched, but will ensure that when the first is switched, the second also operates. This can be implemented with ordinary silicon rectifier diodes such as EM401s, 1N4001s, etc.

The various wiring arrangements are illustrated in Figure 2.

## HOW IT WORKS

There are two distinct parts to the project: the first is a capacitor discharge supply used to operate the switch solenoids, the second is a remote indicator unit.

The capacitor discharge supply unit charges a capacitor which is then discharged into the switch solenoid, which then operates the switches. This unit is capable of changing one switch every half second or so, and can power a larger number of switches together.

The remote indicator unit, or 'remoter', has the job of 'remembering' which way the switch set was last switched and indicates the direction with a pair of LEDs mounted as part of a signal map.

Consider the capacitor discharge unit. Diodes D1-D4 rectify the 14-18 volt AC input to provide a DC supply capacitor C1 smooths this for IC1, which regulates the voltage supply for the remoters. Up to fifteen remoters can be run off the output of IC1.

Transistor Q1 and surrounding components form a current source which charges C2 via D5. LED1 forms the voltage reference and doubles as an indicator which illuminates for the time when the capacitor is being recharged after use. Diode D5 prevents reverse biasing of the transistor when C2 is charged and C1 is below the peak input voltage value.

Using a current source for the charging element, removes the need for a large series resistor and speeds up recharging as well as making the system short-circuit proof.

Diode D6 is a "freewheel" diode which prevents possible reversing of the polarization of C2 by the flyback voltage of a solenoid.

When a button is pressed, making a connection from the output of the unit to a solenoid, C2 discharges into the coil,


changing the switch. After C2 is discharged, the only current flowing through the coil is the recharge current of about 375 mA. When the button isolates the solenoid, the current is free to charge C2, which takes about a quarter of a second. When C2 reaches the input voltage, Q1 saturates, LED1 goes out, and the unit is ready to operate again.

The 375 mA charging current is insufficient to harm a solenoid if it is left connected for any reason. As the controller can withstand indefinite shorting itself, the whole system is protected against abuse and failure of switches, etc.

Each remoter consists of an R/S type flip-flop formed by two transistors. Assume initially that Q1 is on, and Q2 off. The collector current of Q1, via R1, illuminates LED1, and the saturation collector voltage of Q1 ensures that Q2 remains off.

When a solenoid is activated by the discharge of the capacitor, a large voltage spike appears across it. Suppose that the voltage across the coil appears on R10. Capacitor C2 filters out brief induced spikes, so that no signal other than the correct one can affect the circuit. When the longer duration discharge pulses appear on R10, some current reaches the base of Q2, turning it on. This turns on LED2 via R2 and removes the base drive from Q1, and it turns off. Thus LED1 goes out, and the collector voltage on Q1 keeps Q2 turned on via R3. The reverse operation occurs when a pulse appears on R9.

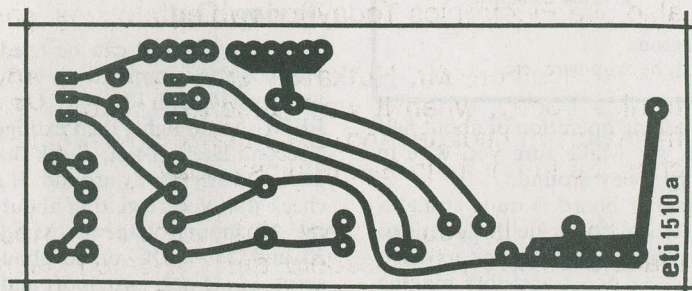Transistors are used rather than an IC as they have a higher output drive, are less intolerant of supply voltages, and ICs normally have more than one flip-flop in each package and you waste the rest.



## Logic Output


One advantage of remoters is that they can output the state of a switch set as logic levels for feeding into a digital system or computer. Astute readers will have noticed a certain provision in these model railway projects for a computer interface. The collectors of the transistors in each remoter circuit give a 'low' voltage when the respective side is that one carrying the traffic. For a 5 V supply, the levels are TTL. This is the main reason that the

remoters are run from a carefully regulated supply, apart from a desire to keep LED illumination level fairly constant. For those needing CMOS or other levels, the resistor values for 8 V and 12 V supplies are shown on the diagrams. (R1-2 and R3-4 will vary.)

Coupled with position sensing systems, the remoters can allow a simple anticrash logic system to be hardware implemented!

ETI



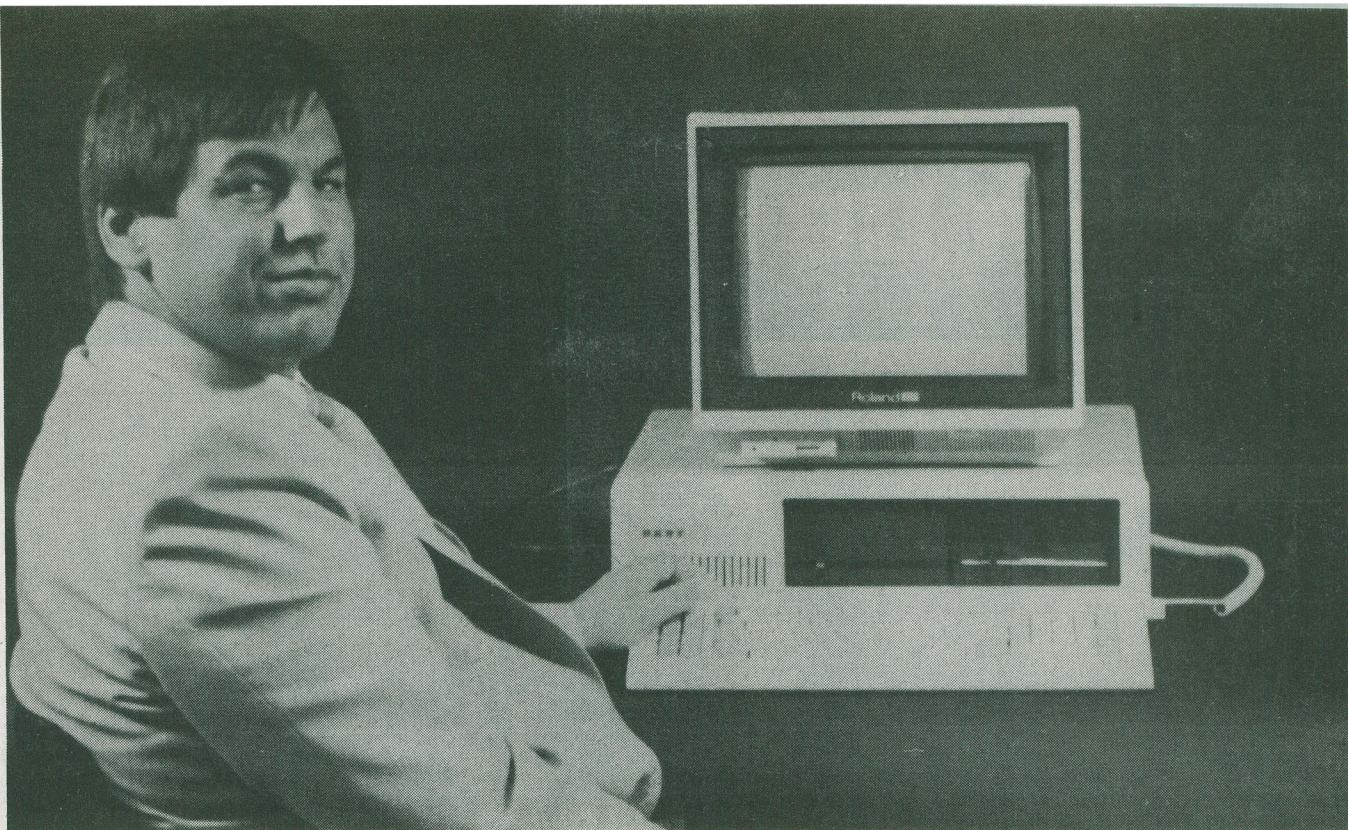

## **Electronics Today helped Eugen Hutka build his business.**

Eugen Hutka, President of Exceltronix Components and Computing Limited and its subsidiaries, learned early in his business career that advertising can deliver sales and profits. "The selection of the publication is, however, the key," says Mr. Hutka.

Electronics Today was the publication chosen as the base of Mr. Hutka's marketing plan when his company was launched and, "it has delivered from my first half page insertion, to now when I contract for thirty-six pages annually and also use Electronics Today for two catalogues, spring and fall."

In addition, Mr. Hutka tested Computing Now!, a sister publication to Electronics Today, when it was launched in April, 1983. The result in sales and profits was immediate and Exceltronix advertising in Computing Now! now matches the intensity in Electronics Today.

This tells you a great deal about all Moorshead Publications and their readers. Clearly, the readers are dedicated microcomputer users for both personal and business use who read advertising and use it to buy the products they need. Next month is the month you and your company should take advantage of this as Mr. Hutka has. It can help you build your business as well.

Let our Account Executive show you how Electronics Today can deliver for your company.

**Electronics  
Today** INTERNATIONAL **can help build your business as well.**


For Advertising Information Call (416) 423-3262

In Quebec (514) 735-5191


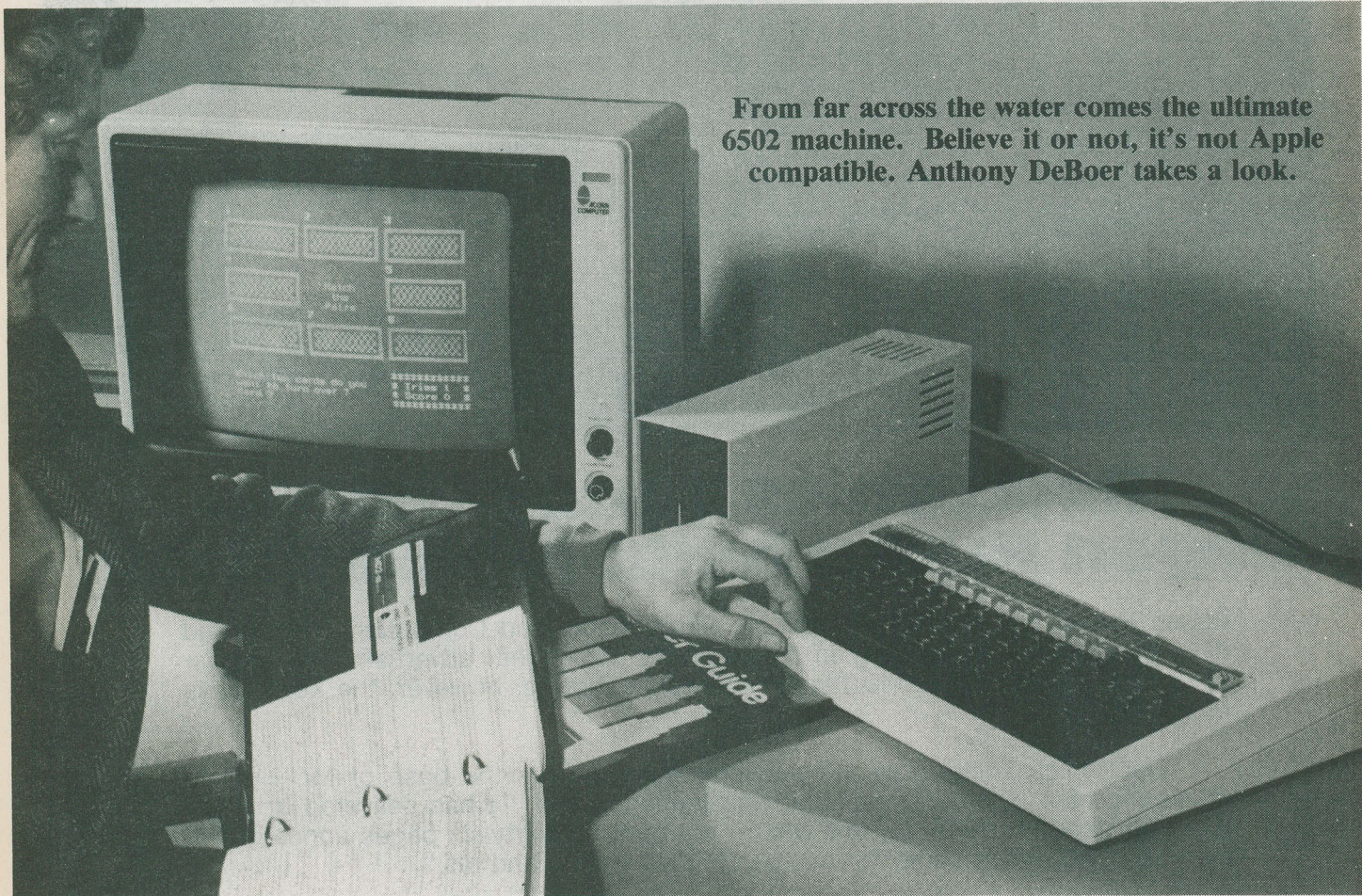
# Acorn BBC Review

From far across the water comes the ultimate 6502 machine. Believe it or not, it's not Apple compatible. Anthony DeBoer takes a look.



FROM THE foggy isles that brought us the Queen, the Beatles, and the ZX-81, not to mention the language most of us speak, comes the computer we're reviewing this month. Like the Multitech computer that came from a sunny island halfway around the other side of the world for the June review, it also uses a 6502, but unlike it, the Acorn BBC microcomputer bears no further resemblance to the Apple.

Like Ontario's Cemcorp Icon (a.k.a. the Bionic Beaver), the BBC micro was designed as an educational machine. The British Broadcasting Corporation (BBC) decided they wanted a machine to use as part of an educational television show they were doing, called "Making the Most of Your Micro". Meanwhile, Acorn Computers was working on a successor to their Atom microcomputer, a fairly popular machine in Britain that never

really took off in the Canadian market. Eventually, the two lines of effort became one, and the Acorn BBC micro was born. The computer has since been phenomenally successful in the British market, and is now available in Canada.

## Hardware

Internally, the BBC consists of a 2 MHz 6502 (twice the speed your ordinary garden variety 6502 runs at) addressing 32k of RAM and somewhat more than 32k of ROM. The upper 16k of ROM contains the "Machine Operating System" — all on one chip — which does all the I/O and selects one of up to four other such chips to occupy the other half of ROM space. BASIC occupies one such ROM, leaving the other sockets free for things like the disk operating system and the word processor ROM.

Externally, the machine consists mainly of a flat box with a keyboard on the front upper part, as pictured in the photos accompanying the article. The back side has, besides the usual power cord and switch, video connectors for your choice of monitor, modulated RF, or RGB signals, along with connectors for cassette, analog input, RS423 (which is similar to good old RS232), and Econet (a network system Acorn offers). The remaining connections are on the bottom of the machine, a rather unusual place for this kind of thing, although this apparently puts them along the front edge of the main printed circuit board. They include the connector for the disk drives, a user port, a printer port, a "1 MHz bus", and another one marked "tube", which we'll get to later.

The keyboard on the BBC, while having a feel to it that is quite unlike anything



but the earlier Atom keyboard, is still quite usable. It has real keys that go up and down properly, unlike the other major British micro, which shall at this point go unnamed. What more could you ask for?

The keyboard generates the full ASCII set, with the exception that the reversed quote (CHR\$(96)) comes out as a British pound sign. In addition, there are ten programmable function keys, giving 30 possible codes depending on the shift and control keys. There are also four arrow keys and both a regular caps lock key and a shift lock key.

The disk drives that came with the computer were double-sided 80-track machines, storing a reputed 400k per disk. Despite the high capacity, they gave no trouble at all. The cable connecting the drives to the computer was a fairly heavy beast, being ribbon cable in a copper mesh interference shield encased in heavy-duty vinyl.

### Looking at it

The BBC's graphics compare quite well with those of the much more expensive IBM compatibles, both in resolution and, more surprisingly, in drawing speed. For a humble 6502, it certainly moves like greased icecubes on a hot summer's day. In the highest resolution mode, there are 640 by 200 pixels (and/or 80 by 25 characters of text), although only monochrome is offered in this mode. That is, you can select one of the machine's sixteen basic colours for the background and another for the foreground. The first eight are the basic black, white, red, blue, green, yellow, cyan, and magenta, while the other eight are various flashing pairs of these colours. You can, for example, set things up so that the screen will flash back and forth between green letters on a red screen and magenta letters on a cyan screen. They flash back and forth *ad nauseum*, or at least until your eyes give up trying to watch them and fall from their sockets to the floor.


The most colourful mode offers all sixteen colours, but at only 160 by 200 resolution. A bit grainy, but it has possibilities. Since the sixteen display colours are not tied one-to-one to the sixteen actual colours, you can do some really neat pseudo-animation here. For example, you can declare all sixteen colours to be black, and then draw something. Nothing will appear until you selectively tell colours that they're visible. Since declaring a colour takes only a tiny fraction of the time it takes to actually draw something, you can make things appear, disappear, reappear, or seem to move very quickly.

One nice feature is that the BBC uses standard graphics coordinates. In all modes, the screen appears to your pro-

gram to be the same size. Coordinates go from 0,0 at the lower left-hand corner to 1279,799 at the upper right, regardless of how many pixels there actually are. Rounding off to the actual coordinates is done internally. This means that if you write a program to work in one graphics mode, you don't have to rewrite it to work in another one.

Another nice feature is that text and graphics can be mixed freely, since the character generator plots the characters directly on the graphics screen. Anyone who's ever tried labelling a graph on an Apple or similar machine will appreciate this.

At this point, maybe the reason why the BBC does graphics as quickly as a much more powerful 16-bit IBM should be explained. Even though an 8088 is faster than a 6502 ten times out of ten, the software being run can make a world of difference. IBM BASIC, to do solid coloured areas, uses a PAINT statement. You outline the area you want and then PAINT it. Flexible though this is, it requires masses of CPU power to examine each point, find your outline, and stay within the lines. The BBC, on the other hand, uses a much simpler triangle routine. You feed it three points, and the triangle thus defined gets coloured in.

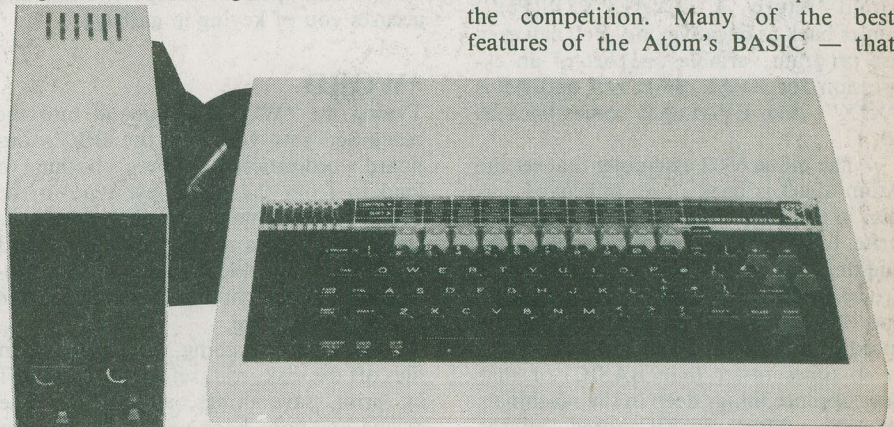

Two triangles give you a square or a rectangle, and a number of 'pie slices' will give you a circle.

There's only one complaint to be made about the BBC's colour graphics capability. You'd expect this machine, the epitome of all British hardware, to hold strongly to the Queen's English in its choice of BASIC keywords. Yet it has, for the purpose of setting text colours, a COLOR statement. Yes, you heard it right — the "U" is missing. Must be a Yankee on the design team.

### Bells and Whistles

Among the high-tech hardware the BBC mounts under its plastic exterior is a speech synthesizer. Yes, the machine can talk to you. Although it limits you to the 206 words in its ROM (unless you can

figure out the instructions on how to code your own words), you can be quite creative with what you have. Video games can say things like "INTRUDER ALERT", "GO LEFT", and "GET OFF THE MACHINE". The choice of words is rather interesting, including "QUEBEC" but not "ONTARIO". *Eh bien*, but you can still accomplish things here.

To the left of the keyboard is a little plastic plate which, when pried up, reveals a pair of sockets. Rumour has it that what goes here are extra ROM cartridges for the speech synthesizer, giving it a larger vocabulary.

More conventional sound synthesis is also included. Although the hardware itself looks very similar to the Commodore 64's sound chip, with three music channels and one effects channel, the BASIC interface is vastly different. On the 64, you use masses of utterly incomprehensible POKES to make sound. The BBC has a SOUND statement in BASIC to cause sound and an ENVELOPE statement to manipulate the sound envelope. This seems much more civilized.

### BASICally Better

The BBC's BASIC is another of the BBC's features that set it well apart from the competition. Many of the best features of the Atom's BASIC — that

wild, wonderful, non-Microsoft language — have been retained, but this new BASIC is much more like the standard versions of BASIC most North American programmers are used to. It's still non-Microsoft, but in many ways it's better.

The big feature is proper functions and procedures. No more of bad old BASIC, where you would write a routine to GOSUB, and then have to remember the line number (heaven help you if you renumber the program...) and be sure the variables you used in the subroutine didn't cause any problems with the rest of the program. Instead, the procedure gets a proper name, and the variables you use in it can be local, completely separate from the rest of the program. For example:



## Computer Review

```
10 MODE 0
20 PROCsquare(640,400,300)
30 FOR X = 100 TO 200
40 PROCsquare(600,400,X)
50 NEXT:END
100 DEF PROCsquare(X,Y,R)
110 MOVE X-R,Y-R
120 DRAW X-R,Y+R
130 DRAW X+R,Y+R
140 DRAW X+R,Y-R
150 DRAW X-R,Y-R
150 ENDPROC
```

As you can see, this makes programming a whole lot easier and more structured. The variable X in the main program is completely separate from the X in the procedure. Functions can be similarly defined, with multiple lines including IFs and so on.

This procedure capability, together with REPEAT ... UNTIL and IF ... THEN ... ELSE, makes BBC BASIC a structured language. You can write programs having a clear and logical flow of execution, with the subroutines properly isolated from each other and from the main program.

This BASIC has other neat tricks, too. There's an EVAL function that evaluates expressions. For example, if A\$ were equal to "2+2", then EVAL(A\$) would return 4. EVAL("COS(PI)") comes back as negative one. You can even use program variables as part of an expression for EVAL. If X is 7 and A\$ is "X\*X", then EVAL(A\$) comes back as 49.

The inline 6502 assembler that set the Atom apart is back in an improved version in the BBC. What this lets you do is write 6502 microprocessor code in the middle of your BASIC programs. Most programmers won't need this at all, but it does let you write code that runs at the speed of the machine (typically a hundred or so times faster than BASIC) or that does obscure things deep in the machine's internals. Most BASIC-based micros make it difficult to do machine code at all, or if they do allow it, they make it difficult to write and assemble the code, but the BBC makes 6502 code accessible and almost easy to use. It's still not for beginners, but it's a big step in the right direction.

The BBC employs a unique program statement editing system. When you use the arrow keys on the keyboard, a second cursor appears. You move this to the statement you want to edit, and then use the COPY key to copy characters from there. The copied characters, along with any others you might hit, appear back at the main cursor. The system, while a bit strange at first, actually does work quite well.

Another way in which this BASIC differs from almost every other BASIC on

the planet is in what it says when it doesn't understand what you're typing in. Most others say "Syntax error", which is obtruse and technical, but this one is much more direct and to the point. It says "Mistake". You can save face and blame the computer when you get a syntax error, but it's hard to do anything but admit you were wrong when the computer cheerfully accuses you of keying in garbage.

### \*WORD

Typing the \*WORD command into the computer gets you into the BBC's on-board word processor. There's nothing to load in from the disk; just type in the command and bang, the computer switches ROM chips and you're into word processing. Considering how long a program like WordStar can take to load, this is a real advantage.

Once you're going, you can pull in files off the disk, edit, reformat, type stuff in, print, save things, and so on. The escape key pops back and forth between command mode, where you can key in commands, and editing mode, which lets you type in and edit text. The function keys, together with shift and control, are used to do things like move blocks, reformat, etc. It is a very good word processor, easily adapted to by anyone used to WordStar or a similar system, or easily learned.

### CP/M

Part of the BBC's design is that it can mount a second microprocessor via a connector on the bottom of the computer called "the tube". In this configuration, the second processor runs whatever language you're using while the 6502 in the computer handles I/O.

The first choice offered for a second processor is a second 6502 with 64k of

RAM, which makes the computer faster and capable of handling more data, especially since you no longer need to share the computer's memory with the screen graphics area.


Second is a Z-80, again with 64k, with which one can run CP/M on one's machine. Acorn claims that a BBC running CP/M is better than a more conventional CP/M machine, since I/O is all handled by the 6502 in the main machine, leaving more time and memory space to the Z-80.

Third is a 16-bit National Semiconductor 16032 chip with up to 16 megabytes of RAM. This might not be enough to knock Cray out of business, but it is probably more than enough computer for any expansion needs.
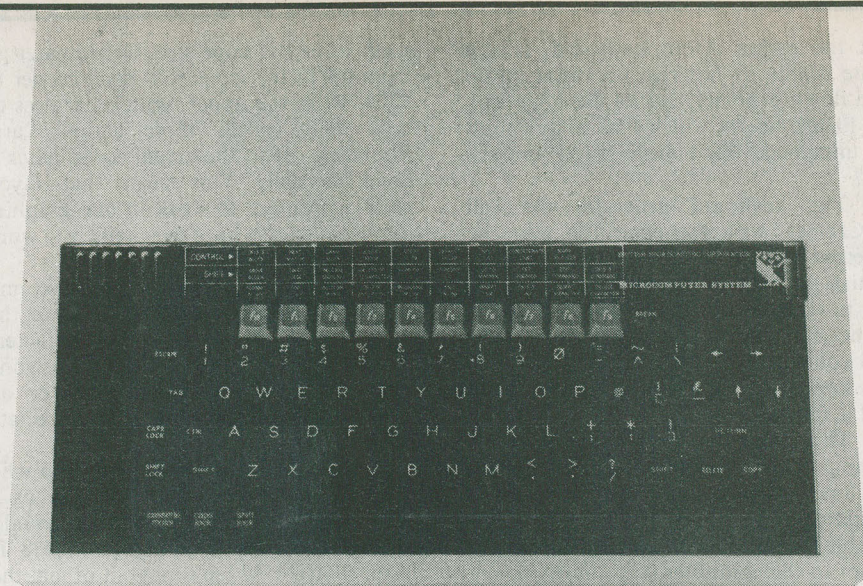
### Software

The introductory disk that comes with the computer includes, besides the disk formatting program and a verify routine, a series of demo programs and games. There's one that draws a desert island and then animates the waves in the ocean around it. There's also a sketch program that lets you make simple drawings. And then there's Mars Lander. You can try to land your lander gently, as the rules call for, or you can play by the Computing Now! rules, which involve attaining the greatest possible velocity prior to impact. The record so far is well over a kilometre per second.

The BBC started out as an educational computer, however, and an educational computer needs educational software. Unto this end, Acorn markets a line of such software. The titles we got to review with the machine included Gas Diffusion, Gas Laws, Speed, Density, Gravitational Fields, and Venn Diagrams. Each comes in a plastic case, with a book and a disk inside.





# Learn robotics and industrial control as you build this robot

New NRI home training prepares you for a rewarding career in America's newest high-technology field.

The wave of the future is here. Already, advanced robotic systems are producing everything from precision electronic circuits to automobiles and giant locomotives. By 1990, over 100,000 "smart" robots will be in use.

## Over 25,000 New Jobs

Keeping this robot army running calls for well-trained technicians. . . people who understand advanced systems and controls. By the end of the decade, conservative estimates call for more than 25,000 new technical jobs. These are the kind of careers that pay \$25,000 to \$35,000 a year right now. And as demand continues to grow, salaries have no place to go but up!

## Build Your Own Robot As You Train at Home

Now, you can train for an exciting, rewarding career in robotics and industrial control right at home in your spare time. NRI, with 70 years of experience in technology training, offers a new world of opportunity in one of the most fascinating growth fields since the computer.


You need no experience, no special education. NRI starts you at the beginning, takes you in easy-to-follow, bite-size lessons from basic electronics right on through key subjects like instrumentation, digital and computer controls, servomotors and feedback systems, fluidics, lasers, and optoelectronics. And it's all reinforced with practical, hands-on experience to give you a priceless confidence as you build a programmable, mobile robot.

## Program Arm and Body Movement, Even Speech

Designed especially for training, your robot duplicates all the key elements of industrial robotics. You learn to operate, program, service, and troubleshoot using the same techniques you'll use in the field. It's on-the-job training at home!

Building this exciting robot will take you beyond the state of the art into the next generation of industrial robotics.

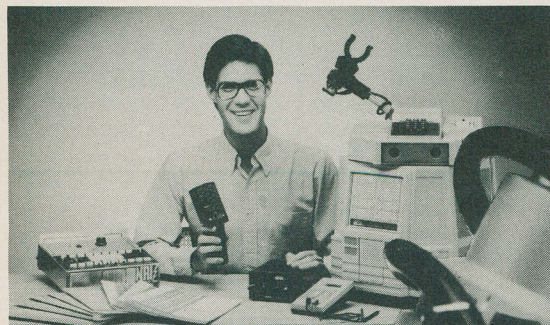You'll learn how your completely self-powered robot interacts



You get and keep Hero 1 robot with gripper arm and speech synthesizer, NRI Discovery Lab for electronic experimentation, professional multimeter with 3 1/2-digit LCD readout, 51 fast-track training lessons.

with its environment to sense light, sound, and motion.

You program it to travel over a set course, avoid obstacles using its sonar ranging capability. Program in complex arm and body movements using its special teaching pendant. Build a wireless remote control device demonstrating independent robot control in hazardous environments. You'll even learn to synthesize speech using the top-mounted hexadecimal keyboard.

## Training to Build a Career On

NRI training uniquely incorporates hands-on building experience to reinforce your learning on a real-world basis. You get professional instruments, including a digital multimeter you'll use in experiments and demonstrations, use later in your work. And you get the exclusive NRI Discovery Lab®, where you examine and prove out theory from basic electrical concepts to the most advanced solid-state digital electronics and microprocessor technology. Devised by an experienced team of engineers and educators, your experiments, demonstrations, and equipment are carefully integrated with 51 clear and concise lessons to give you complete confidence as you progress. Step-by-step, NRI takes you from the beginning, through today, and into an amazing tomorrow.

## Send for Free Catalog Now

Send for NRI's big free catalog describing Robotics and Industrial Control plus over a dozen other high-technology courses. You'll see all the equipment you get in detail, get complete descriptions of every lesson, find out more about career opportunities for trained technicians. There's no cost or obligation, so send today. Your action today could mean your future tomorrow.



## NRI SCHOOLS

McGraw-Hill Continuing  
Education Center  
330 Progress Avenue  
Scarborough, Ontario M1P 2Z5  
or telephone 416-293-8787

**WE'LL GIVE YOU TOMORROW.**




## Computer Review

There is quite a difference between the elementary and the secondary level software. Taking the Density package as an example, it uses bright colours and large letters to attract the children's attention. One gets to play a game against the computer involving the guessing of densities for a number of common substances. At the end, after telling you who got the best score so far, it says to "Tell your teacher you have finished".

The highschool level software is much more highbrow, being command driven rather than prompted along, allowing you to set up problems and watch them get solved, graph the results, and so on.

For some reason only the elementary level programs were protected, having a character embedded in the first filename on the disk that disables the video driver, preventing you from seeing what was on the disk. Break and Escape didn't work either. Is this supposed to say something about the state of the educational software market and the illegal copying therein? Are highschool teachers more honest than elementary school teachers? Maybe it's just that the different packages were written by different people, some of whom were more trusting than others.

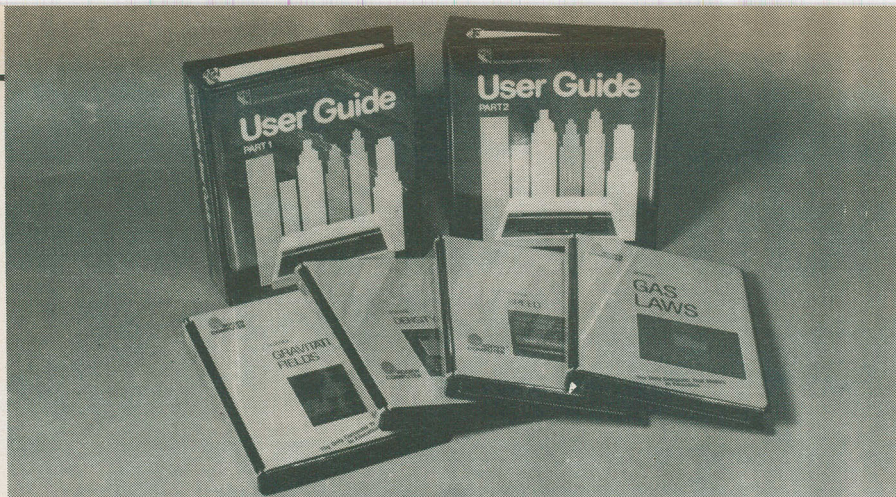

### Conclusions

The BBC is a very impressive computer, having excellent graphics and BASIC, along with all the features you could ask for. Over in Britain, it's allegedly selling at four hundred pounds for the basic machine, although once it gets to Canada the price finds its way into the vicinity of fourteen hundred dollars. This may be a bit steep, but computers generally tend to come down in price after their introduction. Even so, it is easily the most impressive computer to come across this reviewer's desk to date. Highly recommended.

### Quick Reference

<b>Mfg:</b>	Acorn
<b>CPU:</b>	6502
<b>RAM:</b>	32k
<b>Screen:</b>	80 x 25
<b>Graphics:</b>	640 x 200
<b>Colours:</b>	8
<b>Sound:</b>	Yes
<b>Video:</b>	RGB
<b>Price:</b>	\$1495
	\$1495 for dual drives.

Acorn Computers Corp., 14 Woodborough Rd., Guelph, Ont. (519) 837-2022.  
ETI

## AUDIOVISION

### COMPUTING/ELECTRONICS

**MAIL ORDER:** Certified cheque, money order, VISA or Master Card plus 5% delivery charge. Ontario residents add 7% P.S.T. We send Canada Post, or Purolator freight collect.

**6502 COMPUTER SYSTEMS**

**PACKAGE 1: \$949.00**

- 64K Computer with Multi-Function Keyboard, Upper/Lower Case and Numeric Keypad
- Disk Drive (Shugart)
- Controller Card
- Zenith 12" Green or Amber Monitor

**PACKAGE 2: \$1,550.00**

- All items in package 1.
- Z80 Card.
- 80 Column Card
- Gemini 10X Printer
- Parallel Printer Card with cable

**PACKAGE 3: \$1,700.00**

- Same as package 2 but with IBM look-alike case and Multi-Function detachable Keyboard

**PACKAGE 4: \$2,100.00**

- Same as package 3 but with IBM look-alike case and Multi-Function detachable Keyboard

(We send Computer Systems via Purolator Freight Collect)

### ACCESSORIES

1. 128K Card ..... \$195.00	8. Delux Self Centered Joystick ..... \$45.00
2. 300 Baud Modem ..... \$155.00	9. Disk Drive (Quentin) ..... \$299.00
3. Talk Card ..... \$40.00	10. Disk Drive (Shugart) ..... \$259.00
4. Musician Card ..... \$155.00	11. Light Pen System ..... \$225.00
5. RS232 Card ..... \$70.00	12. Graphic Tablet ..... \$109.00
6. RF Modulator ..... \$15.00	13. Nashua Diskette, SS/DD ..... \$25.00
7. Joystick (Self-Centered) ..... \$20.00	

### ELECTRONIC KITS

#### DIGITAL DESIGNER FOR COMPUTER TECHNOLOGY

Supplies all necessary signals, voltages and read-outs to design or construct any digital circuit.

**Kit \$54.95**

#### REGULATED POWER SUPPLY KITS

(Transformer not included)

Variable Voltage:  
0-15V, 5A. **Kit \$14.50**  
0-35V, 3A. **Kit \$14.50**

Variable Voltage & Current  
0-50V, 0.5-3A. **Kit \$21.50**

#### SUPER FM WIRELESS MIKE

Complete unit fits into a plastic cigarette case. Picks up and transmits sound up to 300 ft. through a FM Radio

**Kit \$9.50**

#### SOUND/LIGHT ACTIVATED SWITCH

Selectable Sound/Light Control. Works as an On/Off switch activated by intensity of light or sound. Can control up to 200 watts.

**Kit \$11.50**

#### ELECTRONIC CLOCK

Green Led Display with dual tone alarm. Runs on 12VDC (0.2A) or 18VAC.

**Kit \$19.50**

### COLOR ORGAN/LIGHT CHASER

Features variable speed 3 sequence light chaser, or direct hook up to speaker as color organ for Control up to 1500 watt lights.

**Kit \$79.50**

### TELEPHONE CONVERSATION RECORDING UNIT

Easy hook up to Telephone and Recorder for automatic recording of telephone conversation. No battery required.

**Not A Kit \$14.50**

### LOGIC PROBE

For Quick servicing and checking of integrated logic system. Features unique Multi-Lamp readouts, pulse detection, and input overload protection. Max. input Freq. display: 30 MHz. Min. detachable pulse width: 20 ns.

**\$29.50**

### LOGIC PULSER

Allows injection of pulses into circuit nodes without cutting traces, removing ICs; and monitoring circuit response with a logic probe.

**\$33.50**

### DESOLDERING TOOL

Makes parts removal from PC Board a Breeze.

**\$14.50**

### I.C. EXTRACTION TOOL

Extracts all LSI, MSI and SSI devices from 8 to 40 pins.

**\$2.50**

1984 Catalogue ..... **\$1.00**

### MINI-DRILL WITH STAND

Operates on 4 penlite batteries or a AC adaptor (6-12V, 2A)

Speed 2200 RPM  
Ideal for Drilling and Grinding P.C. Boards, Aluminum and Copper Sheets.

**\$45.00**

### POWER TRANSFORMERS

110VCT, 0.5A .....	\$13.50
64 VCT, 0.5A .....	\$8.70
30 VCT, 2A .....	\$9.50
18VCT, 3A .....	\$12.50

### TRANSISTORS

MOSFET 2SK134 .....	\$12.95
MOSFET 2SJ49 .....	\$12.95
MJ15003 .....	\$6.50
MJ15004 .....	\$6.50
2N3055 .....	\$1.45
MJ2955 .....	\$1.45

### ELECTROLYTIC CAPACITORS

10,000 MFD 50V .....	\$ 8.50
10,000 MFD 80V .....	\$15.00

### BOOKS

Apple II & Ie User's Guide .....	\$17.50
Apple II Circuit Description .....	\$27.00
DOS Manual .....	\$15.00

### RACK MOUNT CABINETS

Black Anodized Aluminum Front Panel with Steel Box, Hardware, Ventilation Slots and Instruction.

Panel Size (inch)	Box size (inch)	Price
19 x 7	17 x 6.5 x 12	\$43.50
19 x 6	17 x 5.5 x 12	\$42.50
19 x 5	17 x 4.5 x 12	\$39.50
19 x 4	17 x 3.5 x 12	\$38.50
19 x 3	17 x 2.5 x 10	\$35.50
19 x 2.5	17 x 2 x 10	\$32.50
17 x 6	15.5 x 5.5 x 9	\$37.50
17 x 4	15.5 x 3.5 x 9	\$32.50
17 x 2	15.5 x 1.5 x 9	\$30.50
12 x 6	11.5 x 5.5 x 7	\$26.50
12 x 4	11.5 x 3.5 x 7	\$22.50
12 x 2	11.5 x 1.75 x 7	\$21.50


White Audiowords for Cabinets ..... \$2.50

**EASTERN CANADA**  
578 MARLEE AVE.  
TORONTO, ONT., M6B 3J5  
TEL (416) 781-3263

**WESTERN CANADA**  
P.O. BOX AMF23581  
VANCOUVER, B.C.  
TEL (604) 271-7539



# Electronics in Action

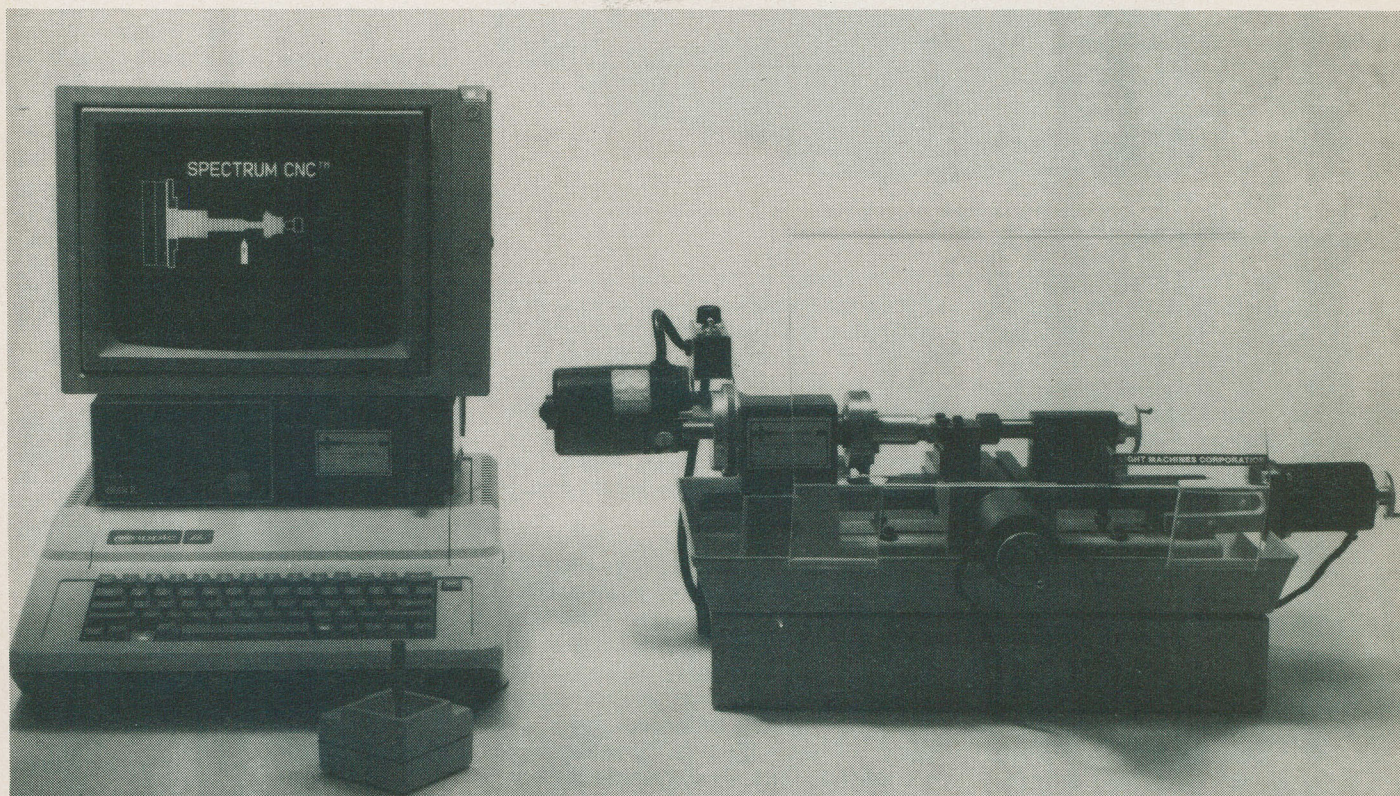

**In a new series, Roger Allan looks at some of the many applications of electronic technology in home and industry.**

## **The Cottage Lathe**

HISTORICALLY, MACHINE shop systems have been enormously expensive due to the demand for high performance and reliability. This has tended to preclude their utilization by schools for training purposes and further, prevented their use by small craftsmen, such as those involved in the cottage industries of wood and metal working. They cannot expand due to the high set-up costs involved. The fundamental major portion of these machines' cost is in the lathe's mechanical precision requirements.

To help overcome this problem, *Light Machines Corporation* now markets the *spectraLIGHT CNC Lathe* which uses machine intelligence to replace the expense of mechanical precision.

Originally designed as an industrial grade machine for short-run small-part fabrication, this lathe has the same

capabilities as machines costing 20 times as much, retailing for about the price of an Apple. It can create any surface of revolution in wood, plastic or metal up to 8 inches in length and up to 3½ inches in diameter.

The lathe uses an Apple II+ or IIe computer (or clone) as its programmable controller. In conventional numerical-control code, this device duplicates most of the same operations performed on any full sized CNC lathe. Using BASIC, the user may add special functions such as polynomial-fit curve cuts, mouse or graphic table programming; the software and operator's manual guides the user through each step. Graphic part verification allows the user to view animations of part programs on the screen before any material is cut.

This device may also be operated with the manual handwheels, directly through the keyboard, or with an optional joystick. The system offers a basic resolution of .0025 inches in both axes, with positioning repeatability to plus or minus .0005 inches. Backlash can be removed by software and adjusted by keyboard com-

mand. A single floppy disk can store several thousand NC blocks, thereby permitting cottage craftsmen to produce small numbers drawn from a very wide assortment of items without necessitating any reprogramming.

## **Electronic Tape Measure**

Determining range by means of ultrasonic echo ranging is a relatively simple process. A short burst of ultrasonic energy is generated electronically, amplified and transmitted by a transducer. The signal travels through the medium (in this case air), reflects from the target object and returns to the transducer. The signal is received, amplified and processed by the system electronics. The time for the round trip can then be determined, and knowing the correct speed of sound in air, the distance to the object may be calculated.

A simple ultrasonic echo ranging system was initially developed by Polaroid for use in their Sonar Auto Focus Camera. It is composed of only two parts: the transducer and the electronics module. The transducer is an electrostatic type which is used to transmit the signal and





### The Electronic Tape Measure

receive the echo. The module contains all of the circuitry needed to generate the transmit signal, drive the transducer, receive the echo and process the information received by the transducer. The distance from the transducer to the target can then be computed with additional circuitry, knowing the speed of sound in air and the time interval between the transmit signal and the received echo as provided by the ranging module. The Polaroid system operates over a distance range of 0.26 to 10.7 meters (0.9 to 35 feet), increasing the receiver amplifier gain and decreasing the bandwidth with time to compensate for signal losses over the distance range. Then, to minimize the system's susceptibility to noise pick-up, a signal integration scheme is employed before the system locks onto an echo. Once the threshold level of the integrator is reached, a signal is generated to indicate a received echo. The logic level outputs for the transmit signal and received echo can be used to perform control functions or calculate distance to the object with a minimum of additional circuitry.

A number of companies have taken Polaroid's development and applied it to uses other than home photography. One of them is the Exergen Corporation which sells a pocket-sized ultrasonic tape measure known as the *Rangescanner*. Accurate to within 1% over the thirty-five foot range, the device is the smallest instrument available offering instant dimensioning.

Looking at it like a packet of cigarettes, the Rangescanner offers a 3-digit LED display showing the distance in either feet or operated by a measurement selector switch (the third digit in the LED display is the decimal). It has the added feature of a mode selector: either "lock" or "scan". In the lock mode, the range of the object being measure is recorded on the LED display. In the scan mode, the device measures the distance 3 times a second, displaying the distance each time. This mode is useful in locating positions; eg., the user presses the dead-man operating switch, and walks backwards or forwards until the correct measurement shows.

Originally designed for real estate people to measure rooms, this device is now used by contractors, builders, engineers and architects, allowing them to walk through take-offs and surveys.

### PC Board Tester

The Metrifast company recently introduced a low cost electronic test instrument called a *Thermoprobe* which is designed to quickly identify dead components on printed circuit boards without direct contact and thereby without using a voltmeter.


Essentially, the solid-state device consists of a thermistor probe connected to a modified wheatstone bridge circuit. It is designed to measure minute temperature changes of 1/25 of a degree Fahrenheit (1/45 °C). Since dead resistors, transformers, diodes or ICs do not emit heat, they can be quickly identified by the unit's built-in meter as the thermistor probe is moved in close proximity to them.

The six-inch long unit is operated by removing the protective front cap and pointing the thermistor probe with 1/16 of an inch of the PC board surface. A nulling wheel at the side of the unit is then turned clockwise until the meter indicator reads "normal". Then, as the thermistor probe is moved slowly at approximately 1/16 of an inch above the components on the PC board, the meter indicator will move to the right or "warm" area of the dial each time the unit is passed over an operational active component. The dial indicator will move back to the nulled position if the active component being tested is dead and therefore not emitting any heat. Utilizing a 9-volt battery, the unit is about the size of a large packet of cigarettes and is designed for field service applications in computers, electronic instrumentation, video and hi-fi repair as well as the home experimentalist.
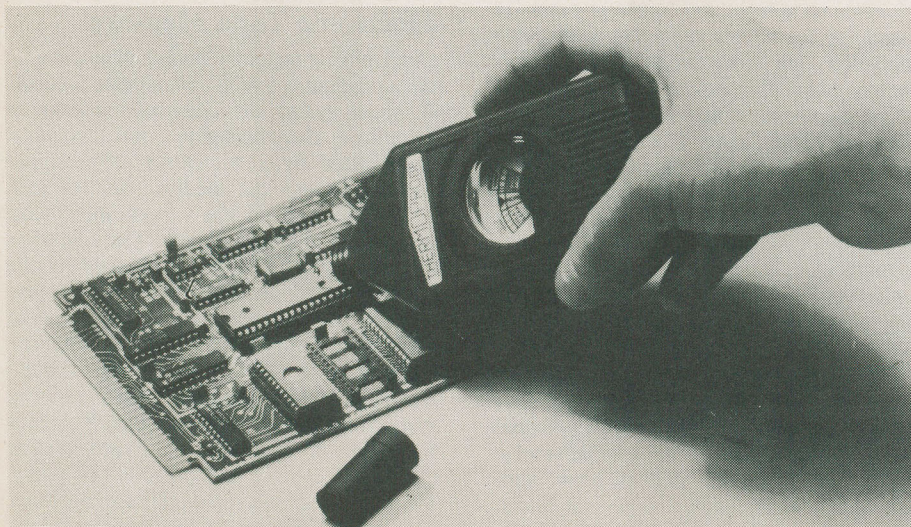
### Seiko TV Watch

The RT10A TV watch marketed by Seiko involves a new advance in video display pictography.

In the Liquid Crystal Video Display (LVD) developed by Seiko and utilized in the watch TV, two types of liquid crystal are enclosed between a sheet of glass and a transistorized silicon base to create 31,920 screen dots similar to the ink dots that make a newspaper photograph. As electrical pressure is applied in the silicon base, the liquid crystals 'stand' or 'lie down', reflecting or absorbing light in accordance with their position, to produce light and dark (blue) dots, thereby making up a picture. Because the liquid crystals reflect light to create the picture, the LVD screen operates best in good light, unlike the traditional cathode ray picture tube. Further, the LVD does not require high



The PC Board Tester



# MODULAR PROBES FOR SALE

For All Oscilloscopes  
To 300MHz  
X1 to X100  
Attenuation

## INSTANT REPAIR

Probe tip, Head, BNC and Cable  
all screw into place  
easily and quickly.

Pictured  
Accessories  
Included



980 Alness St. Unit 7,  
Downsview, Ontario.  
M3J 2S2  
(416) 661-5585  
TELEX 065-28169

Your Probe Specialists

### COMPARE PRICE — COMPARE PERFORMANCE

Model	Attenuation	Bandwidth	Price
M12SW	X1-X10 Switchable	X1-10MHz X10-250MHz	\$56.80
M12X10	X10	250MHz	50.10
M12X10AP	X10 with Readout	250MHz	67.70
M15X100	X100	250MHz	56.80
M15X10HF	X10	300MHz	80.30
M12X1	X1	30MHz	42.40

Coline Canadian Sales & Stocking Source

Circle No. 13 on Reader Service Card


# K.E.M.

## COMPUTER AND ELECTRONICS
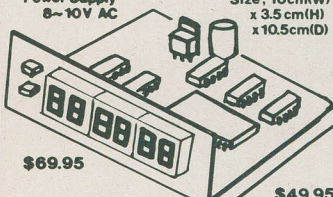
### KEM ORIGINAL ELECTRONICS KITS

**FM WIRELESS MIKE** ..... \$18.95  
76~108MHz ADJ. 3V Battery Operation  
Range Max 80m. PCB Size: 5 x 10cm

**DIGITAL FREQ COUNTER**  
6 Digit LED Display. 10Hz~10MHz  
Input 100mV rms. Range 1MHz or 10MHz  
Power Supply 8~10V AC  
Size: 10cm(W) x 3.5cm(H) x 10.5cm(D)



**MINI AUDIO AMP 5W** ..... \$8.95  
Gain 50dB. Distortion 0.3% Typical  
Input 20Kohm. PCB Size 5cm x 5.5cm

**PRE-SCALER FOR COUNTER** .... 19.95  
200MHz Max. 1+100 Output.  
Input 30mVrms at 100MHz  
Single Power 5Vdc. Size 3.5cm x 5.5cm

**CAPACITANCE METER** ..... 42.95  
3 Digit LED Display. 10pF~999uF.  
6 Step Measuring Ranges. 2% Acc.  
Single Power 6Vdc.  
Size 8cm(W) x 3.5cm(H) x 8cm(D)  
(Same structure as Freq Counter)

Full documents including  
circuit diagram for every  
item ..... \$4.00  
(incl. postage)

### LCD DIGITAL PANEL METER

±199.9mV FS. Power Supply 5Vdc, 3.5mA.  
Plastic Case (Standard DIN Size Mounting)  
9.6cm(W) x 4.8cm(H) x 1.5cm(D)  
Voltage divider, Ohm or Temp Converter (Option)


### SUPER PROGRAMMER (Peripheral for APPLE)

Program 2716, 2732, 2532, 2732A, 2764 & 2564.  
Metal case mounted ..... \$148.00

### STEPPING MOTOR DRIVER KIT -- \$65.00

Controlled by computer or manual.  
With Program for APPLE.  
PCB Size: 11cm x 9cm.

Motor (Option).

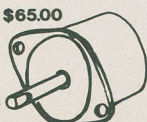

## KAIENTAI ELECTRONICS MERCHANTS LTD

2111 KINGSWAY, VANCOUVER, B.C. V5N 2T4  
MAIL TO: P.O. BOX 69126 STATION 'K'  
VANCOUVER, B.C., CANADA V5K4W4  
PHONE: (604) 435-9697

Circle No. 9 on Reader Service Card

# COMPUTRONIKS

\* A credible place for the intelligent and thrifty.

\* A single stop for Electronic parts, computer accessories, books and software.

\* A reliable store for fast service of Commodore™ & Apple™ computers.

\* We sell satisfaction!

### ELECTRONIC COMPONENTS

Solder Tail IC Sockets ..... 1.3¢/pin  
(several thousand in stock)

4116 200ns ..... \$1.75  
4164 ..... \$8.95  
2016 ..... \$8.75  
MC3242 (128K board) ..... \$14.95  
MC3470 ..... \$8.50  
DAC08 (SAM card) ..... \$3.99  
TTL's, CMOS...low low prices ..... \$CALL  
(complete range)

Special price on Connectors!!!

### COMPUTER ACCESSORIES

Brother HR-15 ..... \$695.00  
Mannesmann Tally (Spirit 80) ..... \$425.00  
Epson (Complete range) ..... \$CALL  
7 Amp Power Supply ..... \$99.00  
IBMTM Disk Drive DSDD  
(Matsushita) ..... \$245.00  
Cardco Printer I/F Graphics  
(for VIC20/COMM 64) ..... \$119.00

### DISKETTES

Nashua SSDD plastic box ..... \$27.95/10  
Maxell SSDD ..... \$35.50/10

Dysan SSDD ..... \$35.95/10  
Datatype SSDD ..... \$34.50/10  
Xidex SSDD blank label ..... \$25.95/10  
(Unlimited warranty from Computroniks)

### UNITRON 2200E

COMPUTER ..... \$775.00

• Apple™ & CP/M™ compatible •  
Dual Microprocessor Z80/6502 • Dual  
Disc Interface • 64K • Multifunction  
IBM style detachable keyboard • one  
year warranty, labour and parts

### PERIPHERAL CARDS

#### Low Low Prices

Controller Card ..... \$49.00  
Z-80 ..... \$63.00  
Auto dial, auto answer MODEM \$159.00  
(Terminal S/W, Upload/Download  
S/W included)  
32K Buffered Graphics  
Printer I/F ..... \$139.00  
Others (Guaranteed low prices) ..... \$CALL

Bare Boards, Joysticks, Computer Covers, Printer Ribbons, Computer  
Paper and other accessories available at low prices.

Dealer Inquiries invited

TO ORDER: Send money order, certified cheque, personal cheques, VISA or  
Master Card (including number, expiry date and signature). Add 5% for shipping  
and handling (Min. \$3.00 per order). Ont. residents add 7% P.S.T.

## COMPUTRONIKS

35 Queen St. E., Brampton, Ont. L6W 2A7  
(416) 453-1166

Circle No. 33 on Reader Service Card.



## Electronics in Action

voltages. In fact, the television screen in the Seiko watch (measuring 30 mm (1.2 in.) diagonally) is powered by two AA batteries in the receiver unit (possessing about 5 hours worth of continuous viewing power), or may be connected to an electrical outlet with an AC adapter.

The receiver for the watch, for which a headphone cord acts as an antenna, will pick up UHF (14-83 ch.), VHF (2-13 ch) or FM (88-108 MHz) as effectively as most portable televisions or TV sets using 'rabbit ear' antennae. Reception is dependent on broadcast electrical waves and will therefore be poor where the signal is weak or blocked by buildings or mountains. The watch has insufficient sensitivity to receive signals underground, even in the basement of a building. However, if the FM signal is weak or distorted by high levels of static interference, switching from the stereo to the mono mode of reception improves the sound quality.

The TV receiver for the watch is designed to operate in Canada and the U.S., and will not decipher signals in overseas countries using different broadcasting systems and frequency ranges. The headphone band size is adjustable by rotating the speakers on the headset.



Seiko's TV watch.

However, as the cord also serves as an antenna, the user has to keep the cord as straight as possible.

In addition to the video and FM reception capability, this watch also tells the time in the customary fashion, but has the added feature of being able to tell it either in 12 (a.m./p.m.) or 24 hour display modes, accurate to plus or minus 10 seconds a month. The day/date calendar adjusts automatically for odd and even months with the exception of February in leap years. Its chronograph has a split

time capability in hours, minutes and seconds with an accuracy of up to 1/100 second over 12 hours. And finally, an alarm may be set to ring for hourly or daily time signals. **ETI**

**Addresses:** Light Machines Corporation, 649 East Industrial Drive, Manchester, New Hampshire, U.S.A. 03103 (603) 625-8600 • Exergen Corp., 307 West Central St., Natick, Mass. U.S.A. 01760 (617) 875-2387 • Metrofast Co., 51 South Denton, New Hyde Park, New York, 11040 (516)328-3333 • Seiko, 285 Yorkland Blvd., Willowdale, Ont. M2J 1S5 (416)496-2221 •

### Complete System +



for  
**\$875.00**

- Fully Apple™// compatible • 48K memory • Disk drive • Disk controller card • Upper/lower case • Hi-res Amber monitor • Color graphics • 90 days warranty

### I.B.M. Compatible



**ECS1**  
**\$1895.00**

- 8088 processor • optional Intel 8087 numeric coprocessor • 64K memory exp. to 256K on board • double sided double density disk drive • detachable keyboard • colour-graphic board • support IBM® software • 90 day warranty

### Complete System Model 2200



for  
**\$999.00**

- Fully Apple // compatible • dual processor 6502 and Z80 • 64K RAM • 24K ROM • 80 or 40 column soft switch • controller card • disk drive • Hi-res amber monitor • colour graphics • detachable keyboard • 90 days warranty

### ECS2 Systems



**\$1195.00**

- Fully Apple // compatible • dual processor 6502 and Z80 • 64K RAM • 24K ROM • controller card • disk drive • Hi-res 111t amber monitor • color graphics • detachable keyboard with special function • 90 days warranty

## ELECTRONIC CONTROL SYSTEMS


1890 Meyerside Drive, Mississauga, Ontario L5T 1B4  
(416)673-1302 Hours — Mon. to Fri. 10-7, Sat. 10-2

## THE BRUNELLE Commander SERIES

Model 5050 is a compact, lightweight 3-1/2 digit multimeter suited for all types of lab or bench operation.

*Dependability you can count on. Meets toughest demands!*

**Model  
5050  
Digital  
Multimeter**

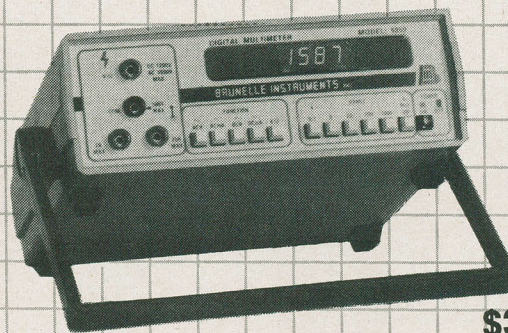

**\$389**

### Featuring

- 5 functions (AC/DC voltage, AC/DC current ranges up to 20 amps and resistance)
- 0.5" large 3-1/2" digit reg LED display
- High resolution 0.1MW, 0.1R, 0.1UA

- High accuracy 0.1%
- High current range 20A
- High voltage range 1,200V
- Automatic Zero Circuitry
- All range with protection circuit
- 2 year warranty

BRUNELLE



INSTRUMENTS

### CANADA

BRUNELLE INSTRUMENTS INC.  
826 Belvedere St  
Sherbrooke, Quebec J1H 4B8  
Tel.: 1-819-569-1408  
Télex: 05-836266  
Mail orders accepted. Send certified cheque or money order. Add \$3.00 for shipping. Quebec residents add 9% P.S.T.

### Available from:

- Active Components Stores across Canada
- Fathom Atlantic, Dartmouth, Nova Scotia

Circle No. 26 on Reader Service Card

Circle No. 5 on Reader Service Card




# Software Now!

FIRST  
ISSUE  
OCTOBER 1984

Canada's Microcomputing Software Magazine

\$2.95

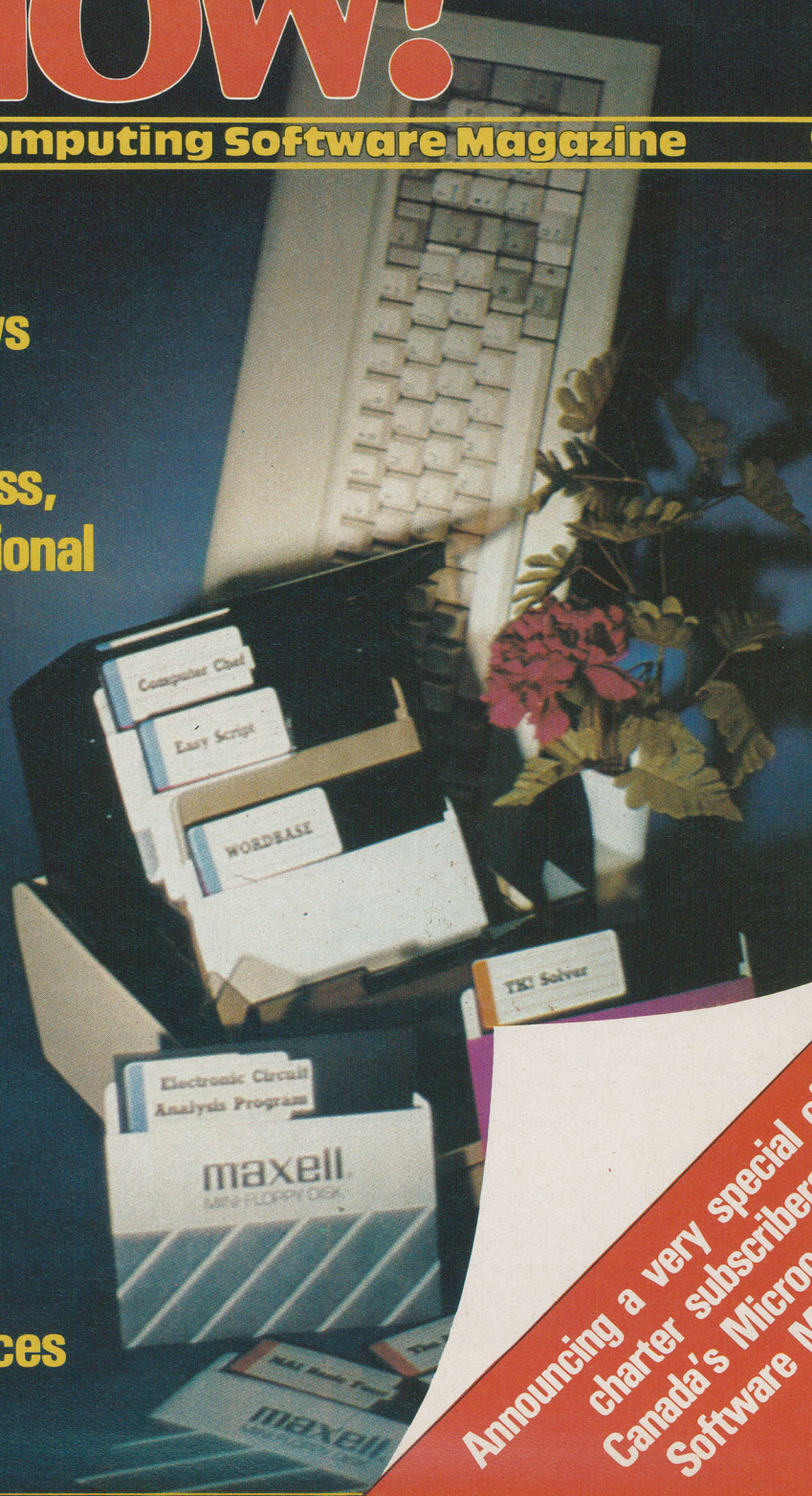- Up to the Minute Reviews
- News of Games, Business, Home, Professional and Education Packages
- Exciting New Applications
- Soft for IBM, Apple, CP/M, Commodore, Radio Shack, MacIntosh and more
- Canadian Sources



Announcing a very special offer for  
charter subscribers to  
Canada's Microcomputer  
Software Magazine!



### From The Editor.

Not knowing about software is a multiple edged sword. Not only don't you know what you need; you don't even know what you're missing. It's terribly easy to leap upon the first package that comes within waving distance of your application and then bend your application to suit it.

This is not the way it should be.

There is software for every use, perfect software for any conceivable purpose . . . but finding what you want can be a drag, if for no other reason than the constant repetition of the tune from Mission: Impossible playing inside your head.

The fabulous thing about editing a magazine like this is that you get to play with every package in the cosmos. However, this is extremely tiring . . . the fabulous thing about reading a magazine like this is that you get the benefit of being able to play with every package in the cosmos without actually having to do all that typing.

**Software Now!** will keep you abreast of what exists, tell you what probably shouldn't exist and inform you about where to get it so you can make it all exist for your needs.

We know that **Software Now!** is going to become one of the most essential accessories any computer user can own. Subscribe . . . Now! . . . and let us prove it to you.

*Steve Rimmer*

**Steve Rimmer**  
Editor,  
**Software Now!**

# Software Now!

---

## First Issue Octo

### A New Canadian Publication for the Ultimate Medium

The difference between we humans and the other inhabitants of the planet is our capacity for making tools. Civilization is often measured by its grasp of technology . . . it's through his use of tools that man has come to be able to manipulate his environment.

The computer is the ultimate tool . . . it is, like man himself, unspecific, and thus adaptable to virtually any task. The same computer can be a bookkeeper, a game, an artist's palette, a composer's amanuensis, a word processor or a programmer's development station.

The computer itself is simply a box full of chips. The power of computers lies in the software that runs on them.

**Software Now!** is the new magazine for people harnessing the power of the microcomputer. In its pages you will find the information which you will need to choose and apply the software that will dedicate your computer to your tasks. It will help you make sense of the myriad of similar software packages, translate the intricate complexities of software claims, understand the watershed breakthroughs in software development . . . and even have a bit of time left over to dematerialize a few aliens.

Perhaps most exciting, however, is that the pages of **Software Now!** will contain news about software for applications you've never even considered running on your computer. Imagine having an overview of the work of the world's most gifted program developers . . . and you'll have a good idea as to what this new publication is about.

**Software Now!** will be dealing with a broad range of systems and applications, encompassing eight, sixteen and thirty-two bit machines and software as diverse as video games, drafting systems and spreadsheets.

We've reached a level of development in microcomputer software wherein one needn't be a computer genius to apply a computer. In fact, one can operate a computer with only a bit more expertise than one needs to successfully make toast. The key that will unlock the power of your computer is the software you plug into it.

**The key to that software is understanding.**

**The key to understanding software is Software Now!**

### The Pedigree

**Software Now!** is published by Moorshead Publications, which also brings you Computing Now!, Electronics Today, Computers in Education and the Printout newsletter. It has been producing successful magazines in Canada since 1977.

Moorshead Publications is unique in the way it produces magazines. The expertise in applying microcomputers has allowed us to make virtually the entire process of publishing electronic. The editorial in the publications is created on word processing terminals and computer type set. All the financial planning is handled by computer, as is filing and list management. The company also

maintains an on line telecommunications computer to communicate with its readers.

The Editor of **Software Now!** is Steve Rimmer, who also edits Computing Now! In the first year of its existence Computing Now! went from a standing start to having over twenty two thousand subscribers, making it Canada's largest consumer microcomputer publication.

Steve has had experience with a wide range of software, from word processors to sophisticated music and graphics packages. He uses a number of computers, including several CP/M based machines, an IBM, an Apple II+, a Commodore and a MacIntosh.



# are w! ber 1984

## Features In The Queue

This is some of the editorial we have lined up for the first few issues of Software Now! You can expect it to change a bit... new software springs up almost daily, and Software Now! will always feature the most important developments in this dynamic field. Articles being developed during the preparation for the magazine include:

Computer Aided Drafting On a Micro • Techniques in MacPaint • How to choose a Spreadsheet • Apple Software Crate • Getting to the Root of UNIX • The Digital Research Pantry • A Thousand and One Word Processors • IBM's Productivity Family • Can Mac Write? • Professional Software Roundup • Power Programs for the 64 • Approaching the C • Word Processing Support Programs • dBase II Enhancements • Will it Run Multiuser? • Concurrent CP/M •.

**Reviews:** 10 Base • Mighty Mail • WORD-BASE • Easy Script • Computer Chef • Electronic Circuit Analysis Program • Superex Retailer • MAI Basic Four • The Print Shop • TK!Solver • Microsoft BASIC for the Macintosh • Sundog • Turbo PASCAL for the IBM • AutoCAD • MultiMate • Lexicheck and Word Juggler • Dataflex • Symphony • OmniTerm 2 • DB Master • Paint Magic.

In addition to this look for these regular features:

<b>The Library</b>	(Our monthly survey of books)
<b>By The Boards</b>	(Public domain software)
<b>Arcade</b>	(A blast at the latest games)
<b>Short File</b>	(A short overview of new releases)

## The Amazing Software Now! Software Disk Free to Charter Subscribers

At Moorshead Publications, we have always managed to launch new magazines with a flying start; this time we want our previous records to be smashed. We believe we have come up with "**an offer you can't refuse**".

The **Amazing Software Now! Program Disk** is, we believe, the best offer ever made to Charter Subscribers to a new magazine. A charter subscriber is one who helps provide the initial circulation base and we feel they deserve something special — what we are offering is just that.

The disk contains some fairly amazing custom written material:

**CalcNow:** A real spreadsheet program with many as the new features of programmes costing a small fortune. CalcNow is perfect for those who want to experiment with a spreadsheet and are dying to see how they work. It is far from a toy.

**DataBox:** A flexible data base manager and is a version of a program we developed for our own company use.

**Poker:** Life is not complete without a video game.

**Phone Jack:** A telecommunications terminal.

The contents of the disks vary depending on the system and additional programs come for some systems: see overleaf for a more complete description.

The **Software Now! Disk** is available in a huge number of different formats but we haven't forgotten you if you haven't got a disk drive or a system that we can accommodate: everyone will also receive a hard copy listing of those programs written in BASIC (listed for Microsoft Basic for you to modify yourself).

This disk will be sent to you **FREE** if we get your subscription order **before September 30th, 1984**. Early orders will get their disks as soon as processing and shipping time allow, later orders will receive them with the first copy of the magazine.

The **Software Now! Disk** is not available at this time **EXCEPT** to **Software Now! Charter Subscribers**. The software is currently in the final stages of development but we must reserve the right to modify the content.

Software Now! is available at a charter rate of **\$19.95** for a one year subscription, **\$34.95** for two years. This rate is valid until September 30th, 1984. This rate includes your choice of a free software disk... please specify the machine operating system and format you want the disk to run with: check those available.


**Software Now! Subscriptions**  
25 Overlea Boulevard Suite 601  
Toronto, Ontario  
M4H 1B1

## YOUR GUARANTEE

If you do decide that Software Now! is not the magazine you expected or want, or if you decide to cancel your subscription for any reason or no reason, you may do so and receive a refund on the unexpired portion at any time.

If, however, you cancel before receiving your **THIRD** issue, we will issue a complete refund. Charter Subscribers receiving the Software Disk as part of their subscription will have just \$3.00 deducted for the raw cost of the disk.

This guarantee is backed by the full resources of Moorshead Publications. Any refund will be made promptly and cheerfully.

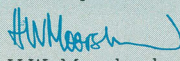  
H.W. Moorshead  
President

**Be a charter subscriber:  
Save up to 50% and get your Free  
Software Now! Disk**

## Advertising

For details on advertising in Software Now!,  
Call our Advertising  
Department: (416) 423-3262.



# The Amazing Software Now! Bonus Disk

**The programs available on the disks are as follows:**

[illegible]

```

ITEM ENTRY PAGE
-----
Record number [ 2 ]

Name of Item: [VIC 20 PROGRAMMER'S REFERENCE GUIDE ]
Supplier's Code: [VW118 ]
Internal Code: [C008 ]
Retail Price: [23.58 ]
Our Cost: [20.88 ]
Profit Per Item: [3.58 ]
Maximum Inventory: [25 ]
Current Inventory: [19 ]
Minimum Inventory: [15 ]

Enter, New Page or Abort: [E]

```

[illegible]

## CalcNow

CalcNow is a fully capable spreadsheet package. It can manage a sheet sixteen columns across by twenty six rows deep. It allows for automatic and manual recalculation, full cursor movement, formulae, constants and labels, disk storage of your sheets and a full hard copy reporting function. Its syntax and behavior is very much like that of the popular packages and for models of the size usually used in small business and personal financial planning it's equivalent to professional . . . and very much more expensive . . . spreadsheet packages.

## Phone Jack

Most computers have telecommunications hardware built into them . . . it's a shame that they don't all have software available to drive it. This program does basic telecommunications and, while its features do vary a bit from system to system . . . based on what the operating systems allowed us to implement . . . it does provide for the basic requirements of calling computer bulletin boards and dial up mainframes.

## Utility Pack

Most revisions of the disk will also have a choice selection of utility programs. These vary a lot from system to system so it's a bit difficult to describe them all here. However, these are the little routines that make life so much easier when you sit down at the keyboard and switch on.

## DataBox

Many commercial data base managers are extremely powerful, extremely expensive and, in fact, grossly over qualified for most tasks. DataBox can handle most of their routine tasks that data base managers are bought for. It is efficient of disk space, reasonably fast and very, very flexible. It can keep track of your files, your stock . . . or even your record collection. It features variable fields, hard copy reporting and flexible search parameters.

These programs will vary a bit from system to system . . . the following outlines the formats in which we can supply this software. You will need your own Microsoft compatible suitable BASIC Interpreter (e.g. GWBASIC, BASIC-80, MBASIC, APPLESOFT, RS BASIC, PET BASIC, Microsoft MacIntosh BASIC, etc.)

**For CP/M\* users:** CalcNow, DataBox, Poker!, Utility Pack, Phone Jack

**For Apple II +DOS Users:** CalcNow, Databox, Poker!, Phone Jack, Utility Pack plus Clef Hanger (An Apple Music Box), Skyhook (a teletype converter) and Fruit Crate (a BBS).

**For IBM Users:** CalcNow, Databox, Poker!, Utility Pack, Phone Jack plus Bandit (A slot machine simulator)

**For Macintosh Users:** CalcNow, Databox, Poker, Phone Jack and Letterhead (a stationary generator).

**For Commodore Users:** CalcNow, Databox, Poker, Utility Pack and Phone Jack.

**For TRS-80 Model III and 4:** CalcNow,  
Databox, Poker

## Poker!

We wanted to include a game on the disk and, after some deliberation decided that a good dimly lit, smokey card game would fill the bill best. This one simulates five card draw poker in the proper cowboy style. It can deal, draw, call, bet . . . do everything but cheat and pull its six gun on a really bad hand. POKER! features a graphic display of the cards being played.

This software is available as a free gift to charter subscribers to Software Now! magazine. To be eligible to receive this disk your subscription order must be at our offices no later than September 30th, 1984.

\* Available for Apple CP/M, Osborne single and double densities, Access Matrix, Kaypro II, Lobo max 80, Morrow Micro Decision, Olympia single and double, Superbrain, Systel/Olympia, DEC VT-180, Nelma Persona, Xerox/Cromemco, 3R Avatar, Casio FP-1000, Epson QX-10VD, Attache, Micromate, if800, Sanyo MBC 1000, Televideo, Zorba and on eight inch single sided single density disk.

**I'd like to become a Charter Subscriber to Software Now! and receive my Amazing Software Now! program disk.**

☐ **One year (12 issues) for \$19.95**

☐ **Two years (24 issues) for \$34.95**

Name \_\_\_\_\_

### Address

City \_\_\_\_\_ Province \_\_\_\_\_ Post Code \_\_\_\_\_

☐ **Cheque enclosed**☐ **Bill my Credit Card (Visa, Mastercard, American Express)**

No. \_\_\_\_\_ Expiry Date \_\_\_\_\_

☐ Bill me (we are happy to bill you but you will NOT qualify for a Software Now! program disk).

**Please specify the format you want for your disk**

**Offer expires September 30th, 1984.**

**Mail to: Software Now! Subscriptions,  
Moorshead Publications, 25 Overlea Blvd., Suite 601, Toronto, Ontario M4H 1B1.**

**Please Specify  
Your Disk Code as follows:**

<b>APP</b>	Apple II + DOS
<b>IBM</b>	IBM PC
<b>MAC</b>	Macintosh
<b>TRS</b>	Radio Shack Models 3 & 4
<b>CBM</b>	Commodore Disk formats
<b>ACP</b>	Apple CP/M
<b>OS1</b>	Osborne Single Sided
<b>OS2</b>	Osborne Double Sided
<b>AMT</b>	Access Matrix
<b>KAY</b>	Kaypro
<b>LOB</b>	Lobo max BO
<b>MOR</b>	Morrow Micro Decision
<b>OLI</b>	Olympia Single sided
<b>OL2</b>	Olympia Double sided
<b>SBR</b>	Superbrain
<b>SYS</b>	Systel/Olympia
<b>DEC</b>	DEC VT-180
<b>NEL</b>	Nelma Persona
<b>XER</b>	Xerox/Cromenco
<b>3RA</b>	3R Altavar
<b>CAS</b>	Casio FP-1000
<b>EPS</b>	Epson QX-10VD
<b>ATT</b>	Attache
<b>MIC</b>	Micromate
<b>SAN</b>	Sanyo MBC 1000
<b>TEL</b>	Televideo
<b>ZOR</b>	Zorba
<b>IF8</b>	#800
<b>8"</b>	8" Disk Single Sided, Single Density



# Heathkit<sup>®</sup>

**introduces the HS-151...the first fully compatible Personal Computer kit featuring Heathkit quality and IBM compatibility. Build it yourself and save \$750.00.**

**Consider this...85% of all the kits we sell are built by people who felt exactly as you probably do now...skeptical. They did it and you can too.**



**Look it over.** It really isn't as complicated as you may think. It's perfectly natural to feel that since a computer is a very complex instrument, a computer kit is going to be even more complicated than any other kit. But that simply isn't so! In fact there are more pre-assembled elements in the computer kit than most others. The central processing unit, the most important part of the computer, is not only pre-assembled, it's factory tested.

So we encourage you to drop in to any Heathkit store to have a look at the computer kit and ask all the questions you want... before you decide.

**We'll show you how to solder.** While you're in looking at the computer kit, ask to see the GDP-135 Soldering Iron which you'll get FREE with the computer kit and the Soldering Course designed to help you assemble the Computer and supplied as part of the kit. This Soldering Course really means business. Not only do you learn the why and how by reading all about it, the course includes an actual circuit board that you wire up and solder. So you learn, and practice and make any mistakes before you start on your kit. And if you'd like, you're invited to bring or send your completed test circuit board in to Heathkit. We'll tell what you're doing right and wrong, and if necessary how to improve your soldering technique. We want you to feel as confident about your success as we do.

**And we'll help if you get stuck.** If you require assistance when you get your kit finished or anywhere else along the way, you can either call or come in any Heathkit store and we'll get you back on track. We're committed to making sure you succeed. And if you've made an honest effort, and assembled your computer according to the instructions, we'll get you up and running, **free of charge — We Guarantee it —**

**It's our business to make sure you're happy with the kit you build.** So we make them as simple, straightforward and interesting as is humanly possible. And as for the manual and step-by-step directions, ask anyone who has built one... Heathkit is famous for the best manuals in the business. All of this means you can learn, have a good time and save \$750.00 while building *your* computer kit.

Our pledge to you... **We won't let you fail!**

• VANCOUVER, B.C. 604-437-7626 FROM VICTORIA 384-7511 • CALGARY, ALBERTA 403-252-2688  
• EDMONTON, ALBERTA 403-468-6195 • WINNIPEG, MANITOBA 204-783-3334 • MONTREAL, QUEBEC 514-332-3666 FROM QUEBEC CITY 647-2887  
• OTTAWA, ONTARIO 613-728-3731 • MISSISSAUGA, ONTARIO 416-277-3191 • MAIL ORDER:—HEATH CO. 416-232-2686

☐ Toll-Free order desk 1-800-268-2502

**Clip coupon and mail today to:**  
**Heath Company, 1020 Islington Ave., Toronto, Ont.**  
**M8Z 5Z3**

Please send my FREE Heathkit Catalogue with details on the new HS-151 Computer Kit, today!

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

Prov. \_\_\_\_\_ Postal Code \_\_\_\_\_



# Machine Code Programming Part 3

In this month's installment, Bob Bennet looks at a few methods of addressing using different CPUs.

LAST MONTH I gave a couple of CPU addressing mode examples, but before I give any more I would like to explain a couple of things. First, whenever possible, I will give other CPU direct equivalents to the Z80 instructions, but I can't possibly mention every CPU. What I hope to do is make it possible for you to recognize your own particular CPU instructions. To help you do this, don't pay too much attention to the *name* of the addressing mode, but rather what *happens* because of the instruction; different manufacturers have, at times, used slightly different terminology to describe similar actions. The second point is, that in every example I will give the hex code first followed by the mnemonic thus, 00h — NOP.

Although machine code doesn't use line numbers, the BASIC statement GO TO 100 has a very near equivalent in machine code, but the comparison cannot be taken too literally. These equivalents are the *jump* or *branch* instructions, part of which form the relative addressing mode. In this mode the instructions are two bytes long, the first byte is the function, and the second is the offset. In the Z80 instruction set, the straightforward jump instruction code is 18h — JR,e, or jump relative by the amount of the offset byte e. Why relative? Well, the value of the offset byte indicates a destination for the jump, relative to the current program position.

Because the offset is only one byte, the maximum jump is 255d (d = decimal) or FFh locations, but in which direction? The numbers 0 to 255d are positive, so a forward direction is indicated; this leaves the problem of going backwards. No sweat, the answer lies in the use of the 2's complement. Never heard of it? Don't worry, all will become clear.

Take the maximum range of a byte, 0 to 255d, and split it; the first section, 0 to 127d (7Fh) are the forward or positive range. The second step is where it might get confusing so watch it carefully; the numbers that are left from 128 to 255d or 80 to FFh, but, because we need a backwards, or negative, direction, the decimal numbers now range from -128 to -1.

Remember that I said you would need a knowledge of the binary system? This is where it comes in handy. The binary equivalents of the decimal numbers 0 to 127 and 128 to 255 are 0000 0000 to 0111 1111 and 1000 0000 to 1111 1111 respectively. A closer examination shows that, throughout the first set of numbers, but 7, the leftmost bit, is 0; and throughout the second set, but 7 is 1.

This makes it possible for bit 7 to be used as a sign bit: reset, or 0, for positive; and set, or 1, for negative. To get the value of the offset byte is easy. Counting the byte after the offset byte in the program as zero, count backwards or forwards until you reach the destination for the jump, as shown in Fig. 6. Another method would be to take the destination address, and the zero address, take the lower from the higher, and add the sign accordingly.

Assume that you have counted 100 places backwards; Fig. 7 shows what happens next. Alternatively, if you subtract the

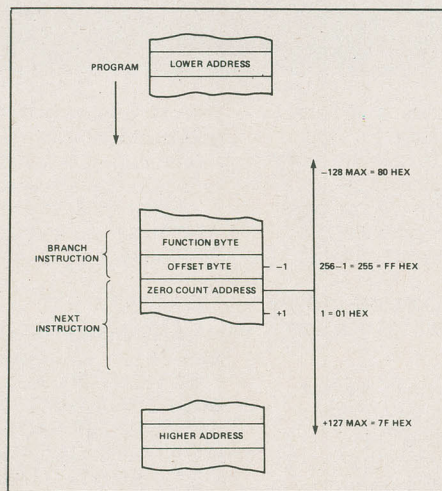


Fig. 6 Counting the value of the offset byte.

backwards count from 256d, the answer is a decimal number equal to the 2s complement, which you then convert to hex.

Some CPUs do not have a straightforward relative jump/branch in the instruction set, but some do support the conditional relative jumps/branches. This is similar to the BASIC IF X = 0 THEN GO TO 100. The Z80 instruction 28h — JR Z,e means jump relative if the zero flag is set, by the amount of the offset e. The 6502 code is F0h — BEQ which means branch when zero flag set. Usually most of the

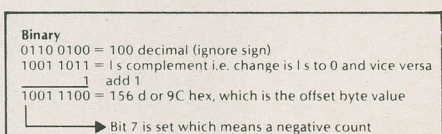


Fig. 7 2's complementing a backwards (negative) count.

flags can be used in the set or reset condition for relative jump or branch instructions.

## Absolutely So

Although the relative jumps and branches are sometimes of great help in a program, their range is rather limited as I have shown. To get further afield requires slightly different techniques, and different instructions of course. This set of instructions requires an absolute destination, or address, to be specified in the instruction. For those of you who like analogies, relative addressing is like saying 'go to the third house past the church' and the absolute equivalent is 'go to 31 Church Street'. This type of jump or branch is only a part of the absolute addressing mode instructions, but for now I'll deal with jumps.

Because, in theory, the whole of our 64K memory is reachable, the addresses will have to be in two bytes, so the total bytes for absolute addressing is at least three. There are special cases that require just one byte, and some that need four, but I'll cover them later. Let's assume for now that we need to jump unconditionally to address 30,000d; Fig. 8 shows how to convert the decimal number into the two byte hex number we need.


The Z80 instruction C3 — JP pq, where pq are the address bytes, and the 6502 instruction, 4C — JMP are box examples of jump in the absolute mode. Fig. 9 shows how both examples would be used in a program, when the destination was address 30,000d. Note that the low byte of the address goes straight after the code for jump; please accept that this is so for now, and I'll explain more later on.

In some of the instruction sets the flags status, or condition, can be used just as in the relative jumps.

Leaving the jump/branch instructions let's have a look at some more absolute instructions. The Z80 instruction 3A — LD A, (pq) means load the A register with the contents of the address pq. Note the use of brackets in the mnemonic; without them


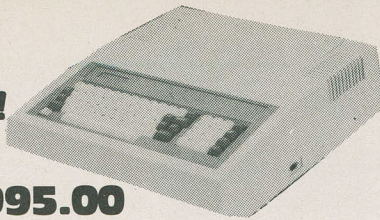
## WINNER: Ultra-modern! Super-efficient! Fully Apple Compatible \$995.00




Please note the distinct features  
Winner offers:

- \*Dual microprocessors 6502 & Z-80A
- \*RS-232 built in
- \*Disk drive interface card built in
- \*40/80 column text display and auto change video output port by soft switch
- \*76K RAM with 4 expansion slots

- \*16K ROM
- \*DOS 3.2 & DOS 3.3 capability
- \*Apple & CP/M compatible
- \*ASCII keyboard with function keys and a numeric keypad
- \*Upper/lower case
- \*Streamline case
- \*OS could be changed when desired without affecting other memory RAM

## CP80 DOT MATRIX PRINTER

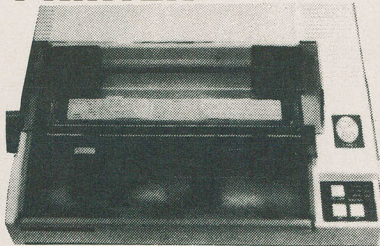

7X8 DOT MATRIX  
80 CPS, 640 dots/line per second  
Bidirectional  
80 Column normal  
142 Compressed  
Friction & Tractor Feed  
Standard Centronics Parallel  
Same as EPSON 80 **\$495.00**

## TTX™ 1014



RELIABLE DAISY  
WHEEL RO PRINTER

**\$595.00**

### 1014 FEATURES

- SERIAL AND PARALLEL INTERFACE
- WORDSTAR™ COMPATIBLE
- QUIET OPERATION
- PROGRAMMABLE PITCH AND LINE SPACING
- COMPACT AND DURABLE
- MICRO, MINI, MAINFRAME COMPATIBLE
- INTEGRAL PIN FEED GUIDE (ADJUSTABLE)
- RIBBON CARTRIDGES AND PRINT-WHEELS READILY AVAILABLE.

SEE OR CALL ABOUT OUR EXTENSIVE LINE OF PRINTERS.

## APPLE COMPATIBLE COMPUTERS

48K Color Computer with numeric keys & function keys **\$549.95**

64K Color Computer with numeric and function keys **\$598.95**

64K Color Computers (Dual-6502 & Z80A, CP/M), Numeric & function keys **\$649.95**

For systems one 12" Green Monitor, 1 Disk Drive & Disk Controller card **\$500.00**

All above Systems  
with New IBM™  
Styling 100.00 extra



- Detachable Keyboard
- Programmable Function Keys
- Built in Key Words for Apple™ Soft, DOS
- Room for two Slim Line Drives



## Mini Modem

**\$99.45**

### Parts

DB-25P Connector	\$ 4.95
DB-25S Connector	\$ 5.95
Covers for 25's	\$ 2.25
DB-9P	\$ 3.95
DB-9S	\$ 4.95
Covers for 9's	\$ 1.98
2716 EPROMS	\$ 6.95
2764 EPROMS	\$14.95
4164 RAMS 200 N/S	\$ 9.75
4116 RAMS 200 N/S	\$ 1.75
2016 RAMS	\$ 9.75
EPROM ERASERS P.E. 14	
8 at a time	\$129.95

### Disk Holders


Disk Bank (50 Disks)	\$39.95
DX 85 (55 Disks)	\$39.95
Data Defender (70 Disks)	\$39.95
Flip "N" File 10	\$ 8.95
Flip "N" File 15	\$13.95
Flip "N" File 25	\$34.95
Flip "N" File 50	\$44.95
Flip "N" File Original 50	\$29.95

### Diskettes

Xidex SS/DD	\$29.95
Xidex (Plain Box) SS/DD	\$24.95
Xidex DS/DD	\$39.95
3M Diskette SS/DD	\$29.95
Verbatim (Datalife) SS/DD	\$34.95
Maxell MD 1-DS/DD	\$34.95
Maxell MD 2-DD/DD	\$49.95
Dysan SS/SD 104-1	\$29.95
Dysan SS/DD 104-2	\$34.95
Dysan DS/DD 204-2	\$49.95
Disk Cleaning Kit Recoton	\$34.95

## 6502 BOARDS & ACCESSORIES

## Timex Sinclair 1000

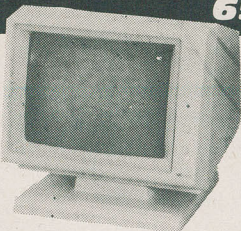


Swivell  
Monitor  
Amber  
GM 1211 \$165.00

### More Monitors

Roland CB 141 Colour	\$395.95
Amdek Colour	\$395.95
GM 1201 Green 12"	\$149.95
GM 1201 Amber 12"	\$159.95
Zenith Green 12"	\$139.95
Zenith Amber 12"	\$149.95

More Available

ABB-1	\$45.00	AKB-2	\$99.00
APPLE II Compatible.		Keyboard: Numeric	
Dual CPU Bare Board		Keypad with Function	
Comm Card	\$98.00	Keys, replacement for	
Serial interface RS232C		APPLE II.	
Card for APPLE II c/w		AC-2	\$89.00
Cable & Manual.		Beige APPLE II Case (for	
AIC-1	\$89.00	above Keyboard)	
Integer Card		Case & Keyboard	
AEC-1	\$89.00	Numeric	\$175.00
80 Column Card		APS-2	\$99.00
AZC-1	\$79.00	Switching Power Supply	
Z80A (CPM) Card		for APPLE II, + 5V 5	
APC-1	\$89.00	amps, + 12V @33 amps.	
Parallel Printer Card		5V @ 1/2 amp, 12V @ 1/2	
ASC-1	\$89.00	amps, c/w on-off switch &	
Serial Printer Card		connecting wires	
ALC-1	\$89.00	AAA-2	
16K RAM (Language Card		Dis Drives 5 1/4", APPLE II	
Speech Card	\$75.00	Compatible, Excluding	
Wild Card	\$89.00	Controller Card	\$299.00
Modem Card	\$175.00	With Controller	\$385.00
(Networker)		ADC-1	\$89.00
40 Column Switch	\$9.95	Disc Drive Controller	
Colour RF Modulator	\$25.00	Card for two drives, Apple	
		II Compatible	
		APPLE II is a registered	
		trade mark of Apple Com-	
		puter Inc.	

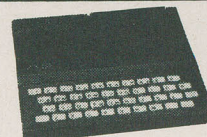

Assembled  
**\$39.95**

ZX81 Printer  
**\$99.00**

## 16K Sinclair Memory \$35.00

### Books

COMPLETE ZX81 BASIC COURSE - Inc. 2	39.95
18998	19.95
NOT ONLY 30 PROGRAMS: 1K	19.95
MACHINE LANGUAGE MADE SIMPLE	24.95
ZX81 ROM DISASSEMBLY PART A & PART B	19.95
UNDERSTANDING ZX81 ROM	19.95
T/S 1000: PROGRAMS, GAMES and	19.95
GRAPHICS	23.95
LEARNING T/S BASIC	29.95
THE BASIC HANDBOOK	19.95
49 EXPLODING GAMES	24.95
COMPUTER FOR KITS SINCLAIR EDITION	8.95
MASTERING MACHINE CODE ON YOUR ZX81	24.95
T/S 1000 USERS GUIDE (Vol 1)	19.95
EXPLORERS GUIDE TO THE ZX81	19.95
ZX81 POCKET BOOK	19.95
GETAWAY GUIDE	19.95
GETTING ACQUAINTED WITH YOUR ZX81	19.95

### Hardware

Sinclair Printers	99.00
Timex Printer	125.00
64K RAM (Memotech)	149.00
32K RAM (Memotech)	79.00
16K RAM (Sinclair)	35.00
Memotech 16K RAM	39.95
500MA	8.95
Memopak Centronics Type	
Parallel Printer Interface	119.00
Memopak ZX81 Keyboard	119.00

Additional Hardware & Software  
for the SINCLAIR ZX81  
AVAILABLE ON REQUEST.

## Orion Electronic Supplies Inc.

40 Lancaster Street West  
Kitchener, Ontario N2H 4S9  
(519) 576-9902

Master Charge & Visa. COD. Cheque.  
Money Orders accepted. COD's, shipping  
& insurance extra. Write for our  
FREE FLYER.

Prices subject to change without  
notice.



# Advanced 6502 Programming

Using the instructions of the 6502 in a non-standard way, you can write quick and efficient machine language programs for the Apple or other computers.

by Yin H. Pun

THERE ARE A FEW programming techniques which you cannot find in most machine language programming books, but they are commonly used by programmers and crackers alike. These techniques use instructions of the 6502 microprocessor in a non-standard way; they are quite useful in writing quick and efficient machine language (even though its structure may be harder for someone else to understand!). I will use the Apple 6502 to explain these techniques, although they can be easily implemented on other 6502 machines.

## Self-Modifying Code

Self-modifying code is not a new instruction. Self-modifying code uses immediate or absolute addressing and can easily replace indirect addressing. Briefly, the operand is changed into another value. For example, you may simulate an indirect JMP instruction with an absolute "JMP" instruction if you simply change the operand to other instruction. The advantage of self-modifying code is its ease of use and 30% faster execution speed. Best of all, self-modifying code uses no zero-page locations like indirect addressing to work.

Try this little gem:

```
BEG JMP OUT
BEG2 LDA #$69
      STA OUT + 1
      LDA #$FF
      STA OUT + 2
OUT JMP BEG2
```

This routine will first "jump" to "OUT" and then "jump" back to the code where it changes itself. The operand of "JMP" at "OUT" will be modified and then executed. The program will jump to address \$FF69, the monitor program of the Apple.

Self-modifying code lends itself useful in quickly storing or retrieving values in a loop.

\* PROGRAM TO POKE \$00 INTO \$2000 to \$3FFF  
\* AND USES SELF-MODIFYING CODE

```
      LDA    #$00      ;Initialize the
                        ;operand of the
                        ;"STORE A" in-
                        ;structionn
      STA    STO + 1
      LDA    #$20
      STA    STO + 2
LOOP  LDA    #$00
      STO    STA        ;self modifying
                        ;code
      INC    STO + 1    ;increment operand
      BNE    NEXT
      INC    STO + 2
NEXT  LDA    STO + 2
      CMP    #$40      ;finished?
      BNE    LOOP      ;no, Loop again
      RTS             ;Yes, and quit
```

The only problem with self-modifying code is that the program becomes quite messy when it is overused. Operands must be initialized back to their original values if the routine is to be used again. It cannot be programmed into ROM for obvious reasons.

## Playing With The Stack

The stack of the 6502 is located in page 1 of the memory map (\$100-\$1FF). It is like a piece of notepaper which the 6502 uses to keep track of subroutine and interrupt return addresses. Also, it may be used to temporarily save an accumulator value.

The "JSR", "jump to subroutine" instruction, analogous to the BASIC "GOSUB", stores the program counter into the stack and loads its 2-byte operand into the program counter. The program flow is thus routed to the subroutine. An "RTS", "return from subroutine" fetches the program counter from the stack and thus returns control to the main program. You may manipulate the stack and the stack pointer to "pop" a return address to fool the microprocessor and make it forget that it had ever jumped to a subroutine. You may alter the return address so that the program will jump to a location other than its return address.

To retrieve the return address during a subroutine and make the microprocessor "forget" the return address, pull the accumulator from the stack twice. The first pull should return the high order byte and the second pull should return the low order byte of the return address.

```
SUBR PLA
      STA HIGH ;store high order byte in
                ;memory
      PLA
      STA LOW  ;store low order byte in
                ;memory
```

\* BUT DO NOT DO AN RTS INSTRUCTION  
\* BECAUSE THE INTENDED RETURN ADDRESS  
\* WILL NOT BE THERE AND THE ADDRESS,  
\* ONE BEFORE THE INTENDED, WILL BE  
\* CONSIDERED.

To place back the return address, push the values back into the stack just before executing the RTS.

```
      LDA LOW
      PHA    ;push low order byte of return
                ;address into stack
      LDA HIGH
      PHA    ;push high order byte of return
                ;address into stack
      RTS
```

Of course, you may execute an "RTS" instruction to simulate a "JMP" by simply pushing an address into the stack. However, you need the address which is always one less than the intended one, so subtract one from the address before pushing it into the stack. This is because the program counter (another register in the 6502) increments the return address before executing it.

For example:

```
LDA #$68
PHA
LDA #$FF
PHA
RTS
```

is the same as:

```
JMP $FF69 ($FF68 + 1)
```

the program may see what location it is running at by jumping to a subroutine, returning and pulling the address from the stack. Peripheral cards use this type of routine to determine what slot the card is in. Here you must use the stack pointer.

For example:


```
JSR $FF58 ;$FF58 simply contains a dum-
           ;my subroutine; it only contains
           ;an "RTS"
TSX       ;transfer stack pointer to X
LDA $100,X ;fetch high order byte
STA HIGH  ;store high order byte in
           ;memory
DEX
LDA $100,X ;fetch low order byte
STA LOW   ;store low order byte in
           ;memory
```



# OSCILLOSCOPES!
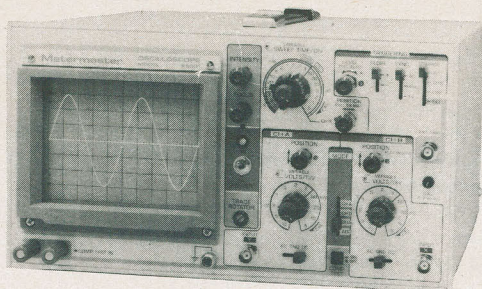
## The Best Buys Available

**Model 65601**  
Dual Trace Bench/Portable Scope




**\$ 695.00**

Probes & FST  
included

Featuring at no extra cost . . . . . 'The Component Tester'

- 20 MHz (-3dB) Bandwidth
- 6" CRT Display
- Fully Automatic Triggering
- Trace Rotator
- 5 mV Vertical Sensitivity
- HF Rejection

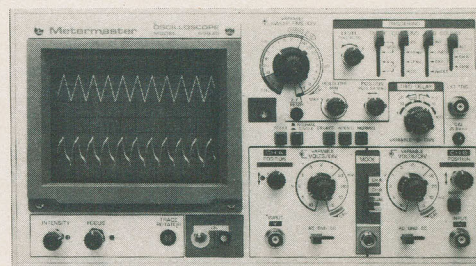**Model 65635**  
Dual Trace Bench/Portable Scope



**\$ 895.00**

Probes & FST  
included

- 35 MHz (-3dB) Bandwidth
- Delayed Sweep (selectable)
- Single Sweep (selectable)
- 6" CRT Display
- 1 mV Optimal Sensitivity
- X-Y or X-Y-Z Operation
- 120V AC Line Operation
- x5 Sweep Magnifier

# MULTIMETERS!


## Go for Quality --- Go for The Best Value

**Models 78020, 78021, 78022**


- AUTO ZERO
- AUTO POLARITY
- 3½ DIGIT LCD
- FULL OVERLOAD PROTECTION ON ALL RANGES
- RECESSED - SAFETY DESIGNED INPUT TERMINALS

Supplied with:

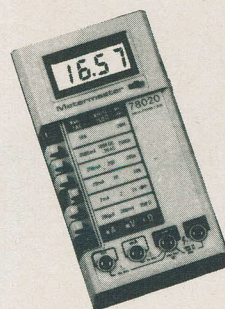
- 28 Page Operating and Maintenance Manual
- Calibration Certificate Traceable to NRC
- Schematic with complete Parts Listing
- Safety Test Leads
- One-year Warranty



**\$ 139.00\***

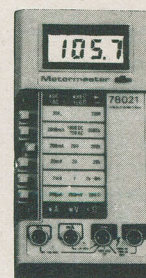

**\$ 99.00\***

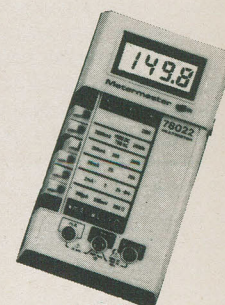

**\$ 89.00\***

- ◆ ±0.1% DC
- ◆ 2000 hrs Bat. life

- ◆ ±0.25% DC
- ◆ 10 Amps AC+DC
- ◆ 200 hrs Bat. life

- ◆ ±0.25% DC
- ◆ 200 hrs Bat. life

\* F.S.T. extra

### Metermaster

A Div. of R.H. NICHOLS CO. LTD.

Head Office: 80 Vinyl Court, Woodbridge, Ontario L4L 4A3



5% Discount for Cash,  
Certified Cheque, or Money Order  
DEALER INQUIRIES INVITED

All prices F.O.B.  
Downsview, Ontario  
subject to change with-  
out notice. P.S.T. extra  
where applicable.

TORONTO (416) 851-8871 • MONTREAL (514) 337-0425 • EDMONTON (403) 432-7746 • OTTAWA (613) 238-7007

Circle No. 22 on Reader Service Card.



## Advanced 6502 Programming

### Simulating a BASIC "PRINT" Instruction

The code below simulates a BASIC "PRINT" instruction by altering the stack. The actual ASCII text to be printed is located immediately after the JSR instruction. The program flow will not return to the code immediately after the JSR instruction, but will skip the next real instruction after text. If the stack were not modified, the routine would return and try to execute the text codes which are garbage. Use a macro-assembler such as TOOLKIT ASSEMBLER or LISA to enter this code.

```
*MANIPULATING THE STACK PRINT ROUTINE
PROINT EQU $FE
COUT EQU $FDED ;$FDED is character output routine for Apple
ORD $800
JSR PRINT ;call print routine to print text below
ASC "MODIFYING THE STACK."
HEX 8D ;must terminate text with a carriage return
($8D = CR)

JSR PRINT
ASC "MAL ALEGNA SKANHT! IT WORKS!"
HEX 8D
BRK ;stop this! or put "RTS" to exit safely

* THIS IS THE ACTUAL PRINT ROUTINE
PRINT PLA ;fetch JSR address low order byte
STA PROINT ;store program pointer in memory
PLA ;fetch JSR address high order byte
STA PROINT+1
PRINT2 INC PROINT ;increment JSR address
BNE PRINT3
INC PROINT+1
PRINT3 LDX #$0
LDA (PROINT,X) ;get character
JSR COUT ;output character
CMP #$8D ;is it a carriage return?
BEQ EXIT ;exit if it is

BACK CLC
BCC PRINT2
EXIT LDA PROINT+1 ;modify stack to restore return address
PHA
LDA PROINT
PHA
RTS ;execute modified return address
```

### "BIT" As A "Reference" Instruction

The "BIT" instruction is used to test bits 6 and 7 of a memory location, so that appropriate action may be taken because of the status of these bits. Usually, a conditional branch (a "BMI" or "BPL" for example) follows this instruction; however, there is another quite uncommon use of this instruction.

Sometimes to save program space, you must introduce dummy instructions to act as spacers to mask other instructions as data. Dummy instructions also are used to activate I/O locations which need only be referenced, such as the speaker and the video mode soft switches. The "BIT" instruction is best suited for a dummy instruction. It is a read instruction which only affects the bit 6 and bit 7 of the status register. Instead of using "LDA \$C030", to toggle the speaker, use "BIT \$C030". "Bit \$C030" does not load the accumulator with garbage and thus keeps it free to do other things for example, keep count of a loop.

A routine to beep the speaker:

```
LOOP LDX #$30 ;number of speaker toggles or "clicks"
BIT $C030
LDA #$10
JSR $FCA8 ;wait routine (wait half the period of the
wave)

DEX
BNE LOOP
```

The "BIT" can be used to activate or test other I/O locations.

```
NO BIT $C010 ;clears the keyboard strobe
BIT $C000 ;check if keyboard is pressed
BPL NO ;if keyboard location is greater than 128, go
test keyboard again
RTS ;otherwise continue
```

or turn on the hi-res screen without affecting other registers:

```
HI BIT $C051 ;select graphics mode
BIT $C057 ;select hi-res graphics
BIT $C054 ;select primary graphics page ($2000-$3FFF)
BIT $C052 ;select whole graphics page (no text at bottom)
```

The "BIT" instruction can be interchanged with the "LDA" instruction, but using "LDA" destroys your data in the accumulator. Therefore, "BIT" makes a good instruction to simply "reference" a certain address where the data passed to or from the address is irrelevant.


To use the "BIT" as a dummy instruction to mask other instructions, use absolute addressing.

For example:

```
ZERO LDA #$00
FF BIT $A9FF ;the data $A9FF actually means
LDA $FF if you disassemble it
starting from FF+1
```

This routine when entered at "ZERO" would load the accumulator with \$00 and execute the "BIT \$A9FF" instruction which is meaningless and does nothing practical. However, if you disassemble the code at FF+1, skipping the "BIT" instruction, you interpret the operand, "A9FF" as an instruction, "LDA #\$FF". This effectively loads the accumulator with \$FF instead. This type of routine is especially useful in conditional branching where you have to load a parameter with a certain value depending on the condition, before it jumps to a subroutine as in the following example.
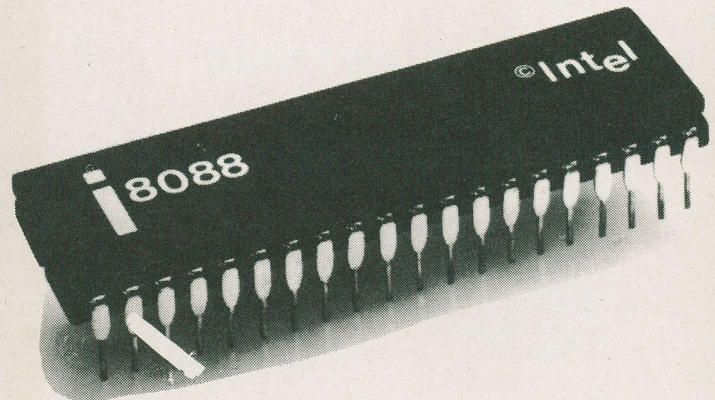
```
COND CMP #$00 ;is accumulator a zero?
BEQ FF + 1 ;if it is, then load accumulator with $FF
ZERO LDA #$00 ;load accumulator with zero if it is not.
FF BIT $A9FF ;the data $A9FF actually means LDA #$FF
if it is disassembled starting from FF+1
```



### Conclusion

These advanced techniques perhaps stretch the limits of the 6502 microprocessor, but should give some insight into some of its hidden capacities. The 6502 is alive and well!

ETI



# CIRCUIT IDEAS

## Tone Control

Last month our circuit feature showed the block diagram of a tone circuit. Here's the complete circuit.

ALTHOUGH fully paid-up members of the Flat Earth Society would have us believe that any form of signal processing is guaranteed to make a pig's ear of the emotional experience of listening to a group of musical morons twanging guitars and wailing, it should be remembered that most recordings are subject to considerable amounts of 'equalization', usually to satisfy the producer's requirement for a particular type of sound. No allowance is made for the introduction of random phase shifts, or that the intricate relationship of harmonics is sent on a one-way trip to the cleaners. The object is to change the sound to make it more satisfactory, and if tone controls are used in the replay process for exactly the same purpose, surely no-one has the right to complain?

The type of tone control fitted to most hi-fi equipment is far from ideal, usually being much too dramatic in operation — for example, if it is required to lift frequencies below about 100 Hz, the effect is usually to lift, by varying amounts,

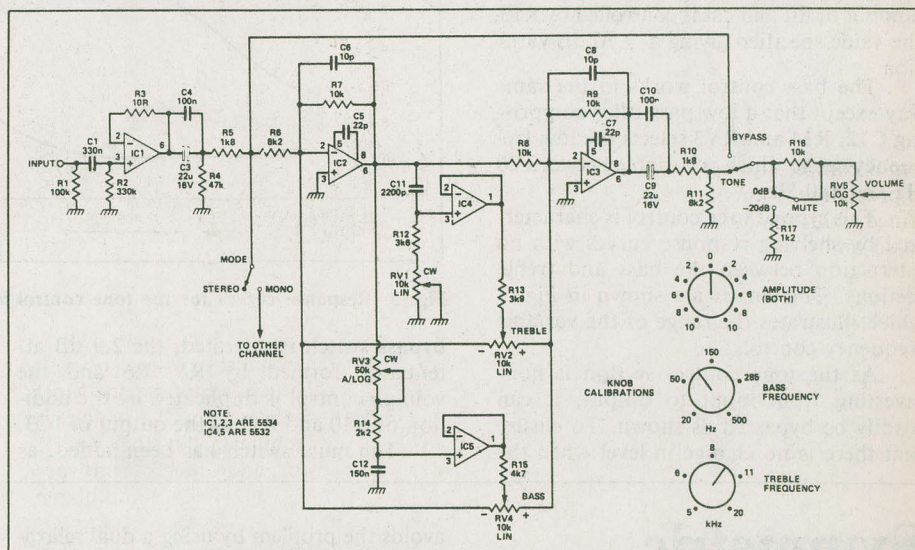


Fig. 2. Circuit diagram of the tone control module.

everything up to at least 1 kHz, and even higher.

The circuit shown in Figures 1 and 2 is somewhat more sophisticated than usual, possessing in addition to the normal lift and cut controls, adjustment of the turn-over frequencies of the two sections.

Operation of the circuit is quite straightforward. IC1 acts as an input buffer, presenting an input impedance of approximately 100k ohms to the line inputs of the preamplifier. The input of IC1 is AC

coupled by C1, which together with R2 fixes the -3 dB point at about 1.5 Hz — low enough to prevent objectionable low frequency phase shift. The output of IC1 drives the pair of inverting stages formed by IC2 and IC3, the input resistor to IC2 being split to allow mono summing of the two channels. The signal path is maintained at unity gain by the equal input and feedback resistors of the two stages.

The output of IC2 feeds two single-pole filters which are buffered by IC4 and

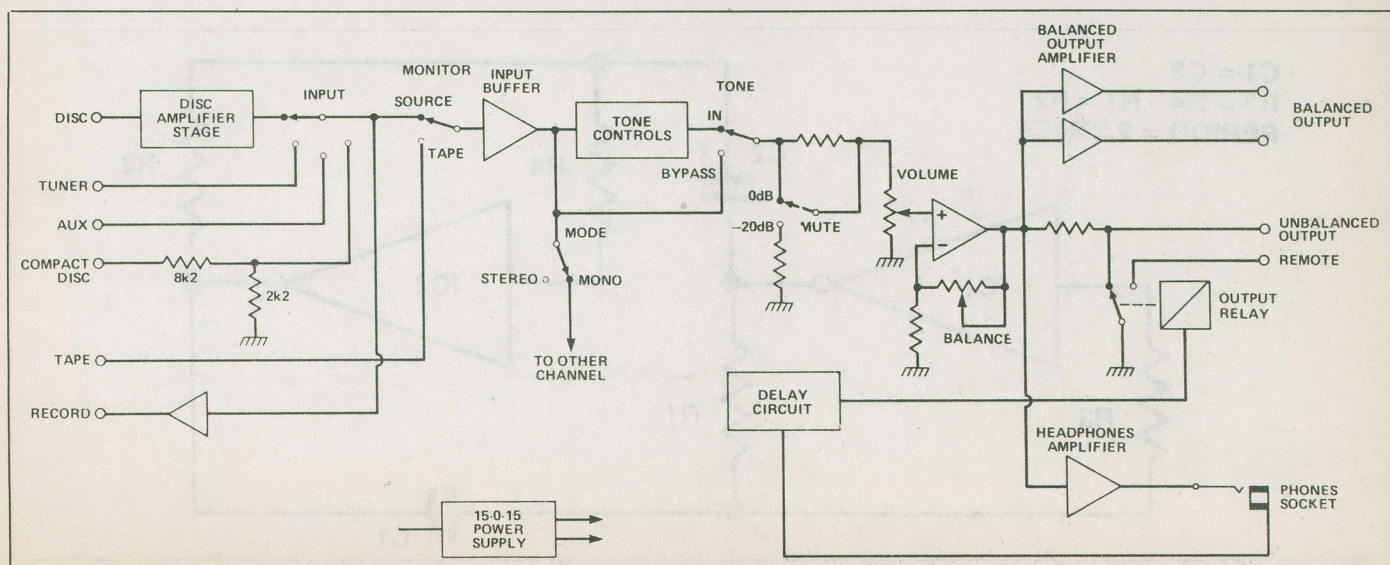


Fig. 1. Block diagram of the extended preamp.



## Circuit Ideas

IC5. The filter formed by C11, R12 and RV1 has a high pass characteristic with its -3 dB point adjustable by VR1 from 5.3 kHz to 20 kHz. Operation of the treble control, RV2, decides the destination of the high frequencies that emerge from the output of IC4 — in the "Cut" position, they are applied as negative feedback to IC2, and in the "lift" position, they bypass R8 giving additional gain to IC3. The amount of lift and cut is controlled by R13, the value specified giving a  $\pm 10$  dB variation.

The bass control works in the same way except that a low pass filter comprising C12, R14 and RV3 selects the low frequency range which is variable between 20 Hz and 480 Hz.

This type of tone control is characterized by shelving response curves with no interaction between the bass and treble sections. The curves are shown in Fig. 3 which illustrates the range of the variable frequency controls.

As the tone control section is non-inverting from input to output, it can readily be bypassed as shown. To ensure that there is no change in level when the

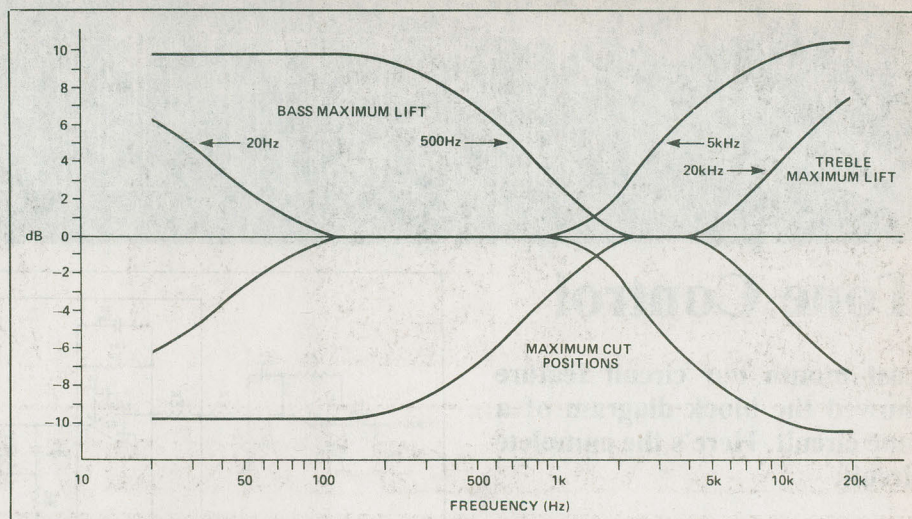


Fig. 3. Response curves for the tone control module.

bypass switch is operated, the 2.9 dB attenuator formed by R5, R6 and the volume control is duplicated by the addition of R10 and R11 at the output of IC3.

The mute switch has been added, as

much for convenience as anything. When changing records or when the phone rings, it is very useful to be able to reduce the overall gain without disturbing the volume control setting.

## Symmetric Multivibrator

Dr. Ton Trancong


THE CIRCUIT uses the dual RC relaxation circuits formed by R1C1 and R2C2, and is self-starting as it has no stable steady-state. While astable multivibrators using a single RC relaxation circuit suffer non-unity space-to-mark ratio due to the transfer voltage not being exactly halfway between the supply voltages, the circuit

avoids the problem by using a dual relaxation circuit based on two inverter sections on the same IC chip.

The voltages applied to the gates of both inverters relax exponentially until one of them reaches its gate's transfer voltage. Hence the states of the inverters change instantaneously and the cycle repeats with the two inverters swapping their roles.

Resistors R3 and R4 should have a value of more than three times that of R1 and R2 for the RC relaxation circuits to behave as if R3 and R4 were infinite. However, too high values of R3 and R4 may affect the operation of the circuit as the voltages at the inputs of the inverters

may then fail to follow the relaxation voltages. The only requirements for proper operation are the IC1 and IC2 must be sections of the same physical integrated circuit chip, and that corresponding components of the dual circuits must have the same nominal values. A 4009 CMOS hex-inverter chip with  $R1 = R2 = 300K$  (20%),  $R3 = R4 = 1M$  (20%),  $C1 = C2 = 680p$  (10%) should produce acceptable results. The frequency obtained is fairly stable (with 33% variation when the supply voltage varies between 3.3 V and 15 V) and its duty cycle is almost a perfect 1:1 over the whole permissible range of supply voltage.

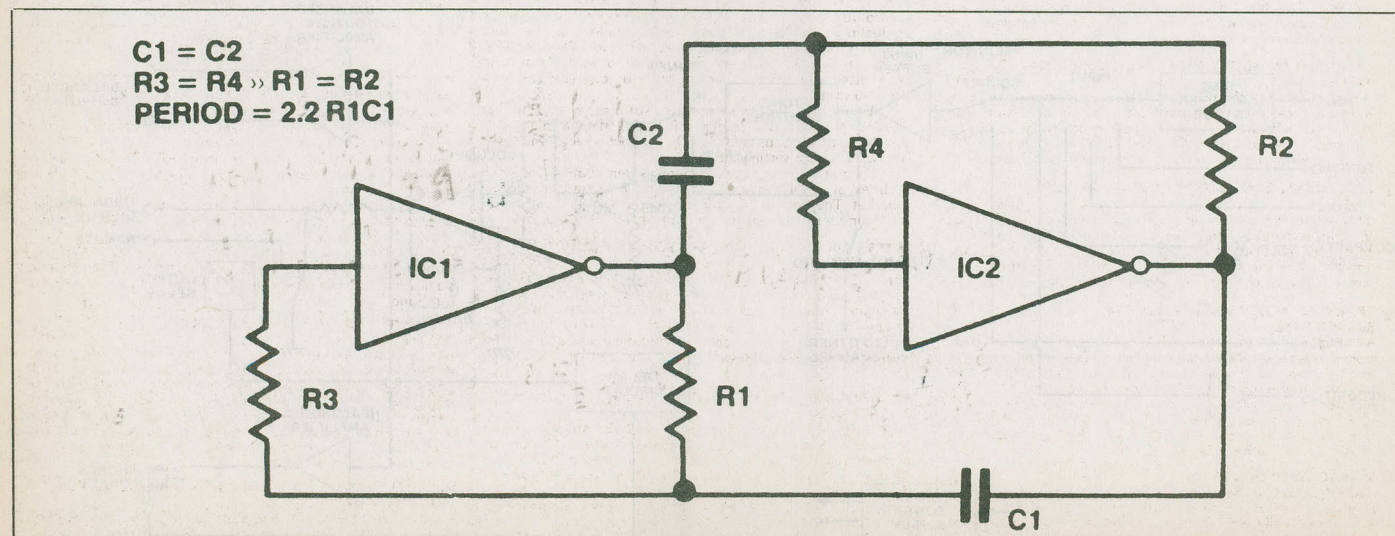

continued on page 52





# Electronics Today Bookshelf

## Top 10 Electronic Books

Based on sales  
from  
**Moorshead  
Publications  
Book Service**

### 1 BP73: REMOTE CONTROL PROJECTS \$8.10 OWEN BISHOP

This book is aimed primarily at the electronics enthusiast who wishes to experiment with remote control. Full explanations have been given so that the reader can fully understand how the circuits work and can more easily see how to modify them for other purposes, depending on personal requirements. Not only are radio control systems considered but also infra-red, visible light and ultrasonic systems as are the use of Logic ICs and Pulse position modulation etc.

### 2 BP90: AUDIO PROJECTS \$7.60 F.G. RAYER

Covers in detail the construction of a wide range of audio projects. The text has been divided into preamplifiers and mixers, power amplifiers, tone controls and matching and miscellaneous projects.

### 3 The GIANT HANDBOOK OF ELECTRONIC CIRCUITS \$27.95 TAB No.1300

About as thick as the Webster's dictionary, and having many more circuit diagrams, this book is ideal for any experimenter who wants to keep amused for several centuries. If there isn't a circuit for it in here, you should have no difficulty convincing yourself you don't really want to build it.

### 4 ELECTRONIC TROUBLESHOOTING HANDBOOK \$11.95 AB019

This workbench guide can show you how to pinpoint circuit troubles in minutes, how to test anything electronic, and how to get the most out of low cost test equipment. You can use any and all of the time-saving shortcuts to rapidly locate and repair all types of electronic equipment malfunctions.

### 5 BP74: ELECTRONIC MUSIC PROJECTS \$7.20 R.A. PENFOLD

Although one of the more recent branches of amateur electronics, electronic music has now become extremely popular and there are many projects which fall into this category. The purpose of this book is to provide the constructor with a number of practical circuits for the less complex items of electronic music equipment, including such things as a Fuzz Box, Waa-Waa Pedal, Sustain Unit, Reverberation and Phaser-Units, Tremolo Generator etc.

### 6 BP44: IC 555 PROJECTS \$7.75 E.A. PARR, B.Sc., C.Eng., M.I.E.E.

Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. Included in this book are Basic and General Circuits, Motor Car and Model Railway Circuits, Alarms and Noise Makers as well as a section on the 556, 558 and 559 timers.

### 7 BP37: 50 PROJECTS USING RELAYS, \$7.75 SCR's & TRIACS F.G. RAYER, T.Eng.(CEI), Assoc.IERE

Relays, silicon controlled rectifiers (SCR's) and bi-directional triodes (TRIACS) have a wide range of applications in electronics today. This book gives tried and practical working circuits which should present the minimum of difficulty for the enthusiast to construct. In most of the circuits there is a wide latitude in component values and types, allowing easy modification of circuits or ready adaptation of them to individual needs.

### 8 BP79: RADIO CONTROL FOR BEGINNERS \$6.80 F.G. RAYER, T.Eng.(CEI), Assoc.IERE

The aim of this book is to act as an introduction to Radio Control for beginners to the hobby. The book will commence by dealing with the conditions that are allowable for such things as frequency and power of transmission. This is followed by a "block" explanation of how control-device and transmitter operate and receiver and actuator(s) produce motion in a model.

Details are then given of actual solid state transmitting equipment which the reader can build. Plain and loaded aerials are then discussed and so is the field-strength meter to help with proper setting up.

The radio receiving equipment is then dealt with which includes a simple receiver and also a crystal controlled superhet. The book ends with the electro-mechanical means of obtaining movement of the controls of the model.

### 9 99 TEST EQUIPMENT PROJECTS YOU CAN BUILD \$15.95 TAB No.805

An excellent source book for the hobbyist who wants to build up his work bench inexpensively. Projects range from a simple signal tracer to a 50MHz frequency counter. There are circuits to measure just about any electrical quantity: voltage, current, capacitance, impedance and more. The variety is endless and includes just about anything you could wish for!

### 10 BP76: POWER SUPPLY PROJECTS \$7.75 R.A. PENFOLD

Line power supplies are an essential part of many electronics projects. The purpose of this book is to give a number of power supply designs, including simple unregulated types, fixed voltage regulated types, and variable voltage stabilised designs, the latter being primarily intended for use as bench supplies for the electronics workshop. The designs provided are all low voltage types for semiconductor circuits.

There are other types of power supply and a number of these are dealt with in the final chapter, including a cassette power supply, Ni-Cd battery charger, voltage step up circuit and a simple inverter.

## ELECTRONIC THEORY

### ELEMENTS OF ELECTRONICS — AN ON-GOING SERIES

F.A. WILSON, C.G.I.A., C.Eng.,	
BP62: BOOK 1. The Simple Electronic Circuit and Components	1.70
BP63: BOOK 2. Alternating Current Theory	\$ 8.55
BP64: BOOK 3. Semiconductor Technology	\$ 8.55
BP77: BOOK 4. Microprocessing Systems And Circuits	\$11.70
BP89: BOOK 5. Communication	\$11.70

The aim of this series of books can be stated quite simply — it is to provide an inexpensive introduction to modern electronics so that the reader will start on the right road by thoroughly understanding the fundamental principles involved.

Although written especially for readers with no more than ordinary arithmetical skills, the use of mathematics is not avoided, and all the mathematics required is taught as the reader progresses.

Each book is a complete treatise of a particular branch of the subject and, therefore, can be used on its own with one proviso, that the later books do not duplicate material from their predecessors, thus a working knowledge of the subjects covered by the earlier books is assumed.

BOOK 1: This book contains all the fundamental theory necessary to lead to a full understanding of the simple electronic circuit and its main components.

BOOK 2: This book continues with alternating current theory without which there can be no comprehension of speech, music, radio, television or even the electricity utilities.

BOOK 3: Follows on semiconductor technology, leading up to transistors and integrated circuits.

BOOK 4: A complete description of the internal workings of microprocessor.

BOOK 5: A book covering the whole communication scene.

PH247: DIGITAL TECHNIQUES \$29.00  
Covers logic circuits, Boolean Algebra, flip-flops, registers, combinational logic circuitry, and digital design.

## PROJECTS

### BP48: ELECTRONIC PROJECTS FOR BEGINNERS \$7.75 F.G. RAYER, T.Eng.(CEI), Assoc.IERE

Another book written by the very experienced author — Mr. F.G. Rayer — and in it the newcomer to electronics, will find a wide range of easily made projects. Also, there are a considerable number of actual component and wiring layouts, to aid the beginner.

Furthermore, a number of projects have been arranged so that they can be constructed without any need for soldering and, thus, avoid the need for a soldering iron.

Also, many of the later projects can be built along the lines as those in the 'No Soldering' section so this may considerably increase the scope of projects which the newcomer can build and use.

### 221: 28 TESTED TRANSISTOR PROJECTS \$5.00 R.TORRENS

Mr. Richard Torrens is a well experienced electronics development engineer and has designed, developed, built and tested the many useful and interesting circuits included in this book. The projects themselves can be split down into simpler building blocks, which are shown separated by boxes in the circuits for ease of description, and also to enable any reader who wishes to combine boxes from different projects to realise ideas of his own.

### BP71: ELECTRONIC HOUSEHOLD PROJECTS \$7.20 R.A. PENFOLD

Some of the most useful and popular electronic construction projects are those that can be used in or around the home. The circuits range from such things as '2 Tone Door Buzzer', Intercom, through Smoke or Gas Detectors to Baby and Freezer Alarms.

See order form in this issue.



# Electronics Today Bookshelf

## BP49: POPULAR ELECTRONIC PROJECTS \$7.75 R.A. PENFOLD

Includes a collection of the most popular types of circuits and projects which, we feel sure, will provide a number of designs to interest most electronics constructors. The projects selected cover a very wide range and are divided into four basic types: Radio Projects, Audio Projects, Household Projects and Test Equipment.

## BP94: ELECTRONIC PROJECTS FOR CARS AND BOATS \$7.60 R.A. PENFOLD

Projects, fifteen in all, which use a 12V supply are the basis of this book. Included are projects on Windscreen Wiper Control, Courtesy Light Delay, Battery Monitor, Cassette Power Supply, Lights Timer, Vehicle Immobiliser, Gas and Smoke Alarm, Depth Warning and Shaver Inverter.

## BP95: MODEL RAILWAY PROJECTS \$7.60

Electronic projects for model railways are fairly recent and have made possible an amazing degree of realism. The projects covered include controllers, signals and sound effects: striboard layouts are provided for each project.

## BP93: ELECTRONIC TIMER PROJECTS \$7.60 F.G. RAYER

Windscreen wiper delay, darkroom timer and metronome projects are included. Some of the more complex circuits are made up from simpler sub-circuits which are dealt with individually.

## BP113: 30 Solderless Breadboard Projects-Book 2 \$8.85 R.A. Penfold

A companion to BP107. Describes a variety of projects that can be built on plug-in breadboards using CMOS logic IC's. Each project contains a schematic, parts list and operational notes.

## BP104: Electronic Science Projects \$8.85 Owen Bishop

Contains 12 electronic projects with a strong scientific flavour. Includes Simple Colour Temperature Meter, Infra-Red Laser, Electronic clock regulated by a resonating spring, a Scope with a solid state display, pH meter and electrocardiograph.

## BP110: HOW TO GET YOUR ELECTRONIC PROJECTS WORKING \$7.60 R.A. PENFOLD

We have all built circuits from magazines and books only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.

## BP84: DIGITAL IC PROJECTS \$7.60 F.G. RAYER, T.Eng.(CEI), Assoc. IERE

This book contains both simple and more advanced projects and it is hoped that these will be found of help to the reader developing a knowledge of the workings of digital circuits. To help the newcomer to the hobby the author has included a number of board layouts and wiring diagrams. Also the more ambitious projects can be built and tested section by section and this should help avoid or correct faults that could otherwise be troublesome. An ideal book for both beginner and more advanced enthusiast alike.

## BP67: COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS \$7.05 F.G. RAYER, T.Eng.(CEI), Assoc. IERE

Numeral indicating devices have come very much to the forefront in recent years and will, undoubtedly, find increasing applications in all sorts of equipment. With present day integrated circuits, it is easy to count, divide and display numerically the electrical pulses obtained from a great range of driver circuits.

In this book many applications and projects using various types of numeral displays, popular counter and driver IC's etc. are considered.

## BP99: MINI - MATRIX BOARD PROJECTS \$7.60 R.A. PENFOLD

Twenty useful projects which can all be built on a 24 x 10 hole matrix board with copper strips. Includes Doorbuzzer, Low-voltage Alarm, AM Radio, Signal Generator, Projector Timer, Guitar Headphone Amp, Transistor Checker and more.

## BP103: MULTI-CIRCUIT BOARD PROJECTS \$7.60 R.A. PENFOLD

This book allows the reader to build 21 fairly simple electronic projects, all of which may be constructed on the same printed circuit board. Wherever possible, the same components have been used in each design so that with a relatively small number of components and hence low cost, it is possible to make any one of the projects or by re-using the components and P.C.B. all of the projects.

## BP107: 30 SOLDERLESS BREADBOARD PROJECTS - BOOK 1 \$8.85 R.A. PENFOLD

A "Solderless Breadboard" is simply a special board on which electronic circuits can be built and tested. The components used are just plugged in and unplugged as desired. The 30 projects featured in this book have been specially designed to be built on a "Verobloc" breadboard. Wherever possible the components used are common to several projects, hence with only a modest number of reasonably inexpensive components it is possible to build, in turn, every project shown.

## BP106: MODERN OP-AMP PROJECTS \$7.60 R.A. PENFOLD

Features a wide range of constructional projects which make use of op-amps including low-noise, low distortion, ultra-high input impedance, high slew-rate and high output current types.

## CIRCUITS

### How to Design Electronic Projects

#### BP127 \$8.95

Although information on standard circuit blocks is available, there is less information on combining these circuit parts together. This title does just that. Practical examples are used and each is analysed to show what each does and how to apply this to other designs.

### Audio Amplifier Construction

#### BP122 \$8.95

A wide circuits is given, from low noise microphone and tape head preamps to a 100W MOSFET type. There is also the circuit for 12V bridge amp giving 18W. Circuit board or strip-board layout are included. Most of the circuits are well within the capabilities for even those with limited experience.

### Electronic Circuits for Model Railways

#### BP213 \$4.50

Lots of circuits including three types of controllers including one with simulated inertia and one with high power. Signalling and lighting systems are discussed at length and the suppression of RF interference. There are also 4 "steam whistle" and "chuffer" circuits.

## BP80: POPULAR ELECTRONIC CIRCUITS - BOOK 1 \$7.75 R.A. PENFOLD

Another book by the very popular author, Mr. R.A. Penfold, who has designed and developed a large number of various circuits. These are grouped under the following general headings: Audio Circuits, Radio Circuits, Test Gear Circuits, Music Project Circuits, Household Project Circuits and Miscellaneous Circuits.

## BP98: POPULAR ELECTRONIC CIRCUITS, BOOK 2 \$8.85 R.A. PENFOLD

70 plus circuits based on modern components aimed at those with some experience.

## BP39: 50 (FET) FIELD EFFECT TRANSISTOR PROJECTS \$6.75 F.G. RAYER, T.Eng.(CEI), Assoc. IERE

Field effect transistors (FETs), find application in a wide variety of circuits. The projects described here include radio frequency amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers and tone controls, as well as various miscellaneous devices which are useful in the home.

This book contains something of particular interest for every class of enthusiast - short wave listener, radio amateur, experimenter or audio devotee.

## BP87: SIMPLE L.E.D. CIRCUITS \$5.40 R.N. SOAR

Since it first appeared in 1977, Mr. R.N. Soar's book has proved very popular. The author has developed a further range of circuits and these are included in Book 2. Projects include a Transistor Tester, Various Voltage Regulators, Testers and so on.

## BP42: 50 SIMPLE L.E.D. CIRCUITS \$5.75 R.N. SOAR

The author of this book, Mr. R.N. Soar, has compiled 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components - the Light Emitting Diode (L.E.D.). A useful book for the library of both beginner and more advanced enthusiast alike.

### THE ACTIVE FILTER HANDBOOK

#### TAB No.1133 \$13.95

Whatever your field - computing, communications, audio, electronic music or whatever - you will find this book the ideal reference for active filter design.

The book introduces filters and their uses. The basic math is discussed so that the reader can tell where all design equations come from. The book also presents many practical circuits including a graphic equalizer, computer tape interface and more.

## MASTER HANDBOOK OF 1001 PRACTICAL CIRCUITS \$26.50 TAB No.800

## MASTER HANDBOOK OF 1001 MORE PRACTICAL CIRCUITS \$23.95 TAB No.804

Here are transistor and IC circuits for just about any application you might have. An ideal source book for the engineer, technician or hobbyist. Circuits are classified according to function, and all sections appear in alphabetical order.

## BP88: HOW TO USE OP AMPS \$8.85 E.A. PARR

A designer's guide covering several op amps, serving as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible.

## BP65: SINGLE IC PROJECTS \$6.05 R.A. PENFOLD

There is now a vast range of ICs available to the amateur market, the majority of which are not necessarily designed for use in a single application and can offer unlimited possibilities. All the projects contained in this book are simple to construct and are based on a single IC. A few projects employ one or two transistors in addition to an IC but in most cases the IC is the only active device used.

## BP117: PRACTICAL ELECTRONIC BUILDING BLOCKS BOOK 1 \$7.60

Virtually any electronic circuit will be found to consist of a number of distinct stages when analysed. Some circuits inevitably have unusual stages using specialised circuitry, but in most cases circuits are built up from building blocks of standard types.

This book is designed to aid electronics enthusiasts who like to experiment with circuits and produce their own projects rather than simply follow published project designs.

The circuits for a number of useful building blocks are included in this book. Where relevant, details of how to change the parameters of each circuit are given so that they can easily be modified to suit individual requirements.

## 223: 50 PROJECTS USING IC CA3130 \$5.00 R.A. PENFOLD

In this book, the author has designed and developed a number of interesting and useful projects which are divided into five general categories: I - Audio Projects II - R.F. Projects III - Test Equipment IV - Household Projects V - Miscellaneous Projects.

## 224: 50 CMOS IC PROJECTS \$5.25 R.A. PENFOLD

CMOS IC's are probably the most versatile range of digital devices for use by the amateur enthusiast. They are suitable for an extraordinary wide range of applications and are also some of the most inexpensive and easily available types of IC.

Mr. R.A. Penfold has designed and developed a number of interesting and useful projects which are divided into four general categories: I - Multivibrators II - Amplifiers and Oscillators III - Trigger Devices IV - Special Devices.

## THE MASTER IC COOKBOOK \$17.95 TAB No.1199

If you've ever tried to find specs for a so called 'standard' chip, then you'll appreciate this book. C.L. Hallmark has compiled specs and pinout for most types of ICs that you'd ever want to use.

## BP118: PRACTICAL ELECTRONIC BUILDING BLOCKS - Book 2 \$7.60 R.A. PENFOLD

This sequel to BP117 is written to help the reader create and experiment with his own circuits by combining standard type circuit building blocks. Circuits concerned with generating signals were covered in Book 1, this one deals with processing signals. Amplifiers and filters account for most of the book but comparators, Schmitt triggers and other circuits are covered.

## BP24: 50 PROJECTS USING IC741 \$6.75 RUDI & UWE REDMER

This book, originally published in Germany by TOPP, has achieved phenomenal sales on the Continent and Babani decided, in view of the fact that the integrated circuit used in this book is inexpensive to buy, to make this unique book available to the English speaking reader. Translated from the original German with copious notes, data and circuitry, a "must" for everyone whatever their interest in electronics.

## BP83: VMOS PROJECTS \$7.70 R.A. PENFOLD

Although modern bipolar power transistors give excellent results in a wide range of applications, they are not without their drawbacks or limitations. This book will primarily be concerned with VMOS power FETs although power MOSFETs will be dealt with in the chapter on audio circuits. A number of varied and interesting projects are covered under the main headings of: Audio Circuits, Sound Generator Circuits, DC Control Circuits and Signal Control Circuits.

## BP50: IC LM3900 PROJECTS \$5.40 H.KYBETT, B.Sc., C.Eng.

The purpose of this book is to introduce the LM3900 to the Technician, Experimenter and the Hobbyist. It provides the groundwork for both simple and more advanced uses, and is more than just a collection of simple circuits or projects.

Simple basic working circuits are used to introduce this IC. The LM3900 can do much more than is shown here, this is just an introduction. Imagination is the only limitation with this useful and versatile device. But first the reader must know the basics and that is what this book is all about.

## ELECTRONIC DESING WITH OFF THE SHELF INTEGRATED CIRCUITS \$12.95 AB016

This practical handbook enables you to take advantage of the vast range of applications made possible by integrated circuits. The book tells how, in step by step fashion, to select components and how to combine them into functional electronic systems. If you want to stop being a "cookbook hobbyist", then this is the book for you.

See order form in this issue.



# Electronics Today Bookshelf

## RADIO AND COMMUNICATIONS

**BP96: CB PROJECTS** \$7.60  
**R.A. PENFOLD**  
 Projects include speech processor, aerial booster, cordless mike, aerial and harmonic filters, field strength meter, power supply, CB receiver and more.

**222: SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS** \$7.60  
**R.A. PENFOLD**  
 In this book, R.A. Penfold has designed and developed several modern solid state short wave receiver circuits that will give a fairly high level of performance, despite the fact that they use only relatively few and inexpensive components.

**BP91: AN INTRODUCTION TO RADIO DXing** \$7.60  
 This book is divided into two main sections one to amateur band reception, the other to broadcast bands. Advice is given to suitable equipment and techniques. A number of related constructional projects are described.

**BP105: AERIAL PROJECTS** \$7.60  
**R.A. PENFOLD**  
 The subject of aerials is vast but in this book the author has considered practical designs including active, loop and ferrite aerials, which give good performances and are reasonably simple and inexpensive to build. The complex theory and math of aerial design are avoided.

**BP125: 25 Simple Amateur Band Aerials** \$7.60  
**E.M. NOLL**  
 Starting from simple dipoles through beam, triangle and even mini-rhombics (made from TV masts and 400ft of wire) this title describes several simple and inexpensive aerials to construct yourself. A complete set of dimension table are included.

**BP46: RADIO CIRCUITS USING IC's** \$5.40  
**J.B. DANCE, M.Sc.**  
 This book describes integrated circuits and how they can be employed in receivers for the reception of either amplitude or frequency modulated signals. The chapter on amplitude modulated (a.m.) receivers will be of most interest to those who wish to receive distant stations at only moderate audio quality, while the chapter on frequency modulation (f.m.) receivers will appeal to those who desire high fidelity reception.

**BP92: ELECTRONICS SIMPLIFIED—CRYSTAL SET CONSTRUCTION** \$6.80  
**F.A. WILSON**  
 Aimed at those who want to get into construction without much theoretical study. Homewound coils are used and all projects are very inexpensive to build.

**BP70: TRANSISTOR RADIO FAULT-FINDING CHART** \$2.50  
**CHAS. E. MILLER**  
 Across the top of the chart will be found four rectangles containing brief descriptions of various faults; viz. — sound weak but undistorted; set dead; sound low or distorted and background noises. One then selects the most appropriate of these and following the arrows, carries out the suggested checks in sequence until the fault is cleared.

## AUDIO

**205: FIRST BOOK OF HI-FI LOUDSPEAKER ENCLOSURES** \$3.75  
**B.B. BABANI**  
 This book gives data for building most types of loudspeaker enclosure. Includes corner reflex, bass reflex, exponential horn, folded horn, tuned port, klipschorn labyrinth, tuned column, loaded port and multi speaker panoramic. Many clear diagrams for every construction showing the dimensions necessary.

**HOW TO BUILD A SMALL BUDGET RECORDING STUDIO FROM SCRATCH...** \$15.95  
**TAB No.1166**  
 The author, F. Alton Everest, has gotten studios together several times, and presents twelve complete, tested designs for a wide variety of applications. If all you own is a mono cassette recorder, you don't need this book. If you don't want your new four track to wind up sounding like one, though, you shouldn't be without it.

**BP51: ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING** \$7.75  
**M.K. BERRY**  
 Electronic music is the new music of the Twentieth Century. It plays a large part in "pop" and "rock" music and, in fact, there is scarcely a group without some sort of synthesiser or other effects generator.

This book sets out to show how electronic music can be made at home with the simplest and most inexpensive of equipment. It then describes how the sounds are generated and how these may be recorded to build up the final composition.

**BP81: ELECTRONIC SYNTHESIZER PROJECTS** \$6.80  
**M.K. BERRY**

One of the most fascinating and rewarding applications of electronics is in electronic music and there is hardly a group today without some sort of synthesiser or effects generator. Although an electronic synthesiser is quite a complex piece of electronic equipment, it can be broken down into much simpler units which may be built individually and these can then be used or assembled together to make a complete instrument.

**ELECTRONIC MUSIC SYNTHESIZERS** \$10.95  
**TAB No.1167**  
 If you're fascinated by the potential of electronics in the field of music, then this is the book for you. Included is data on synthesizers in general as well as particular models. There is also a chapter on the various accessories that are available.

## TEST EQUIPMENT

**BP75: ELECTRONIC TEST EQUIPMENT CONSTRUCTION** \$6.80  
**F.G. RAYER, T.Eng. (CEI), Assoc. IERE**  
 This book covers in detail the construction of a wide range of test equipment for both the Electronics Hobbyists and Radio Amateur. Included are projects ranging from an FET Amplified Voltmeter and Resistance Bridge to a Field Strength Indicator and Heterodyne Frequency Meter. Not only can the home constructor enjoy building the equipment but the finished projects can also be usefully utilised in the furtherance of his hobby.

**THE POWER SUPPLY HANDBOOK** \$15.95  
**TAB No.806**  
 A complete one stop reference for hobbyists and engineers. Contains high and low voltage power supplies of every conceivable type as well mobile and portable units.

## REFERENCE

**BP85: INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE** \$11.75  
**ADRIAN MICHAELS**

This book will help the reader to find possible substitutes for a popular user-orientated selection of modern transistors. Also shown are the material type, polarity, manufacturer selection of modern transistors. Also shown are the material type, polarity, manufacturer and use. The Equivalents are sub-divided into European, American and Japanese. The products of over 100 manufacturers are included. An essential addition to the library of all those interested in electronics, be they technicians, designers, engineers or hobbyists. Fantastic value for the amount of information it contains.

**BP108: INTERNATIONAL DIODE EQUIVALENTS GUIDE** \$8.95  
**ADRIAN MICHAELS**

This book is designed to help the user in finding possible substitutes for a large user orientated selection of the many different types of semiconductor diodes that are available today. Besides simple rectifier diodes also included are Zener diodes, LEDs, Diacs Triacs, Thyristors, Photo diodes and Display diodes.

**BP1: FIRST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES** \$5.75  
**B.B. BABANI**

This guide covers many thousands of transistors showing possible alternatives and equivalents. Covers transistors made in Great Britain, USA, Japan, Germany, France, Europe, Hong Kong, and includes types produced by more than 120 different manufacturers.

**BP14: SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES** \$6.75  
**B.B. BABANI**

The "First Book of Transistor Equivalents" has had to be reprinted 15 times. The "Second Book" produced in the same style as the first book, in no way duplicates any of the data presented in it. The "Second Book" contains only additional material and the two books complement each other and make available some of the most complete and extensive information in this field. The interchangeability data covers semiconductors manufactured in Great Britain, USA, Germany, France, Poland, Italy, East Germany, Belgium, Austria, Netherlands and many other countries.

**TOWER'S INTERNATIONAL OP-AMP LINEAR IC SELECTOR** \$17.95  
**TAB No.1216**  
 This book contains a wealth of useful data on over 5,000 Op-amps and linear ICs — both pinouts and essential characteristics. A comprehensive series of appendices contain information on specs, manufacturers, case outlines and so on.

**CMOS DATABOOK** \$12.50  
**TAB No.984**  
 There are several books around with this title, but most are just collections of manufacturers' data sheets. This one, by Bill Hunter, explains all the intricacies of this useful family of logic devices... the missing link in getting your own designs working properly. Highly recommended to anyone working with digital circuits.

See order form in this issue.

## ROBOTICS

**THE COMPLETE HANDBOOK OF ROBOTICS** \$15.95  
**TAB No.1071**

All the information you need to build a walking, talking mechanical friend appears in this book. Your robot can take many forms and various options — light, sound, and proximity sensors — are covered in depth.

**HOW TO BUILD YOUR OWN SELF PROGRAMMING ROBOT** \$13.95  
**TAB No.1241**

A practical guide on how to build a robot capable of learning how to adapt to a changing environment. The creature developed in the book, Rodney, is fully self programming. can develop theories to deal with situations and apply those theories in future circumstances.

**BUILD YOUR OWN WORKING ROBOT** \$10.95  
**TAB No.841**

Contains complete plans — mechanical, schematics, logic diagrams and wiring diagrams — for building Buster. Buster is a sophisticated experiment in cybernetics you can build in stages. There are two phases involved: first Buster is leashed led, dependent on his creator for guidance; the second phase makes Buster more independent and able to get out of tough situations.

## VIDEO

**BP100: AN INTRODUCTION TO VIDEO** \$7.60  
**D.K. MATHEWSON**

Presents in as non-technical a way as possible how a video recorder works and how to get the best out of it and its accessories. Among the items discussed are the pros and cons of the various systems, copying and editing, international tape exchange and understanding specifications.

**Tab1519: ALL ABOUT HOME SATELLITE TELEVISION** \$22.95  
 Covers such aspects as where to buy, problems in setting up your TVRO station and how to solve them, antenna siting and equipment selection.

**Tab1490: VIDEO CASSETTE RECORDERS: BUYING, USING AND MAINTAINING** \$14.95

A complete handbook for the video enthusiast. You'll learn about how the systems work and how to choose as well as take a technical look at the inside workings. There are also sections on making your own video recordings.

## MISCELLANEOUS

**PH255: COMPLETE GUIDE TO READING SCHEMATIC DIAGRAMS, 2nd Edition** \$11.95  
**J. DOUGLAS-YOUNG**

Packed with scores of easy-to-understand diagram and invaluable troubleshooting tips as well as a circuit finder chart and a new section on logic circuits.

**BP101: HOW TO IDENTIFY UNMARKED IC'S** \$2.75  
**K.H. RECORA**

Originally published as a feature in 'Radio Electronics', this chart shows how to record the particular signature of an unmarked IC using a test meter, this information can then be used with manufacturer's data to establish the application.

**BASIC TELEPHONE SWITCHING SYSTEMS**

**TALLEY** \$17.95  
**HB27**

The Revised Second Edition of this book, for trainee and engineer alike, includes updated statistical data on telephone stations, and new and improved signaling methods and switching techniques. It also includes E & M signaling interface for electronic central offices and automatic number identification methods used in step-by-step, panel and crossbar central offices.

**PH252: DIGITAL ICs: HOW THEY WORK AND HOW TO USE THEM** \$10.95  
**A. BARBER**

The dozens of illustrations included in this essential reference book will help explain time-saving test procedures, interpreting values, performing voltage measurements, and much more!

**AUDIO AND VIDEO INTERFERENCE CURES**

**KAHANER** \$8.95  
**HB21**

A practical work about interference causes and cures that affect TV, radio, hi-fi, CB, and other devices. Provides all the information needed to stop interference. Schematic wiring diagrams of filters for all types of receivers and transmitters are included. Also, it supplies simple filter diagrams to eliminate radio and TV interference caused by noisy home appliances, neon lights, motors, etc.

**BP121: How to Design and Make Your Own PCBs** \$7.60  
**R.A. Penfold**

The emphasis is on practical rather than theoretical techniques. Starts by giving simple methods of copying from magazines, carries on with photographic methods of producing PCBs and continues with layout design.



# A Look At the Memotech 512

An impressive new computer from a company best known for ZX peripherals.

---

by David Norman

---

MEMOTECH HAS served a long apprenticeship in the field of microcomputers as a manufacturer of high quality ZX81 peripherals, and now they are set to take a slice of the home and business market with the MTX 512.

If first impressions are important, then Memotech has scored highly — their product comes beautifully packed and presented. The micro itself is cased in black anodised aluminum and carries a total of 79 keys which have a crisp and positive feel to them. The power supply is a separate unit, equally stylish, and rated at 1A. All the usual cables and documentation are also contained.

## RAM

The MTX 512 is a 64K machine with expansion to 512K. There's no need to worry about shrinking user memory when you're in the graphics mode either; there's an extra 16K for the graphics alone and the graphics RAM is controlled by a separate video processor.

## Plenty Of Ports

The MTX is a wide computer — about 19 inches — so there is plenty of room along the back for a multitude of connectors. They are generally high quality sockets, but deeply recessed and therefore difficult to get at, though this won't matter if the machine is going to stay in one place most



of the time. There is a phono socket so that the sound output from the computer can be sent to a hi-fi. In normal use the sound channels, of which there are four, will pass through the television and can therefore be easily adjusted to the volume of your choice.

Monitor and printer outputs are present, as are two joystick ports which will accept the popular "Atari" type of joystick. All the important CPU signals are available on an edge connector,

though this is normally blanked off in the interests of safety (the machine's safety by the way, not the user's!) and two RS232 interfaces are available as an optional extra. As if this wasn't enough, there is also an uncommitted 8-bit I/O port on the PCB itself, just sitting there as a 16-way IC socket and waiting for the home constructor to pop in a 16-pin header on some ribbon cable so that the micro can start controlling various gadgets around the home.





## Up And Running

The DIN power supply connector was a very tight fit in its socket, but fortunately once it is in, there is no need to disconnect. Not only is there an illuminated switch on the power supply, but there is also a reset button on the computer to bring you out from all crashes, infinite loops and other software nightmares. It is just as well that there is a light on the power supply since the MTX runs silently, without hums or buzzes.

The display on a Hitachi 12 inch colour TV was steady and the colours true, though the TV did need retuning after a warm-up period of about half an hour. There was no "dot-crawl" on either stationary or moving characters. The format of the screen in character mode is 40 x 24 and in general the text is clear and of pleasing proportions. However, I didn't much care for the lower case 'g' so I used the GENPAT command to redefine it. Any character in the standard ASCII set (codes 32 to 127) can be redefined in this way, and you may also define 26 new characters (or graphics) for codes 128 to 154, and type most of them into the computer using the special function keys marked F1 to F8. In graphics mode there are 32 characters on a line, so there is more space between each character. You can use the keyboard to change the character set to Spanish or German, in which case the specialized European symbols occur in place of the English keyboard's square-brackets and so on.

All the video work is done by one chip, the Texas 9929. This is a standard Video Display Processing (VDP) chip capable of producing four display modes, 16 colours and up to 32 sprites, about which more will be said later. One possible source of complaint is that the leading character position in each line may be lost in the television margin. This is not noticeable at first, since the software places print statements a couple of spaces on from the beginning of a line. The general advice must be to try to buy a TV or monitor with a horizontal hold, accompanied by a plea to the manufacturers to

start putting these controls back onto their television sets!

## High Command

The MTX has 24K of ROM, so there is plenty of space for some powerful and sophisticated commands. The manual is a provisional version: it runs to 250 pages and contains a wealth of technical information, but even so it is evident that a more comprehensive manual or book will be necessary to enable the user to get the best out of this computer. The ROM contains the BASIC, an interactive language called NODDY and an Assembler/Disassembler with powerful debugging facilities. Also available are plug-in cartridges for the FORTH and Pascal languages. The MTX BASIC has extra commands to enable the user to handle colour, sound, graphics and sprites without recourse to PEEKs and POKEs (Commodore please note!) and it should please most people. You may be disappointed to see that PROCEDURES and DO . . . UNTIL constructions are missing, but on the other hand you should be pleased to find that syntax is checked at the time of entry, and that keywords may be entered in a shortened form.

## Assemble, Please

The assembler is called from BASIC, and it assembles the code in situ, as part of the BASIC listing. The assembler itself is fairly basic, but it is easy to use and to edit. Numbers may be entered in either hex or decimal, and addresses are printed out in hex. Address labels are obviously accepted, but labels equated to numeric values are not supported. Define Space and Define Byte (incorporating Define String) can be used, but Define Word is absent.

Table 1

CIRCLEDRAW	PLOT	ARC	LINE	ANGLE	VIEW
PHI.	SPRITE	MVSPR	ADISPR	CTLSPR	GENPAT

Table 1. The graphic and sprite group; powerful instructions for multi-level, highly mobile screen displays.

NODDY is a new language designed to simplify text handling. It has only 11 commands, but can be incorporated into BASIC in such a way that the two languages work together. Coupled with the MTX editing keys, it should take the drudgery out of creating programs with a large textual content. Applications are obviously going to suggest themselves in areas of the school curriculum, in the fast-training of personnel in commerce, and in adventure-game writing. Time will tell how useful NODDY will be, and Memotech are to be congratulated for incorporating it into their computer — it's an experiment on their part and a challenge for the software writers to make something of it.

PANEL calls up the front panel display and puts the user directly in control of the MTX monitor at machine code level. Basically it is a window looking in at the registers and memory locations of the computer and it is an invaluable aid to all users interested in writing and debugging program and control of I/O devices at machine code level.

Other interesting commands in this group are the COLOUR, PAPER, INK and ATTRIBUTES which set up the various colour and printing options: the CLOCK and TIMES which handle a real-time clock in hours, minutes and second format, and the SOUND command that passes either 3 or 7 parameters to the Texas 76489 sound chip.

## Sprites And Things

The graphics screen has a resolution of 256 x 192 pixels and the graphic commands are listed in Table 1. PLOT, LINE and CIRCLE are fairly standard point and line drawing commands, but there is also ANGLE, PHI, DRAW and ARC and these are used together to determine the direction of lines and patterns drawn in the style of LOGO's TURTLE graphics. The provisional manual gives short examples of how to handle these advanced graphics, and it is to be hoped that further instructions will be provided in the final version of the manual.




Rear view showing the vast assortment of connectors on the MTX 512.


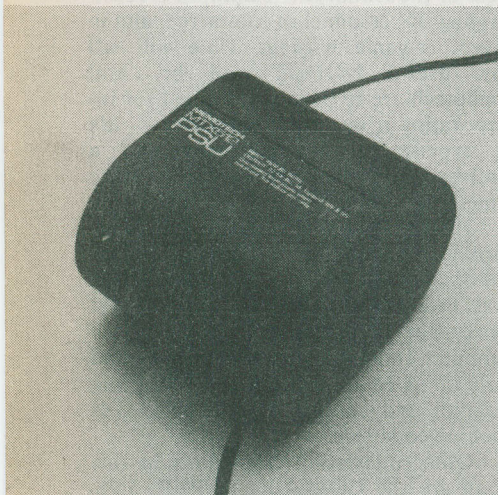
## Memotech 512

And so now to the Sprites: "Up to 32 independently controllable user definable sprites, plus pattern plane and backdrop plane" to quote the specifications, but what exactly does this mean? Think of the TV screen as a drawing board with a small piece of paper on it. The paper represents the physical size of the video screen, 256 x 192 pixels and can be a colour of your choice. This is the "backdrop-plane".



The Memotech power supply


Onto that paper, that screen, goes the text and/or graphics shapes in any ink colour you choose. This is the "pattern-plane". Consider the paper and the ink as a landscape. Now imagine a large piece of cellophane, 8192 x 8192 pixels in size, on which you have placed a small object called a sprite. The cellophane is your "sprite-plane". You can see the landscape beneath the cellophane, except where the sprite obscures it. Furthermore, you can move the sprite across the cellophane (with sprite) relative to the landscape. Finally, imagine that you could have up to thirty-two separate sheets of cellophane all piled on top of the landscape, and each with a moving sprite on it. That's how sprites help to achieve animation effects, and the commands such as MVSPR (move sprite) and CTLSPR (control sprite) help to set up the operating conditions. Once set, the sprites move around independently of the BASIC program, until such time as their parameters are altered. Collision between sprites are detected, and can be checked on by a PEEK to a register in the VDP chip.

### Conclusion

The MTX 512 is a well designed and carefully constructed machine which is

well worth the \$945 asking price. It seems to be suitable for both the home and educational markets, as well as novices and experts alike.

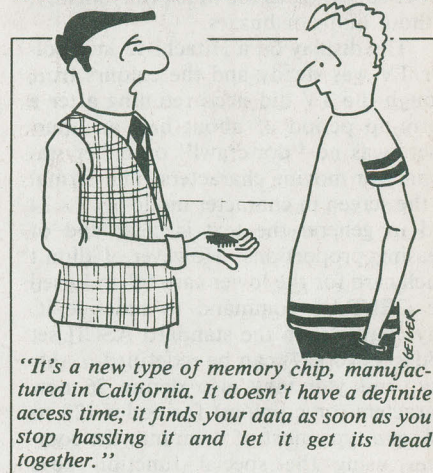The Memotech MTX 512 is available from Gladstone Electronics Supply Co., 1736 Avenue Rd., Toronto, Ontario M5M 3Y7 (416) 787-1448. The distributor for the MTX 512 is EDG Electronic Distributors Inc., 3950 Chesswood Ave., Toronto, Ontario, M3J 2W6 (416) 636-9404 Telex 06-219798. **ETI**



## Circuit Ideas continued from page 46

### DC Lamp Dimmer

The IC which controls the switching is the well known 555 timer, which is intended for monostable or oscillator applications.

Its main internal functions comprise a flip-flop, and two comparators, which can set the flip-flop (and hence the output) into either state. The comparators

switch at one third and two thirds of the supply voltage, but this can be modified by the control voltage input, and thus in this application can change the mark to space ratio.

It can in fact be varied from full on to completely off — though being on for two thirds of the time seems to be a typical setting required.

The FET used requires less than 0V8 on its gate to guarantee turn off — no problem for the 555 IC which is guaranteed to pull down to 0V25.

The circuit can handle lamps up to about 10 watts in size.

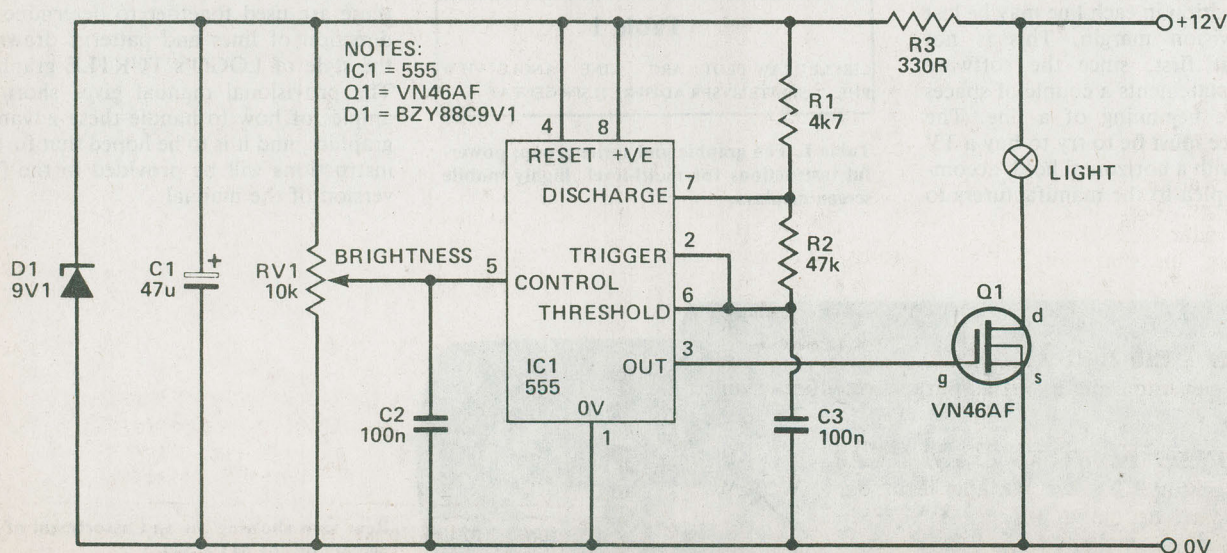


Fig. 1. The circuit. The dimming is obtained by a rapid switching of the lamp, controlled by the 555 timer.

**ETI**



which it loses when turned off, or on EPROM, so it can remember when it wakes up). As its experience grows, the RB5X develops rankings or levels of confidence in each of its possible responses. Eventually, the RB5X creates a range of appropriate learned responses to all of the circumstances it encounters in a room.

As well as moving and lifting and carrying, the RB5X has a number of capabilities that the other robots of the home variety can't do. For example, it has a fully resident voice recognition capability whereby the robot can hear and understands your words and respond either with information or with an action. It has the ability for radio communications whereby it can communicate through a modem to a remote computer, to a computer in the same room, directly to another robot, or to a security device. That means that the robot can teach another robot what it has learned, or, it can be programmed to patrol an environment (one's home) and detect intruders or a fire, transmit the information to the police or fire department, and raise an alarm. In the realm of navigation, the robot can be provided with an on-board compass such that no matter what direction it faces it will know where it is, or alternatively, a rotating sonar sensor enables the robot to scan the environment, compare the readings with prior knowledge, determine where it is, and via the compass, determine in which direction it is to move. As a continuation of the security aspects of the robot, it can be fitted with a fire detector and extinguisher. It can sense both temperature and the rate of change of the temperature. For example, it can tell the difference between a person or an animal walking by (simple body warmth), a stove turned on for cooking (relatively hot but unchanging) or a fire (very hot and getting hotter). It then is capable of raising an alarm (siren, lights) and via a cartridge carried in a dolly pulled behind it, detect where the hottest portion of the fire is, point the nozzle and release a blast of pressurized CO<sub>2</sub> at the base of the fire. This either extinguishes it, or delays its spread until humans can show up and deal with it themselves. And lastly, it can do the vacuuming via a device mounted on a dolly pulled behind it. As for doing widows, have patience; they're working on it. (The problem is reach — RB5X is too short).

There are also programs to teach, via TinyBASIC, such things as physics (interaction of sensors, etc.) and mathematics (patterns and geometry); it can be programmed to bring one the mail, water the plants, take the kid for a ride in the dolly, and at least in one publicity photo, take the dog for a walk (though I don't think this author's 85 pound pooch would take too kindly to that idea).

Essentially, then, for an assembled base price of roughly \$2,300, the RB5X

comes about as close to a real life R2D2 as can currently be found.


What then of the future? It's all well and good for companies like RB Robots to develop production models that can do things, but nonetheless home/hobby robotics are still firmly stuck in the position that microcomputers were six or seven years ago; the technology is there, but the uses still have to be developed by the home hobbyist. Fortunately, there are a number of companies that directly or indirectly recognize this, and are attempting to provide the home robotics person with parts and systems that can be amalgamated into working devices. As such, there are a number of areas to be covered: information processing, sensing, mobility, grippers, and education.

In the realm of information processing, or controllers, there are a number of companies: Cybernetic Micro Systems with its CY500 Stored Program Stepper Motor Controller, HHS Microcontroller's R8E Microcontroller, and so on. To delve into their capabilities is redundant. Their addresses are found at the end of this article.

In the realm of sensing there are also a number of companies, though basically one three will be mentioned here. The Votrax Inc. company manufactures a personal speech system which is about as good as one gets. The Ezra C. Lundal Inc. Company manufactures a sonic ranging device designed as a distance sensing and control unit, as well as a distance monitor device about the size of a packet of cigarettes. Perhaps the most versatile ranging device is Polaroid's Ultrasonic Ranging System developed for one of their cameras, and now used in a variety of applications, particularly robotic sensing systems. A run-down on what it does and how it does it can be found in this issue of ETI under 'Electronics in Action'.
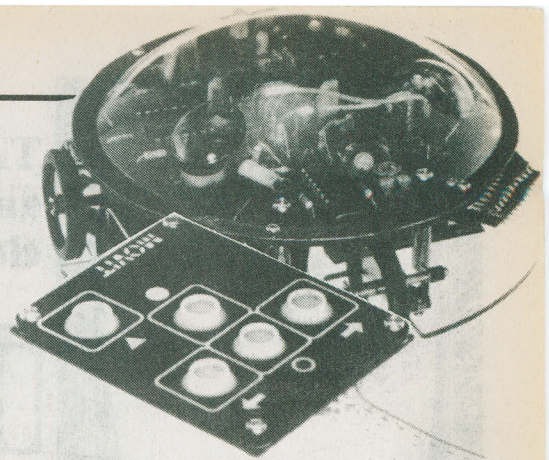
## Do It Yourself

Mobility can be handled one of two ways. One can purchase an off-the-shelf base, such as Hobby Robots RBU-IIT unit which can carry up to 275 pounds over flat terrain at 3 feet per second, though at \$1500 (US) a unit, it's a bit pricey. Far better to build one yourself. To that end Stock Drive Products in a veritable mother-lode for the robotics enthusiast via their *Handbook of Small Standardized Components* and their *Design and Application of Small Standardized Components*, which includes a 51 page robotics design section. This latter volume prefaces each section over the course of almost 800 pages with diagrams, descriptions and explanations dealing with small scale engineering; e.g., how to select the right gear, how many teeth should it have and why, etc. It's a superb quick course in small scale engineering with real life examples. It costs \$7.95 US. In combination with the other volume (730 pages,



The Memocon Crawler from MOVIT, designed in the turtle fashion, can be programmed from a five function keypad to perform basic robotic actions.

\$5.95 US) which contains every sort of little thing (24,000 different gears, bushings, pulleys, motors, whatever) this writer can safely say that no hobbyist dealing with matters mechanical could or even should try to design anything without possessing a copy.

In the realm of grippers, the MACK Corporation's 'low profile actuators' are about as good as they come. Primarily designed for industry, the smaller ones have application in robotics.

In the world of education, there are an increasing number of courses available for the would-be roboticist through community colleges and universities. However, they require attendance. Perhaps the best correspondence, self-tech program in robotics is the one offered by the Heathkit Company, costing \$150 (an industrial applications course in Robotics cost another \$150.) It covers almost everything and in combination with the Stock Drive Products' volumes, will set roboticists well on their way to success.


And finally, for those who want a quick taste of what the problems are and how to deal with them, the MACK Corporation has a free booklet, originally intended for internal use by their employees, entitled *Robotics . . . Start Simple*. It is a good introduction into what sort of problems the roboticist is likely to face and how to overcome them.

What then of the future? If the hobbyists get going, then perhaps the \$2 billion a year industry by the end of the decade will come about, and the indications are good that it will. After all, the speech synthesis device used by the RB5X was originally designed by 17-year-old Arnold Tang of Honolulu, Hawaii, and the RB5X's fire extinguisher mechanism was developed by Mark Turner while a student at the Golden High School in Golden, Colorado, and entered into the school's science fair where it (not surprisingly) took first place in the Engineering Division.

Just like the developments in microcomputers six years ago.

For selected addresses see page 10.



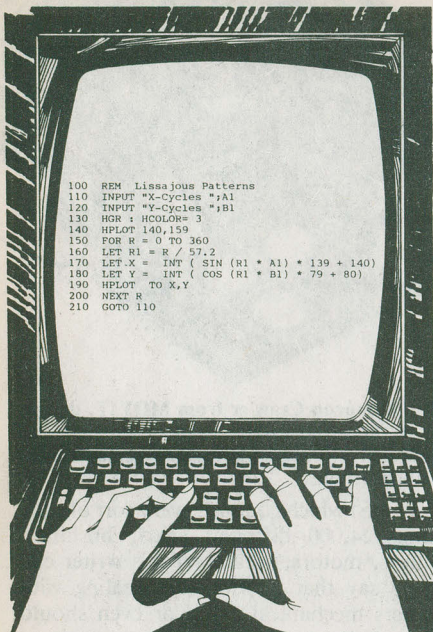

**Timekeeping: find Easter, print a calendar for any year, and try some graphics with an analog clock.**

# Computing Today

## Apple Listings by Anthony DeBoer

THE THREE programs presented here are concerned with the subject of time. Computers, with their ability to do math and follow complicated sets of rules, are well suited to figuring out times and dates. Consider, for example, the rules for leap years: every fourth year is a leap year, but every hundredth (1800, 1900, etc.) is not, except for every four hundredth (2000, for example), which is. Keeping track of a seven-day week through 365 and/or 366 day years is another interesting trick.

Of course, if you think that's complicated, you ain't seen nothing yet. Check out the rules for when Easter occurs: "the Sunday which follows the full moon which occurs on, or next after, the

day of the spring equinox." They don't figure these things out by throwing darts at a calendar, much as it may seem that way. You'll almost need a degree in astronomy to plan your spring vacation.

### The Silicon Solution

Starting off, we have a program that prints out calendars for any year of the Gregorian calendar. Although written in Applesoft BASIC, it could probably, with a bit of programming knowledge, be adapted to just about any other BASIC. It asks for a year and a month — enter zero for the month to get all twelve — and then prints up the calendar(s). A hardcopy option lets you print out the results.

The second program figures out when Easter Sunday falls in any given year or years. It asks for a starting year and an ending year, and then prints up a list of the dates on which Easter will fall in those years.

Third, we have a clock program. While it doesn't keep accurate time, it does show off the Apple's animated graphics capability (using both high-res screens) fairly well. It even makes nice mechanical clicking sounds as it goes around. Of the three, this is the only one that probably isn't worth trying to translate to another computer's BASIC, since it uses so much that is Apple-specific.

### Calendar

```
100 REM Calendar by Anthony DeBoer
110 DEF FN D(R) = (Y = (R * INT (Y / R)))
120 I$ = CHR$(124) + " "
130 DIM MN$(12): FOR N = 1 TO 12: READ MN$(N): NEXT
140 DATA JANUARY,FEBRUARY,MARCH,APRIL,MAY,JUNE,JULY,
    AUGUST,SEPTEMBER,OCTOBER,NOVEMBER,DECEMBER
150 TEXT : HOME : PRINT "Calendar": PRINT
160 INPUT "Year = ";Y: PRINT
170 INPUT "Month (0 for all year) = ";M
180 IF M < 0 OR M > 12 THEN 170
190 PRINT : PRINT "Hardcopy? ";
200 GET H$: IF H$ < > "Y" AND H$ < > "N" THEN 200
210 PRINT H$: IF H$ = "Y" THEN PRINT CHR$(4);"PR#1"
220 IF M > 0 THEN GOSUB 260: GOTO 240
230 FOR M = 1 TO 12: GOSUB 260: NEXT
240 IF H$ = "Y" THEN PRINT CHR$(4);"PR#0"
250 END
260 REM figure out what day the month starts on
270 D = Y:A = M - 2: IF A < 1 THEN A = A + 12:D = Y - 1
280 C = INT (D / 100):D = D - 100 * C
290 W = INT ((13 * A - 1) / 5)
300 Z = W + INT (C / 4) + INT (D / 4) + 1 + D - 2 * C
310 F = Z - 7 * INT (Z / 7)
320 REM figure out how many days in month
330 L = 28 + INT ((13 * A + 12) / 5) - W
340 IF M = 2 THEN L = 28 + FN D(4) - FN D(100) + FN D(400)
350 REM print calendar month
360 IF H$ = "N" THEN HOME
370 A$ = MN$(M) + " " + STR$(Y): HTAB 20 - LEN (A$)
380 FOR N = 1 TO LEN (A$): PRINT MID$(A$,N,1); " ";: NEXT
390 PRINT : PRINT
400 PRINT " SUN MON TUE WED THU FRI SAT": GOSUB 520
410 I = 0: IF F > 0 THEN FOR N = 1 TO F: GOSUB 460: NEXT
```

```
420 FOR I = 1 TO L: GOSUB 460: NEXT
430 IF D > 0 THEN I = 0: GOSUB 460: GOTO 430
440 IF H$ = "N" THEN GET A$
450 PRINT : PRINT : RETURN
460 REM print calendar cell
470 PRINT LEFT$(I$,5 - (I > 9) - (I > 0));
480 IF I > 0 THEN PRINT I;
490 D = D + 1: IF D < 7 THEN RETURN
500 PRINT LEFT$(I$,1)
510 PRINT I$;I$;I$;I$;I$;I$;I$; LEFT$(I$,1)
520 PRINT "+-----+-----+-----+-----+-----+"
530 D = 0: RETURN
```

DECEMBER 2001

SUN	MON	TUE	WED	THU	FRI	SAT
						1
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29
30	31					



## Easter Sunday

```

100 REM Easter Sunday
110 REM Adapted by Anthony DeBoer from a program by Noel Bailey
    from an algorithm by T. H. O'Beirne
120 PRINT
130 INPUT "FIRST YEAR = ";Y
140 INPUT "LAST YEAR = ";Z
150 PRINT
160 PRINT "EASTER SUNDAY"
170 PRINT "-----"
180 FOR X = Y TO Z
190 A = X - 19 * INT (X / 19); B = INT (X / 100); C = X - 100 * B;
    D = INT (B / 4); E = B - 4 * D; G = INT ((8 * B + 13) / 25)
200 Q = 19 * A + B - D - G + 15; H = Q - 30 * INT (Q / 30);
    I = INT (C / 4); K = C - 4 * I
210 Q = 2 * E + 2 * I - H - K + 32; L = Q - 7 * INT (Q / 7)
220 M = INT ((A + 11 * H + 19 * L) / 433); N = INT ((H + L - 7 * M
    + 90) / 25)
230 Q = H + L - 7 * M + 33 * N + 19; P = Q - 32 * INT (Q / 32)
240 M$ = " APRIL ": IF N = 3 THEN M$ = " MARCH "
250 PRINT P;M$;X
260 NEXT

```

FIRST YEAR = 1981  
LAST YEAR = 1990

## EASTER SUNDAY

-----  
19 APRIL 1981  
11 APRIL 1982  
3 APRIL 1983  
22 APRIL 1984  
7 APRIL 1985  
30 MARCH 1986  
19 APRIL 1987  
3 APRIL 1988  
26 MARCH 1989  
15 APRIL 1990


## Clock

```

100 REM Clock by Anthony DeBoer
110 DIM C(59),S(59)
120 PI = 3.1415927
130 T = PI / 30: FOR N = 0 TO 59: X = N * T: C(N) = COS (X):
    S(N) = SIN (X): NEXT
140 HGR : HGR2 : HCOLOR= 3
150 TI = 1: TM = 0: TP = 60
160 TF = 3: NT = 9 / 10
170 SP = 49200: S = 0
180 POKE (49236 + S),0
190 POKE 230,(64 - 32 * S)
200 CALL - 3086
210 GOSUB 390
220 REM Do clock face
230 FOR T = 0 TO 59 STEP 5: R = 90: GOSUB 310: HPLLOT X,Y: R = 80:
    GOSUB 310: HPLLOT X,Y: NEXT
240 REM Do minute hand
250 HR = 90: HT = TM: GOSUB 340
260 REM Do hour hand
270 HR = 60: HT = INT (TM / 12): GOSUB 340
280 GOSUB 390
290 TM = TM + TI
300 S = 1 - S: GOTO 180
310 IF T >= TP THEN T = T - TP
320 IF T < 0 THEN T = T + TP
330 X = R * S(T) + 140: Y = 96 - R * C(T): RETURN
340 HPLLOT 140,96: SR = HR / 3
350 R = SR: T = HT - TF: GOSUB 310: HPLLOT TO X,Y
360 R = HR: T = HT: GOSUB 310: HPLLOT TO X,Y
370 R = SR: T = HT + TF: GOSUB 310: HPLLOT TO X,Y
380 HPLLOT TO 140,96: RETURN
390 REM Click speaker
400 QV = PEEK (SP) + PEEK (SP): RETURN

```

The clock  
at 12:03

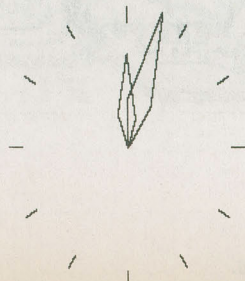

ETI

DON'T JUST THINK ABOUT IT  
-DO IT!



PARTICIPATION

## APDIAL The Terminal Program for Apple CP/M Users

If you use an Apple compatible system under CP/M, you will probably have found that communications software for your computer is a bit scarce. At best, you can get very savagely stripped down versions of other CP/M terminals, which offer limited facilities.

There's a small purple dragon in your computer crying out for APDIAL.

APDIAL is a complete terminal package which can either stand alone or act as a front end for a protocol transfer system, like MODEM7. Among its features are:

- Written in machine code for blinding speed.
- Dials, waits for carrier and can autoloop if the line is busy.
- Automatically drops into terminal mode if it gets a carrier.
- Has an internal menu driven phone number library.
- Written for the Apple... APDIAL is not hacked from other software.
- Can boot MODEM7 or another file transfer program automatically.

The APDIAL disk comes with both a COM file and an extensively commented source file which can be assembled with ASM or MAC. It comes configured for the low cost PDA 232C card, although users with even a rudimentary knowledge of assembler can change a few equates in the source and adapt it for any of the popular communications cards.

APDIAL costs \$19.95, which includes postage, packing and a brand new, high quality disk. Ontario residents please add 7%.

Electronics Today Software  
25 Overlea Boulevard, Suite 601  
Toronto, Ontario  
M4H 1B1



# Servo Interface



**Looking for something useful to do with those servos you threw in the back of the closet? Why not interface them to the ZX81 (or other favourite micro) and get them to do some work around the house.**

**by Rory Holmes**

THE SERVO interface is built on a single-sided PCB. An additional double-sided PCB is used to make a lead-through type of edge connector plug, similar to that used on the ZX printer. The interface electronics are too bulky to be mounted directly on the Sinclair edge-connector, but our small Verobox-enclosed plug, wired to the main board via ribbon cable, puts less strain on the expansion connector. Although this interface has been designed for use on the ZX81, real adventurers can modify it for use on just about any other micro with accessible I/O ports.

Start construction with the main PCB, soldering in the links and resistors first (there should be eight links altogether), followed by the IC sockets and other components. Insert Veropin terminals at all the computer bus connections, since this makes wiring up to the ribbon cable easier. Veropins, or a five-way Molex connector socket should also be used at the servo output terminals as illustrated on the PCB overlay diagram of Fig. 1.

The double-sided board is really an extender to allow the use of peripheral connectors. If you don't need the peripherals, you can substitute a suitable connector and wire the ribbon cable to it. If you need the PCB, it's easy to make up with the paint-and-etch method, or you can use the self-adhesive foil patterns available commercially.

## Adjust Your Address

The three DIL switches can be replaced by appropriate wire links if the address combination that you wish to use is going to be a permanent fixture. The address selection details given below should be studied to appreciate the possible configurations of the address decoder. Observe that the two switches corresponding to the Z80 control lines (those nearest C4), would

always be set to logic low, i.e., closed. Also note that IC3 is positioned the other way round to the other ICs.

## Pot Luck

The edge connector PCB is cut to exactly fit into the smallest Vero potting box. By a lucky coincidence, the 23-way Sinclair expansion bus will exactly fit the inside of this box. The solder tags on the edge socket are spaced wider apart than the PCB thickness and must be adjusted slightly — don't forget the keyway orientation shown in the wiring layout. One row of tags should first be soldered as they are to the 'underside' PCB terminals and then the other row can be bent down to reach the topside terminals, allowing the assembly to fit in the Verobox.

Figure 3 shows how slots should be cut in the box to house the edge connector

plug and socket. Two large size stick-on rubber feet should be positioned on the inside of the lid to hold the board firmly in place as the lid is screwed down. If one of the feet is stuck above the ribbon cable entry point, it will act as a cable clamp. A very neat and solid connector system will result from this construction method.

## Address Selection

With the ZX81, IC8 and 9 must be fitted while IC7 is optional, depending on the degree of address decoding required. Jumper links JB and JC should be fitted, but not link JA. The memory map given in part 1 showed the address line logic levels needed to decode different address ranges. These logic levels are set on the switches to decode the required addresses for the servo locations.

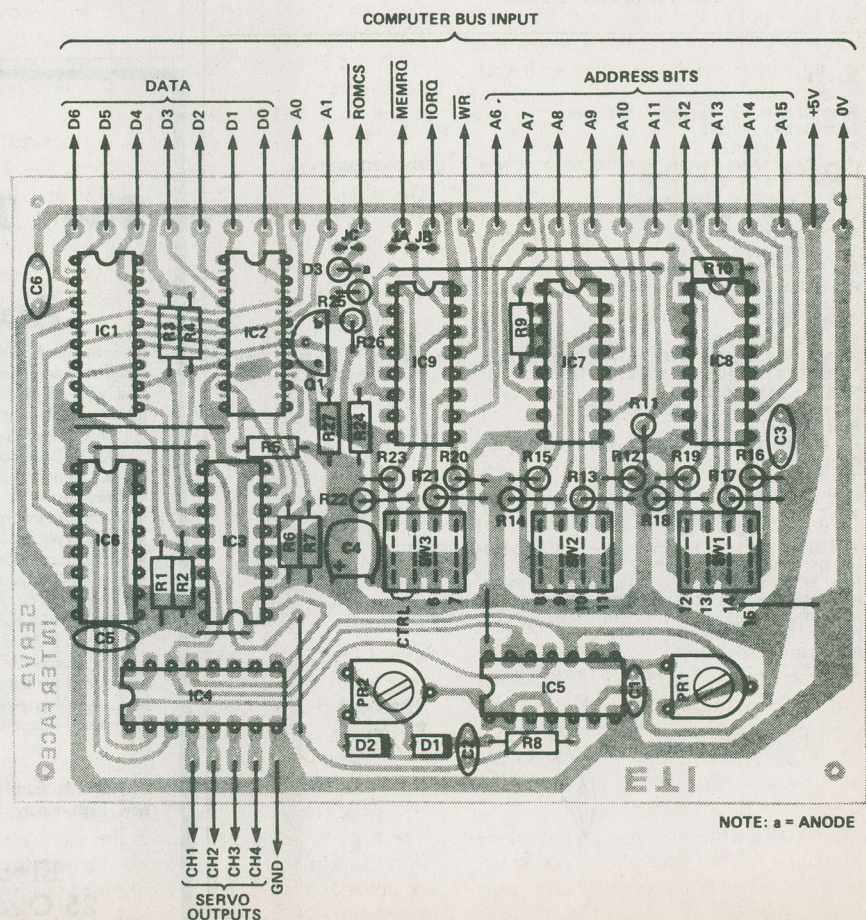


Fig. 1. Overlay for the servo arm interface board.



the instruction would mean: load the A register with the two byte number pq; two into one won't go! To get the number in the A register into the address pq, the instruction in the Z80 set is 32 — **LD (pq), A**.

This mode of addressing need not be restricted to a single register; a Z80 example is 2A — **LD HL, (pa)**, where the byte is pq is loaded into L and the byte in pa + 1 is put into H. If you forget which byte goes where, just remember H for high (byte), and L for low; using the DE pair, the high byte will go into register D.

**FIRST STEP:** divide decimal address by 16  
 1,875  
 16 | 30,000 remainder 0 = 0 x units  
**SECOND STEP:** divide this by 16  
 117  
 16 | 1,875 remainder 3 = 3 x 16  
**THIRD STEP:** divide again by 16  
 7  
 16 | 117 remainder 5 = 5 x 16  
 As the result is less than 16, we stop therefore 30,000 decimal = 7530 hexadecimal

Fig. 8 One way of converting decimal to hex.

Those of you with Sinclair micros may have noticed, in the manual appendix dealing with the character set, the words 'after ED' or 'after CB' etc. This is where a four byte absolute instruction may be found and is explained as follows. The instruction 4B in the Z80 set means **LdC, E**, but after ED means **LD BC, (pq)**. Fig. 10 shows how this is used in a program. The use of ED and CB, etc., is very similar in principle to the use of shift keys, where one key with shift has a different function to the unshifted version.

## A Direct Extension

This section should explain, in part at least, some of the differences in terminology that I mentioned earlier. In one book I read, the author gave an example of absolute addressing, using 3A — **LD A, (pq)** for the Z80 set. He went on to say that this mode is sometimes called the direct or extended mode. As the 6800 set uses both of those modes I'll give a couple of examples.

In the direct mode, the instruction 96h is concerned with loading the accumulator with the byte held in an address, but there is only one byte used for the address. This is because the high byte of the address is supplied by the computer automatically and the byte is 00. So when the computer meets the instruction 96 FF, it interprets it as meaning **Ld A, (pq)**, where pq is 00FF. An example of the extended form from the 6800 set is 87 — **LD (pq), A** where the two bytes pq must be put in by the programmer. As a last example, I'll use the 8085 set; in that set 3A — **Ld A, (pq)** is considered as being in the direct mode.

Now for a little bit more explanation of terminology. That 6800 direct mode example I gave above is sometimes called *zero page addressing*, or sometimes, *abbreviated absolute form*. No matter what it is called, it still works in the manner that I

have described. Those of you with a 6502 can use zero page addressing, which simply means the first page (of RAM) runs from addresses 0000 to 00FF. All you have to do as a programmer is specify the low byte of the address from 00 to FF, and the computer adds the 00 automatically, as already explained. Now you can see that it does help to know how your computer has its memory mapped out. A computer that has ROM starting at address 0000 cannot use zero page addressing in the form **Ld (pq), A**, because you cannot write to ROM.

## Pop Goes The Weasel

In the instructions that I've already covered, the two bytes, pq, have been used as an address. Later on I will be giving addressing mode using pq as numbers, but for now more explanations. These explanations concern not only what has gone before, but what is yet to come. Firstly, let us recall the stack pointer register, SP, as we'll be looking at this in rather more detail.

As you will recall, the stack is a portion of RAM which the computer reserves for its own use, and, like the variables area, the size can fluctuate. The stack is used to store two byte addresses or numbers, either at the command of the programmer, or as part of a computer controlled sequence. Curiously, the stack is sort of upside down, with the latest piece of information going on top of the one before, which makes for a last in, first out, situation.

To help you understand the stack and the manipulation of pq, I am going to use two single-byte instructions. These are the **PUSH** and **POP**, or **PUSH** and **PULL** instructions. Because pq takes up two bytes push and pop concern register pairs. The Z80 set allows the push and pop of every register pair (see part one of this series) and also allows the A register to be paired with the flags register, F, for this purpose.

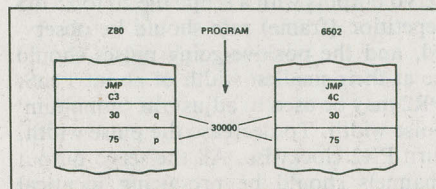


Fig. 9 Absolute jump instructions.

Don't be misled, though: the use of the AF pair allows only A to be loaded (with any number up to FFh), but you can't load the F register.

Using the HL pair to make things clear, the Z80 instruction EF — **PUSH HL** will store the contents of HL on the stack. See Fig. 10 while following the explanation. Supposing HL contained the number or address 30,000d or 7530h before the instruction E5 — **PUSH HL** was encountered by the program. On reaching E5 the stack pointer will be pointing to the

next empty address available on the stack. First the low byte in L is copied into that address. The stack pointer, sp, is then decremented (by one) and the high byte in H is copied into the new address pointed to by SP. The register is decremented again so that it is now pointing to the next available address.

The reverse happens on the pop instruction which, in the Z80 set is E1 — **POP HL**. This instruction will increment SP (by 1), the byte in the new address is copied into H; SP is incremented again, and the next byte goes into L. Now SP is pointing to the next available address on the stack.


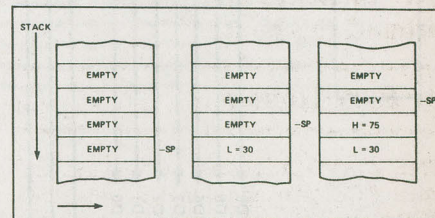


Fig. 10 Pushing the number 7530 hex in the HL pair.

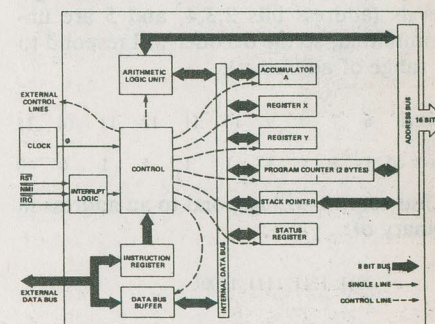The 6502 set allows the pushing and popping of only two single registers onto the stack. These are the accumulator and the status register; for example, 48 — **PHA** copies the contents of the accumulator onto the stack. Notice that I keep saying copies onto the stack: this is to emphasise the fact that pushing does not destroy the contents of registers.



The final couple of points will be of interest to Z80 users mainly. If you have pushed a sequence of register pairs onto the stack, before popping them off again remember that last in, first out rule. Having said that, what happens if you push HL then pop DE? With that question, we'll leave you next month.

ETI



## Servo Interface

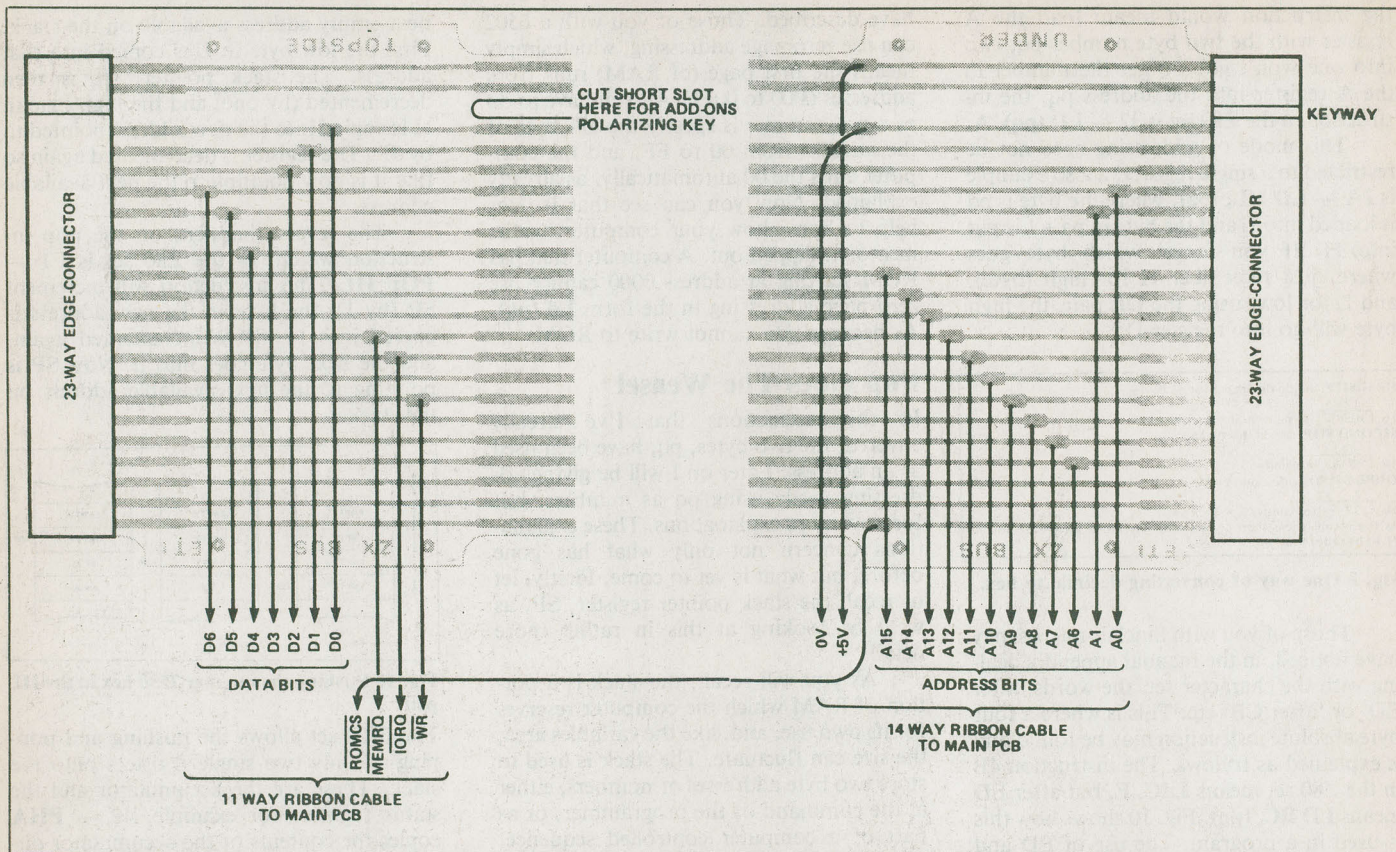


Fig. 2. Overlay for the edge connector PCB; this will allow the use of other peripherals. Ribbon cable with 14 ways and 11 ways is used, although one of the wires from the 11-way piece is soldered to the other side of the PCB as shown.

As an example, the switches on the PCB could be set to the following logic levels (address bits 2,3,4, and 5 are uncommitted, so the decoder will respond to a range of addresses):

switch	6	7	8	9	10	11	12	13	14	15
logic level	1	1	1	1	1	1	1	1	0	0

Thus servo 1 will respond to an address in binary of:

0011 1111 1111 1100  
or 3 F F C

in hexadecimal. In decimal this gives servo addresses of:

- Servo 1 POKE 16380, X
- Servo 2 POKE 16381, X
- Servo 3 POKE 16382, X
- Servo 4 POKE 16383, X

The servo 4 location is the highest byte of the second 8K block.

### Testing

Once all the cables are wired up, the interface can be tested by plugging in to the Sinclair expansion port. Ensure that the jumper links and IC/address switch combinations are set up, and start with no ICs plugged in. If the computer resets correctly and still seems to work, then the first hurdle is over. Check that the 5 V power

rail appears at all the IC sockets and then disconnect the interface to plug in all the ICs. With both presets at mid-travel, turn PR1 45° anti-clockwise and PR2 45° clockwise; this will give a suitable pulse width to start with.

Plug in the interface again, reset the computer, and write zeros (using either the POKE or OUT command) to your chosen servo locations. On checking the servo outputs with a scope the 20 to 25 mS repetition (frame) rate should be observed, and the positive-going pulses should be at their smallest width of about 1 mS. PR2 may be used to adjust the 'minimum' pulse width. To decrease the pulse width, turn PR2 clockwise. All the servo output channels should be producing identical pulse sizes, but with the appropriate phase lag according to the time slot where they occur.

Now, choosing a specific servo channel, observe the pulse output on a scope as the number 17 is written to this channel. The pulse width should shift to be about 2 mS, and this 'maximum' pulse width can be adjusted using PR1. If a servo is at hand it can be connected up as shown in the diagram of Fig. 4, whereupon it should immediately take up the position dictated by the pulse width. Different numbers can now be POKED to the servo to test a number of pulse positions.

### PARTS LIST

#### Resistors (all 1/4 W, 5%)

R1-8,25,26	10k
R9-23,27	3k3
R24	470R

#### Potentiometers

PR1	47k miniature horizontal preset
PR2	470k miniature horizontal preset

#### Capacitors

C1	470p ceramic
C2,3,6	10n ceramic
C4	47u 16 V tantalum
C5	100n ceramic

#### Semiconductors

IC1,2	74LS170
IC3	40103B
IC4	4555B
IC5	4093B
IC6	4520B
IC7-9	74LS85
Q1	2N5210
D1-3	1N4148

#### Miscellaneous

SW1-3	4-way single-pole DIL switches (wire links can be used)
-------	---

PCBs; 0.1" 23-way double-sided edge connector; 5-way Molex connector socket; Veropins; case for interface, size 146x91x23 mm; case for plug — general purpose Vero potting box; 14 and 11-way ribbon cable.



# Book of the Month

## Secrets of the Commodore 64


by P. Cornes &  
A. Cross

List Price \$9.50

Number BP135

## Secrets of the COMMODORE 64


P. CORNES & A. CROSS

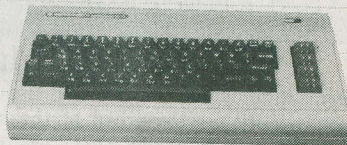


This is a book to supplement the instruction manual of the Commodore 64; it does a more thorough job of explaining how to use random numbers, POKes, sprites, input routines, sound, and machine code. The explanations include computer printouts to illustrate the functions.

Available from: Moorshead Publications 25 Overlea Blvd.  
Suite 601, Toronto, Ontario M4H 1B1 (416) 423-3262

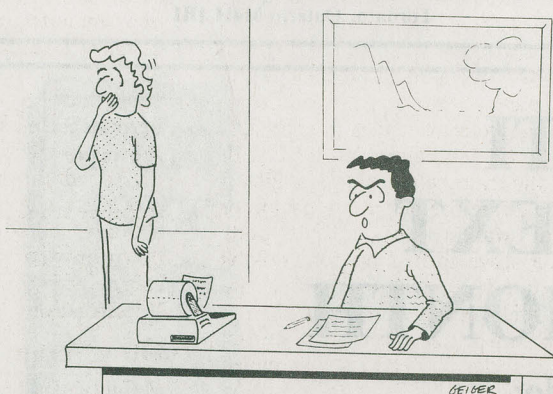See order form in this issue. All prices include shipping. No sales tax applies.




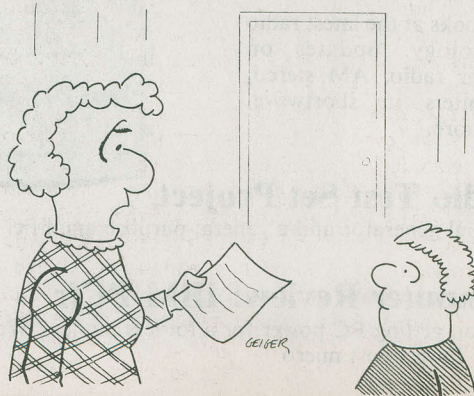"What's this roll of toilet paper doing in my adding machine, and where's my expensive calculator paper?"



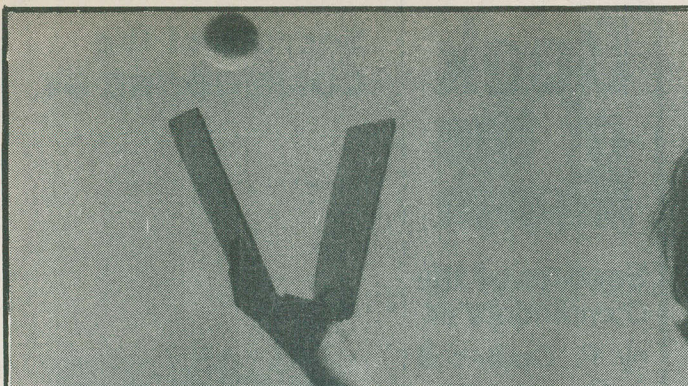"I think your father's been working with computers for too long. He left a message that says, 'IF I AM LATE, THEN STORE DINNER IN FRIDGE. ELSE GOTO OVEN AND HEAT DINNER. END.'"





### Catcher's Mitt/Magazine Binder

Ah, summertime. You've worn out the old mitt already with heavy duty service down at the sandlot, and it's time for a replacement. With just such a predicament in mind, we offer the ETI Catcher's Mitt.

Sturdily made from vinyl and chromed metal, it has been field-tested and is guaranteed to catch at least three out of ten balls if they're thrown into it slowly and carefully.

Rained out? Cold weather coming? We're ready for that, too. They also will hold 12 issues of Electronics Today; a diabolically clever spring arrangement holds the magazines without cutting or punching. In addition, for no extra charge, we print on the spine: Electronics Today, Computing Now!, or Moorshead Publications.


They're available postpaid for \$9.25 — don't forget to specify the one you want — and Ontario residents are required on pain of death to add 7% provincial sales tax. Send to:

**Moorshead Publications Binders**  
Suite 601, 25 Overlea Blvd.  
Toronto, Ontario M4H 1B1

## ETI NEXT MONTH
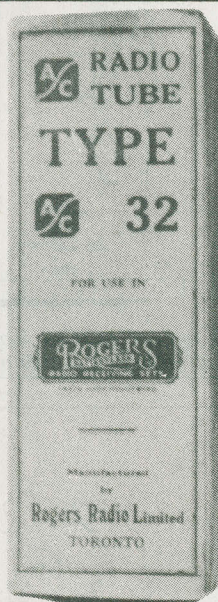
### Radio: What's Happening

ETI looks at the latest radio technology: updates on cellular radio, AM stereo, computers in shortwave, and more.



### Audio Test Set Project

A signal generator and a general-purpose amplifier in one.

### Computer Review: IBM PCjr


Are you getting PC power for a lot less money? We look at IBM's lowest-cost micro.

### RS232 Explained

We unravel the secrets of the RS232 computer communications standard.



# THE OEM COMPONENT LEADER SWITCHCRAFT®

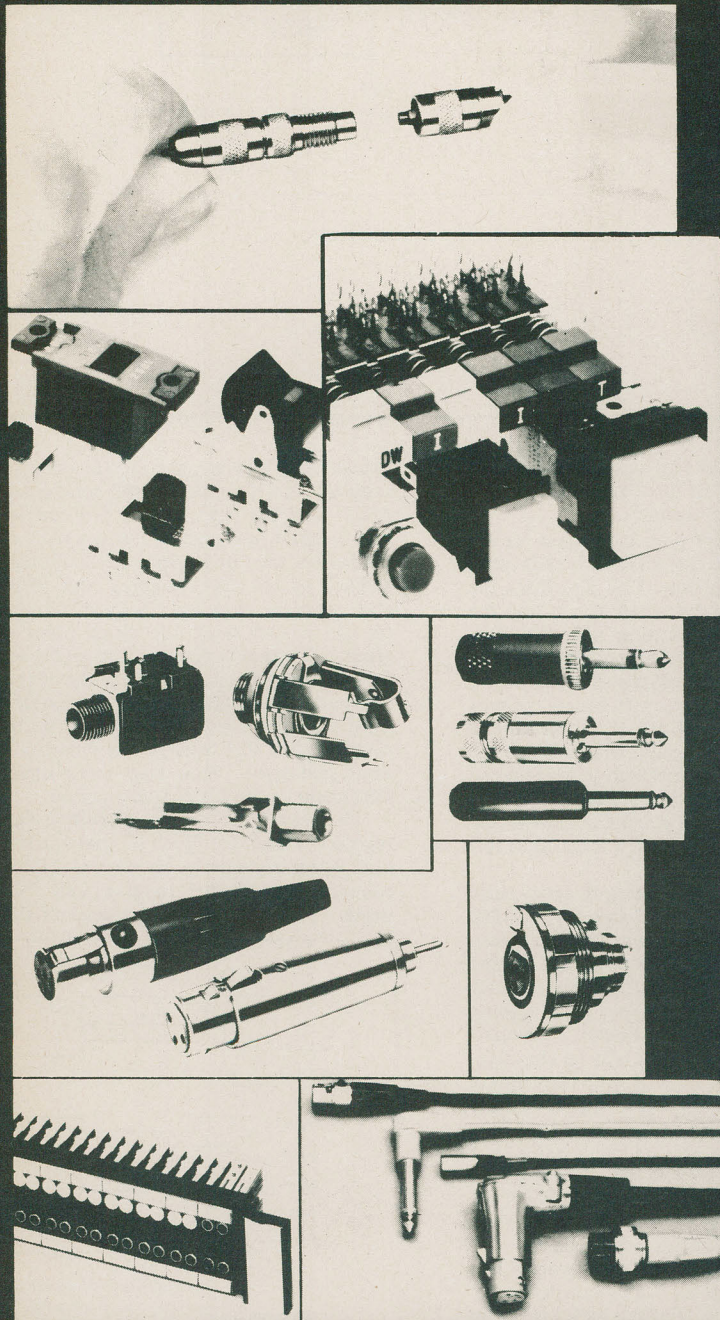

## HIGH TECHNOLOGY COMPONENT LEADER

For example, Switchcraft Fiber-Conn™ Fiber Optic Connectors have low attenuation — less than a 1.7 dB — with compact industry-accepted Tri-Part design. Switchcraft is committed to designing such vital components required for new high-technology equipment and systems.

## “TRADITIONAL” COMPONENT LEADER

Over 6,000 field-proven components developed especially for the electronic OEM market...single, multiple-station, lighted/unlighted pushbutton switches; long-life jacks and plugs; audio/general purpose connectors; cable assemblies; jack panels, jackfields, patching systems; audio accessories.

Whatever your component need, you owe it to yourself to check with the leader, Switchcraft, for the most efficient, cost effective products available. Profit from the company's four decades of helping customers design new, special components for their new, special equipment and systems.

## FOR SWITCHCRAFT® LITERATURE ON —

PRODUCT	REQUEST
Fiber-Con® Connectors	NPB370
Phone Jacks	J104
Phone Plugs	P202
Audio Connectors	A404/C502
Jackfields	J110
Multiswitch® Switches	NPB349/S325
Double Wipe Slide Switches	S330
Molded Cable Assemblies	M701

Prices/Specifications Subject To  
Change Without Notice

**SWITCHCRAFT INC.**

is represented in Canada, by —



**Atlas Electronics Limited**  
50 Wingold Avenue, Toronto,  
Ontario, Canada M6B 1P7, Telex  
No. 069-69538. Telephone  
416-789-7761.

Branches: ☐ Quebec 514-337-5260  
☐ Ottawa 613-744-1212 ☐ Alberta  
403-240-3838 ☐ British Columbia  
604-225-5011 ☐ Saskatchewan/  
Manitoba 204-889-0214

Circle No. 3 on Reader Service Card



## Servo Interface

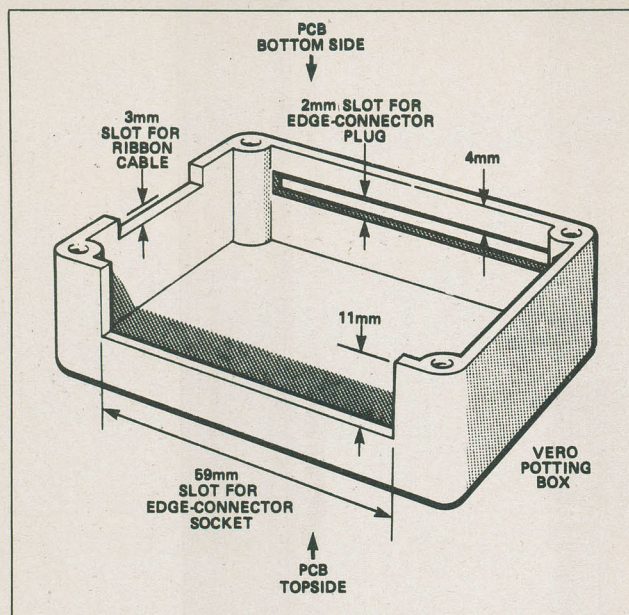


Fig. 3. Construction of the edge connector box.

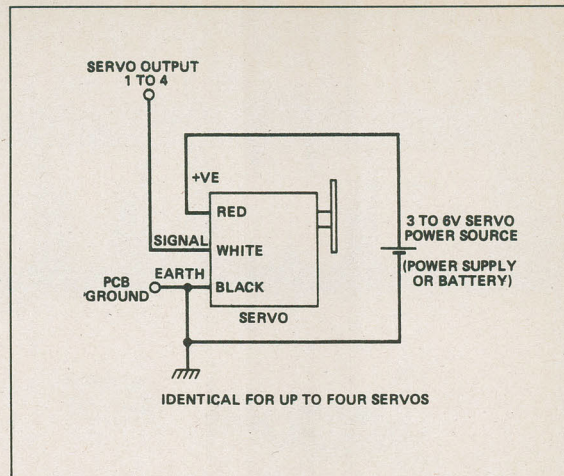


Fig. 4. Servo connections.

### HOW IT WORKS

#### Timing Generator

Each servo requires a pulse width variable from between 1 to 2mS and repeated every 20mS. The servo's position corresponds to the width of this pulse. Our system uses a seven bit binary number to represent this position which in turn controls the pulse generation. One position value is stored in an eight bit register for each servo channel. The data in these four registers is taken sequentially and used to generate a pulse of proportional width using a presettable down counter. The particular data for each channel is addressed by a two bit counter, which also routes the resultant pulse, via a demultiplexer, to the appropriate servo. An asymmetric clock, which triggers the two bit channel counter, also initiates the pulse generation. It has a full period of 5mS; thus all four servo channels are dealt with in 20mS to give the required frame rate. The timing diagram is shown in Fig. 8.

The detailed circuit diagram is shown in Fig. 7. The heart of this circuit is the eight bit binary down counter IC3, and its associated loading clock built around IC5b,c. Counter IC3 has eight preset inputs for determining the count start position. Input J0 is taken high for reasons of stability; we shall assume the other seven are set up to some binary value (this may be between 0 and 127). The clock input on pin 1 of IC3 is fed from a fast clock via an unusual form of AND gate (one half of decoder IC4 provides an AND function). The fast clock uses IC5a as a standard Schmitt trigger oscillator, its exact frequency being adjustable by PR1. The CARRY OUT signal on pin 14 of IC3 provides the servo pulse signals and is normally high during counting, but goes low when the count reaches zero. Since it's tied to one input of the AND gate, it disables the clock as zero is reached to prevent further counting. The CARRY

OUT Line is also sent to the decoder IC4 where the pulses are distributed to their corresponding servo channels.


CARRY OUT goes high again for another pulse when the ASYNC LOAD input on pin 9 is taken low. This also loads the binary value on the preset inputs into the counter, though counting will not commence until the LOAD input returns high. The LOAD pulses from the slow clock have an asymmetric duty cycle which remains low for a period of 1mS, thus determining the minimum servo pulse width. When the ASYNC LOAD returns high IC3 is released to count towards zero. CARRY OUT switches low after a time determined by the fast clock and the preset binary value, thus terminating the pulse.

The allowable variation in servo pulse width for a given clock frequency, say 250 kHz, will thus be determined by the binary value. At a value of zero, it will be the minimum 1mS dictated by the LOAD pulse. When the binary input is 127 (taking into account the J0 preset input, it's actually 255), the pulse width will be the maximum of 1mS + (255x4uS). The inset timing diagram of Fig. 8 illustrates the pulse generation. NAND gates IC5b and c (forming the slow clock), are configured as a standard CMOS astable with variable duty cycle. The overall frequency is set by C2 and the total value of the preset PR2; while D1 and D2 separate the charge and discharge paths through each arm of the preset to alter the duty cycle independently of frequency (1mS high and 4mS low). The minimum pulse size for binary zero can thus be altered from 1mS by adjusting the duty cycle with PR2. The maximum pulse at binary 127 depends on the fast clock frequency and may be adjusted with PR1.

The two-bit binary counter formed from IC6, addresses the servo whose par-

ticular pulse is being generated at any given moment. IC6 is a dual four-bit counter (the 4520). The first two bits of one counter, pins 3 and 4, are used as the A and B addresses for the pulse selection. Counting is clocked on the negative-going edge of the load pulse by using the clock enable input on pin 2 and tying the clock input to ground. These repeating address states perform two functions: they select one of four registers containing the servo position data word and, they also select one path of the demultiplexer IC4 to route the pulse to its associated servo. Thus four servo timing slots occur in the 20mS frame period.

IC1 and 2 are the servo position data registers (74LS170s). Each IC contains four 4-bit words of memory, and they are simply connected in parallel to give four 7-bit words. These registers are special in that

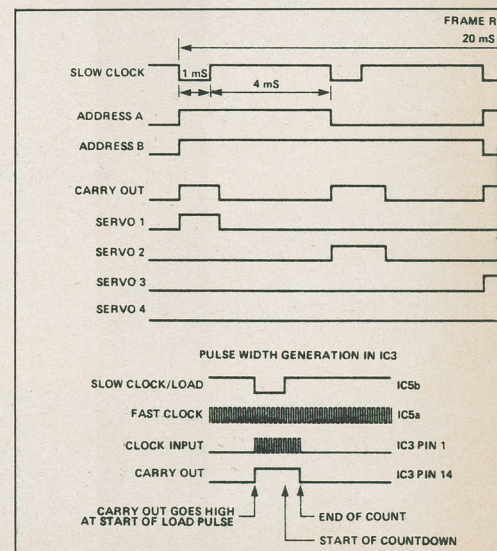



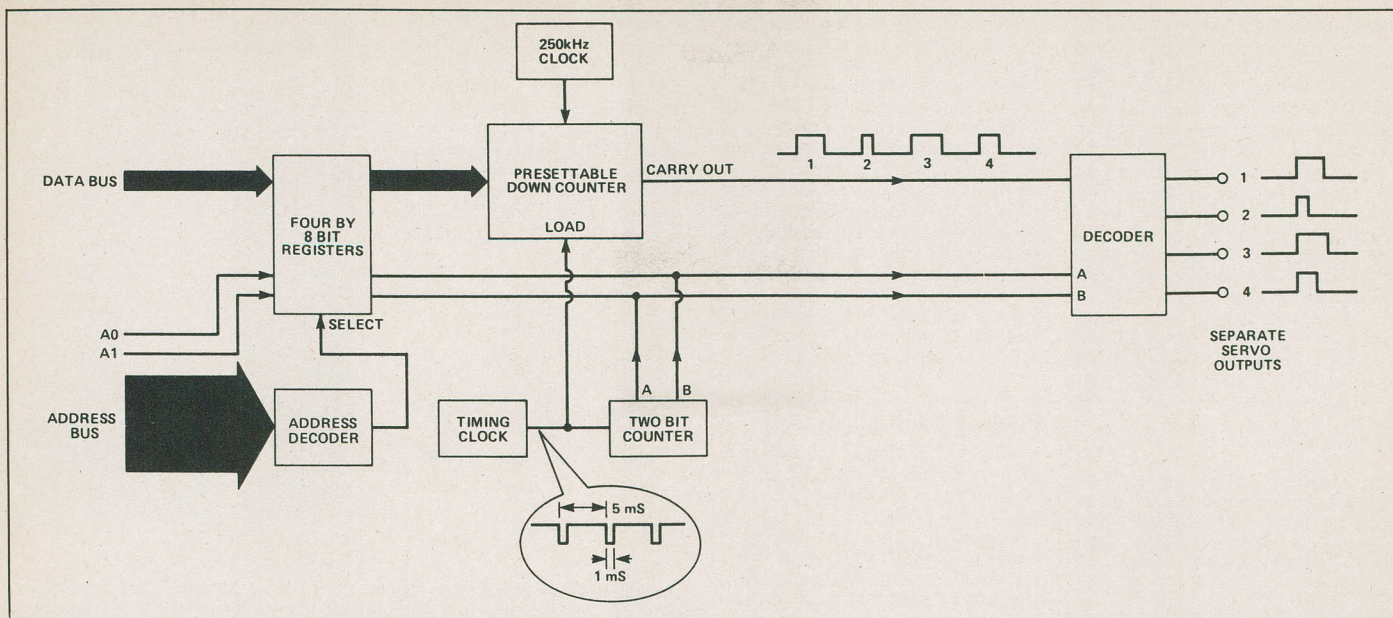


Fig. 5. Block diagram of the ETI Servo Interface.

they contain separate read and write address decoding for each word, allowing simultaneous reading and writing. The data inputs (on pins 15, 1, 2 and 3 and connected to the computer's data bus) are also separate from the data outputs (on pins 10, 9, 7, and 6) that are sent to the timing generator. Thus the timing generator can read the four registers in turn, by scanning through the read addresses on pins 4 and 5, while at the same time the computer can address any register via the write addresses on pins 13 and 14, and write new data into this location with a 'memory write' instruction. The write addresses are wired to the computer's least significant address bus bits, so the registers will simply appear as consecutive memory locations ('write only' memory). Direct memory mapping is thus achieved between the computer and the ser-

vo positioning.

The **READ ENABLE** input on pin 11 (active low) is grounded to allow permanent read access for the timing generator. The **WRITE ENABLE** input on pin 12 is driven from the address decoder output. Thus, the registers will only 'see' the computer's data bus when the interface is specifically addressed by the microprocessor for a memory write operation.

Capacitors C3, C4 and C5 are included across the supply lines providing the requisite TTL supply decoupling.

#### Address Decoder


The block diagram of Fig. 5 gives an overall view of the servo interface system. The address decoder block can be considered as essentially separate from the main timing generator; its circuit is shown separately in Fig. 6. The address decoder merely allows the computer to send information to the timing generator. It detects when the computer outputs an address that corresponds to its own address, and then enables the servo position registers, so allowing them to be written to from the data bus. Certain control lines from the microprocessor are also gated into the address decoding so that the registers will not be enabled unless the computer is specifically writing to memory.

The decoder is built from a cascaded arrangement of identical four-bit TTL comparators, IC7, 8 and 9. Each comparator compares a binary word on the A inputs to that set up on the B inputs. If the two words are the same, then the A = B output on pin 6 goes high, so long as the A = B input is also high. The A = B inputs are connected to the A = B outputs of the preceding stages, to give a total of 12 bits of comparison. The A inputs go directly to the most significant address bus bits and two control lines, while the B inputs are set by links or switches that

tie the TTL inputs to ground when closed. Pull-up resistors R12-23 ensure a logic high input when these switches are open. One, two or all three of the comparator stages may be used on the PCB depending on the application. Resistors R10 and R11 ensure that the A = B inputs are kept high if the preceding stages are not used. With the control line arrangement shown on the circuit diagram, (SW3c,d must be closed to suit Z80 control signals), we are left with 10 lines for the address bits. Ten bits will decode a 16 bit address space into 64-byte blocks as the memory map diagram in Fig. 4 illustrates. This will usually be quite adequate since the switches can set this block anywhere in memory.

To summarize, when the address bits and control lines all correspond to the logic levels set on the switches, then the A = B output goes high. This output is buffered and inverted by transistor Q1 to provide the **WRENABLE** output for the timing generator. For Sinclair users, it is also taken via D3 and a jumper link to the ROM chip select line (**ROMCS**). If this line is logic high, the Sinclair 8K ROM is switched off; when IC9's output is logic low, the diode allows the ROM to be selected by the ZX81 as necessary. The 8K ROM is not fully decoded on the ZX81, and 'echoes' of it appear across the 64K address space. It is often useful to place the interface at an address within one of these echoes and the jumper link achieves this by de-selecting the Sinclair ROM when the interface is addressed.

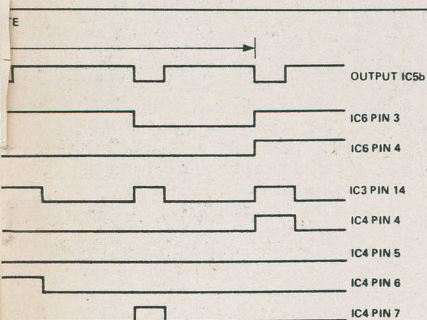Jumper link Jb selects the **MREQ** control line for memory-mapped I/O on the ZX81. Since all the address and control line inputs are equivalent, they could be arranged in an arbitrary order with any mix of address bits and control signals monitored for any logic pattern.



Timing diagram for the servo interface.

continued on page 68



## for your information

New manufacturing technologies for improved productivity and product quality will highlight TORONTO '84, the third SME Tool & Manufacturing Engineering Conference and Exposition. Slated for October 2-4 at the Toronto International Centre, the event is sponsored by the Society of Manufacturing Engineers (SME) and produced and managed by Hugh F. Macgregor and Associates, 360 Consumers Road, Willowdale, Ontario M2J 1P8.

Four workshops and three technical sessions focusing on new manufacturing techniques in dimensioning and tolerancing,

EDM, material handling analysis, jigs and fixtures, robot systems, and deburring make up the conference announced today by SME. Running concurrently with the conference, the exposition will feature demonstrations of advanced machine tools, automated production systems, and a wide range of metalworking equipment, tooling and accessories. More than 175 equipment builders and distributors are expected to participate, SME said. Show hours are noon to 9 p.m. Tuesday and Wednesday, October 2 and 3 and noon to 6 p.m. Thursday, October 4.

### LOOSE ENDS

The regulator IC for the Modem Auto-Answer Project in the June issue is incorrectly listed in the parts list as a 7405. It should read 7805. It should read 2 x 4N35.

Looking for transducers to measure velocity or linear and angular displacement? Trans-Tek transducers are available for a wide variety of purposes, and are represented in Canada by Alexander Smart Ltd., 351 Steelcase Rd., Markham, Ontario L3R 4H9, with branches in Montreal, Calgary, and Vancouver.

Circle No.51 on Reader Service Card

### Power Supply Protection


A new power supply supervisory circuit, has been introduced by Motorola. Known as the MC3425,A/3525,A, the device series provides all of the necessary functions required to monitor over-and-under voltage fault conditions. The MC3425,A/3525,A is a dedicated low-cost over-and-under voltage protection circuit packaged in an 8-pin mini-DIP. The new device series is significantly less expensive than earlier products, while providing many of the functional features of the more advanced circuits of this type. Features include programmable time delay and hysteresis. Voltage range is 4.5 to 40V.

In our June issue we published A Computer Output Driver circuit in the Circuit Supplement feature, but for some strange and mysterious reason, unknown to the likes of humans, the parts list was omitted. Our deepest apologies to those of you who lost countless hours of precious sleep, not to mention great quantities of hair. Here is the new and improved parts list:

IC1	74LS02
IC2	74LS00
IC3, IC4	74LS374
IC5	74LS86
Q1-16	2N5551
Q17-32	2N4923, 2N6123
	etc.
D1-16	1N4002, 1N4004
	etc.

Hewlett-Packard is offering a new 54-page book on preparing business graphics for the best presentations, "Steps to Effective Business Graphics". It includes information on choosing a computer graphics system. \$20.79 from HP; if you can't locate an HP dealer, contact them at 6877 Goreway Dr., Mississauga, Ontario L4V 1M8.

Circle No.50 on Reader Service Card

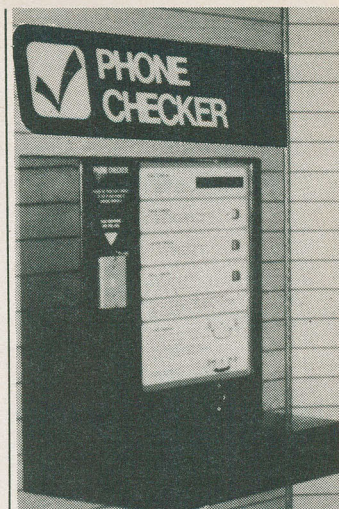

### Phone Checker by David Dempster

In the United States, they are making life a little easier for consumers — at least for those who are having problems with their telephones. They are doing it by making it possible for the consumer to test his or her own portable equipment.

All of AT&T retail Phone Center Stores are to be equipped with Western Electric's Phone Checker, part of the technological and market revolution that has been created by the huge communications company's divestiture program.

Consumers can now bring virtually any make of telephone into the nationwide system of Phone Center Stores and test them free of charge for dial, mouthpiece, receiver, bell and cord operations. The test equipment is either wall or desk mounted in the "Do-It-Yourself" equipment section of the retail outlets. Use of the Phone Checker by the public, will cut down on service call charges for consumers and the company.

The electronic test gear that performs five function checks is housed in a fibreglass-reinforced-polyester cabinet. Operation is simplicity itself. All that the consumer has to do is place the telephone to be tested on the cabinet's shelf and plug it into the Phone Checker's receptacle. A set of simple three-step instructions guides the consumer through each of the test sequences — Dial Check (rotary or pushbutton), Talk Check (mouthpiece), Listen Check (receiver) and Bell Check. Each of the tests can be completed in a matter of minutes.

The Phone Checker is a user-friendly piece of equipment encased in a reinforced plastic cabinet that protects it from the bumps and knocks of everyday use. Its design helps overcome any "mental blocks" that one may have about diagnosing one's own phone. Consumers taking the step of checking their own equipment can reduce the likelihood of being billed for service calls that might prove unnecessary, a cost that has been increasing every year.

# PROBES FOR SALE

## FROM THE BEST SOURCE FOR OSCILLOSCOPE PROBES AND MM/VOM TEST LEAD SETS.



- Low cost
- High Quality
- Excellent Performance
- Slender, Flexible Cable



- Wide Range of Choice
- Switchable X1 and X10 Attenuation Factor
- 100 MHz Bandwidth

MODEL SP100

# \$50<sup>10</sup>

**Your Probe  
Specialists**

Colina Canadian Sales & Stocking Source



**BCS**  
ELECTRONICS  
LIMITED

980 Alness St. Unit 7,  
Downsview, Ontario,  
M3J 2S2  
(416) 661-5585  
TELEX 065-28109



# SPECIAL SALE

**RX 6600**  
For  
**\$479.00**


- 64K Ram
- Z80 (CP/M)
- Special Function Keys
- User's Defined Keys
- Apple II + compatible


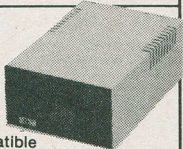
## DISK DRIVE

For **\$239.00**

- Apple II Compatible Shugart 390L
- Slim Line Teac \$249.00
- IBM Slim Line Double Side DD \$249.00




## CARDS & PERIPHERALS

- Z80 \$ 49.00
- 16K Ram \$ 55.00
- Disk Controller \$ 45.00
- 80 Column \$ 69.00
- Light Pen \$199.00
- Joy Stick \$ 38.00
- 5 Amps Power Supply \$ 79.00

## PRINTERS

- Mannesmantlyl Sprit 80 \$425.00
- TTX Daisy Wheel \$575.00

**IBM MAIN BOARD**  
For  
**\$479.00**

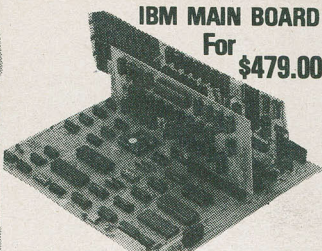

- IBM Compatible bare Board \$ 39.00
- Multi function card \$225.00
- IBM Compt. Case \$ 99.00
- IBM Compt. Power Supply 10 amps 100 watts \$119.00
- IBM Compt. Drive DSDD \$249.00

## IBM PC COMPATIBLE

### KEYBOARD

**\$179.00**



Enhance your IBM PC\* Compatible Computer System with K150 Keyboard.

Use Cherry TS-M0001 switch with life time 20 million operations.

- \*IBM is Trade Mark of International Business
- \*Apple is a registered Trade Mark of Machines Apple Canada Inc.

# ELECTRONIC CONTROL SYSTEMS

1890 Meyerside Drive, Mississauga, Ontario L5T 1B4  
(416)673-1302 Hours — Mon. to Fri. 10-7, Sat. 10-2

Circle No. 35 on Reader Service Card.

# WHY SPEND A FORTUNE ON A DIGITAL CAPACITANCE METER?

The MC100A comes completely assembled and calibrated and at \$89.95 is an outstanding value. The extensive range of 1 pF to 9,999 uF (no external meters required) and true hand held portable size (only 4 3/4" x 2 1/2" x 1 1/2") make the MC100A an extremely practical and easy to use instrument for the hobbyist technician or engineer.


## CHECK THESE OTHER FEATURES

- \*Basic accuracy 1% (± one count) on pF, nF ranges, 3% (± one count) on uF range.
- \*Uses single 9V battery (not included).
- \*Decimal points light up when battery is low or when capacitor is overrange.
- \*Full 4 digit high efficiency LED display uses special circuitry to save on batteries.
- \*Constructed with a tough impact resistant plastic case.
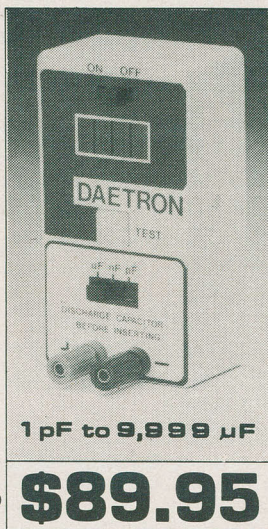
## ONE YEAR PARTS & LABOUR WARRANTY



**DAETRON**  
935 THE QUEENSWAY  
BOX 641  
TORONTO ONTARIO M8Z 5Y9  
(416) 255-9701  
DEALER ENQUIRIES INVITED



1 pF to 9,999 uF

**\$89.95**

## PLEASE SEND ME

(Quantity) MC100A(s) @ \$89.95 \$  
Ontario residents add 7% PST \$  
Postage — \$1.85 (per instrument) (C.O.D. orders add \$1.50) \$  
☐ I ENCLOSE CHEQUE ☐ MONEY ORDER ☐ BILL MY VISA TOTAL \$  
☐ VISA CARD NO. \_\_\_\_\_

EXPIRY DATE \_\_\_\_\_ SIGNATURE \_\_\_\_\_  
Immediate shipping on orders with money orders, VISA or certified cheque.  
Personal cheques please allow 2 to 3 weeks for clearance.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ PROV. \_\_\_\_\_ POSTAL CODE \_\_\_\_\_

MAIL TO DAETRON 935 THE QUEENSWAY BOX 641 TORONTO ONTARIO M8Z 5Y9

Circle No. 14 on Reader Service Card

# MAXI-SWITCH

## Keyboards

For IBM™ and Compatibles



Only available from the following dealers:

- Cornet
- Exceltronix
- J.L.S.
- Ogivar Inc.
- Personal Computers
- President
- Robinhood

## Don't be fooled by IMITATIONS

t.w. wilson sales  
2652 Slough St.,  
Mississauga, Ontario  
L4T 3T2  
(416) 677-8200

## Dealer Inquiries Invited

IBM is a registered trademark of International Business Machines


Circle No. 16 on Reader Service Card.

THE BRUNELLE  
**Commander**  
— SERIES —

- ✓BP SERIES
- ✓ENCAPSULATED
- ✓LINEAR

Dependability you can count on. Meets toughest demands!

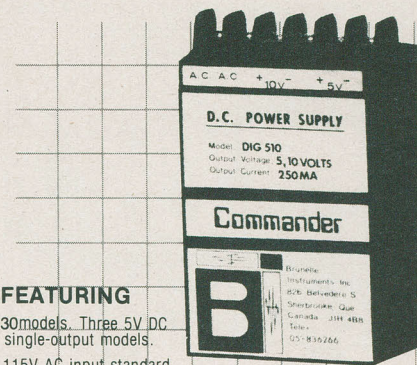SOMETHING  
**NEW**  
IN A  
**POWER**  
**SUPPLY**



## FEATURING

- 30 models. Three 5V DC single-output models.
- 115V AC input standard. Other voltages optional.
- Canadian made from quality components.
- 2 YEAR WARRANTY

- Overvoltage (and short circuit) protection
- standard on single-output models.
- Barrier terminal strip connections for easy installation or removal.



CANADA  
BRUNELLE INSTRUMENTS INC.  
826 Belvedere St  
Sherbrooke, Quebec J1H 4B8  
Tel.: 1-819-569-1408  
Télex: 05-836266


Available from:  
• Active Components Stores across Canada  
• Fathom Atlantic, Dartmouth, Nova Scotia

Circle No. 6 on Reader Service Card



# HAMEG® Oscilloscopes

*For Field Service  
and Laboratory*

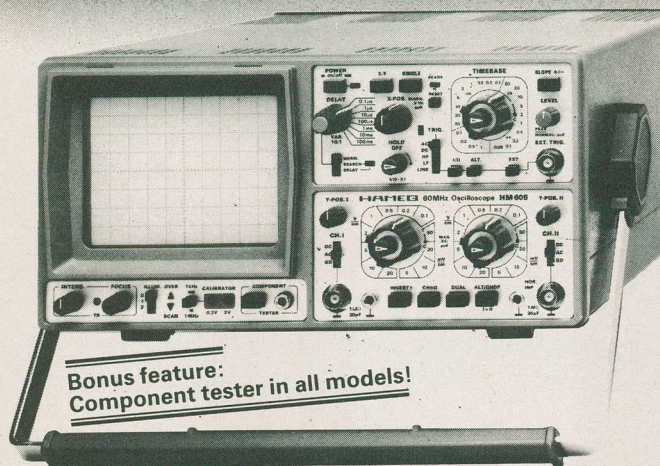

**Bonus feature:  
Component tester in all models!**

## HM 605 60 MHz Dual Trace - \$1550,-

Sensitivity 5mV-20V/div at 60 MHz, 1mV at 15 MHz • Automatic peak-value or normal triggering to 80 MHz • Delay line • Variable sweep delay from 100ns-1s • Timebase range from 2.5s/div to max. 5ns/div • Unique fast-rise-time 1kHz/1MHz calibrator • Bright high-resolution 14kV CRT.

## HM 204 20 MHz Dual Trace - \$1120,-

Sensitivity 2mV-20V/div • Timebase range 2s/div-20ns/div • Automatic peak-value triggering to 50 MHz • Variable sweep delay • Single sweep mode • Y-Output • Z-modulation • Over-scan indicator.

## HM 203 20 MHz Dual Trace - \$835,-


Western Europe's best selling 20MHz-Scope! • Sensitivity 2mV-20V/div • Triggerbandwidth 40 MHz • Timebase range 0.2s - max. 40ns/div

## HM 103 10 MHz Single Trace - \$550,-

Small, compact service scope • Sensitivity 2mV-20V/div • Timebase range 0.2µs-0.2s/div • TV-V and TV-H triggering.
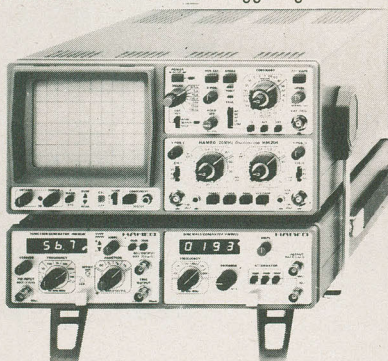
### »Modular System« HM 8000

An expanding  
range of  
signal generators,  
multimeters,  
counter/timers,  
etc. ...



**For more details  
write or call collect:**

**BCS**  
ELECTRONICS  
LIMITED

980 Alness St. Unit 7,  
Downsview, Ontario.  
M3J 2S2  
(416) 661-5585  
TELEX 065-28169

continued from page 64

## for your information

### New Hand-Held Terminal

Definable Data Devices, Inc., has released enhanced versions of its DATA-MAC 8 and DATA-MAC 16 HDST's (Hand-Held Data Storage Terminals). In addition, they are now offering the units to "systems-capable" retailers.

Now field personnel simply enter their information in Definable Data's new DATA-MAC, instead of writing it down. Once stored, it can be dumped directly into the computer without rehandling — even from a telephone booth.

The DATA-MAC is designed to be hand-held. It's small, lightweight, and calculator-shaped. The 40-key keyboard has numbers in a 10-key pad and letters in alphabetic order (a 'qwerty' keyboard is useless one-handed and baffling to non-typists). It's rugged and sealed to withstand harsh outdoor and industrial conditions.

Other features include: remarkably efficient 8K or 16K data memory with proprietary "Memory Sentry" which prevents data loss due to accidental or unauthorized clearance; proprietary "Power Sentry" which retains data for over 15 years without battery charging; all CMOS components; 8 bit single chip microcomputer; 32 character "smart" LCD display; 40 key alphanumeric keyboard; RS232C serial and Centronics parallel interfaces. DATA-MAC's are already in use in conjunction with nearly every kind of micro, mini, and main-frame computer, from Apple and IBM, to DEC and Burroughs. Retail prices begin at \$1295.00. For more information contact: Definable Data Devices, Inc., P.O. Box 769, Wilsonville, OR, U.S.A., 97070; or call (503)682-3131 for complete details.

Circle No.55 on Reader Service Card

NEC Electronics has announced the development of a CMOS gate array containing 11,000 gates; the previous industry record was 8,000 gates. It's a semi-custom chip; logic paths can be tailored to suit the application. The power consumption is 20mW, and the speed is 2 nS per gate.

The Heath Company announces a new air cleaner for home and office; it can be assembled from a kit without soldering. Two filters and an electrostatic precipitator remove particles as small as 0.01 microns (less than 1/2 millionth of an inch). It's at Heathkit Electronic Centres — 65 of them in the U.S. and Canada.

## CIRCUITRONICS

8088DC CPU	\$31.95
8237A-5 Prog. DMA Controller	\$24.50
8250B	\$19.50
8253A-5 Prog. INTRVL. Timer	\$11.95
8255A-5 P.I.A.	\$19.50
8259A Prog. Interrupt Cntrl.	\$ 9.95
8288 Bus Controller	\$18.75
8284 ADC Clock gen. and driver	\$11.85
765AC Disk Controller	\$26.50
SN75477	\$ 2.25
74LS322	\$11.50
14.3818MHZ Crystal	\$ 2.75
4.0000 MHZ Crystal	\$ 2.95
Edge card connectors 62 pin	\$ 2.95
17.43MHZ	\$ 3.25
74LS629	\$ 6.50

Remember we have all parts

### In Stock

Please send certified cheque or money order Only!. All orders will be shipped C.O.D. Post Canada or add \$3.50 for postage & handling. Ontario residents add 7% P.S.T.

**CIRCUITRONICS**

2305 Yonge St., Suite 290 Toronto, Ontario M4P 2C7



## CORONA PRICES SLASHED

Now the Corona is Even MORE Affordable  
Now is the Time to Buy the Computer Rated  
Most Compatible with the IBM PC

TWO DOUBLE SIDED DRIVES, 256K **\$3795.00**

Includes MS-DOS, Multimate, Basic & PC Tutor

Prices of other configurations also reduced. Ask us about the new 1 year warranty

### NEW KAY PRO COMPUTERS WITH \$3000 FREE SOFTWARE!

New KAYPRO 2 ..... **\$1995<sup>00</sup>**  
New KAYPRO 4 ..... **\$2795<sup>00</sup>**  
New KAYPRO 4 + 88(w/MS-DOS) ... **\$3395<sup>00</sup>**  
New KAYPRO 10 ..... **\$3995<sup>00</sup>**

**APPLE II+ COMPATIBLE** More features than the Apple II +  
Complete Computer System with disk, High-res Monitor  
from **\$890<sup>00</sup>**

### F-10-40 40 CPS DAISY WHEEL PRINTER

Serial **\$1695<sup>00</sup>** Serial + Parallel **\$1795<sup>00</sup>**  
1 Year Warranty

**SATISFACTION GUARANTEED** All orders shipped within 48 hours  
upon receipt of payment.

# AAAA

21 Amber, unit 4  
Markham, Ont.  
L3R 3K5  
(416) 477-4033

COMPUTER SYSTEMS

Circle No. 32 on Reader Service Card.

## Quality • Reliability • Versatility All in One

### Introducing The New Infinity Computer

#### FEATURING

- Compact Design
- 12" Amber 20MHz Swivel Base Monitor
- 1/2 Height Silent Direct Drive (XI)
- Dual Disk Controller
- 188 Built-in Function Keyboard
- 10 User Define Keys (keep program upto 5 years)
- Numeric Keypad
- Auto Line Feed
- Auto Repeat
- Upper Lower Case Cap Lock
- Heavy Duty Power Supply
- Runs Apple™ II plus Program



**\$999.00**

#### Extended Warranty Plan available

Apple is a Registered Trademark of Apple Computer Inc.


1/2 Height Silent Direct Disk Drive

Introductory Offer: **\$245.00**

Infinity Diskette

**\$19.95**

Dealers Inquiries Invited

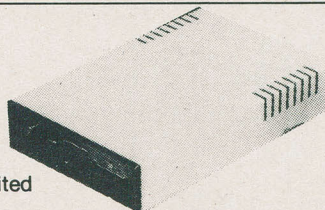

TERMS: Send cheque or money order (allow 2 weeks for personal cheque). Credit Cards welcome.  
No COD. Quebec residents add 9% sales tax. Add 5% for shipping and handling. Minimum order  
\$10.00, 20% restocking fee for returned merchandise. Prices and availability subject to change  
without notice. Do not send Cash.

## INFINITE CANADA INC.

785 Plymouth Ave.,  
Suite 123, TMR. Que. H4P 1B3  
Tel: 514-342-6454

Circle No. 12 on Reader Service Card

## E|MP MODEMS



Available  
in  
September

- Bell 103/212A compatible
- interface: EIA RS232C
- 0 to 300/1,200 bps Full Automatic
- Full duplex, Auto dialer, Auto-answer
- compatible, IBM and most personal computers.

### Modem MM101 only \$89.95

- 300 Baud - Full Duplex • Bell 103 compatible • Direct connection between microcomputer and telephone.

We also feature EMP Telephone products (Hand-held models — Emergency models — Cordless models) Sales Agents for ELEC PCB Boards, Multi layer — double and single sided.

DISTRIBUTORS AND DEALERS

INQUIRIES WELCOME

### MARK GEE ENTERPRISES LTD.

P.O. Box 249, Station "G", Toronto, Ont. M4M 3G7

Tel: (416) 862-8887

Telex 06-218808

#### Mail Orders:

Send certified cheque or money order, plus \$5.00 for shipping and handling. Ont. residents add 7% P.S.T. to

#### MCS MICROTRONICS INC.

483 Queen St. West,  
Toronto, Ont. M5V 2A9

Circle No. 1 on Reader Service Card

## 8088 Based Single Board Computer

#### Features:

- 5 Mhz 8088 processor
- up to 256K Bytes of 4164 type RAM
- 24 bits parallel IO (8255A-5) on 34pin header
- EPROM Socket for 2716, 2764 or 27128
- 160 mm x 234 mm (dual Eurocard size)
- Requires just 500 Ma. at 5 VDC ± 5%
- Provisions for expansion
- Schematics and application data (coprocessor, print spooler, Ramdisk, etc.)

PCB only (with documentation)

..... \$ 35.00

Complete kit for 128K system

..... \$250.00

Assembled and tested 128K system

..... \$342.00

Extra 64K bytes RAM

(8 x 150 ns. 4164's) ..... \$ 70.00

### H.T. Watt & Associates Ltd.

1245 California Avenue,  
Brockville Ontario K6V 5Y6

**Phone (613) 345-1199**

Mail orders accepted: 10 day money-back guarantee. Send certified cheque or money order. Ontario residents please add 7% P.S.T. Add \$10.00 for shipping and handling.

Circle No. 17 on Reader Service Card





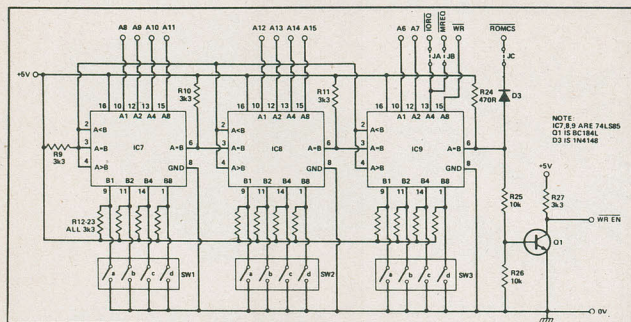
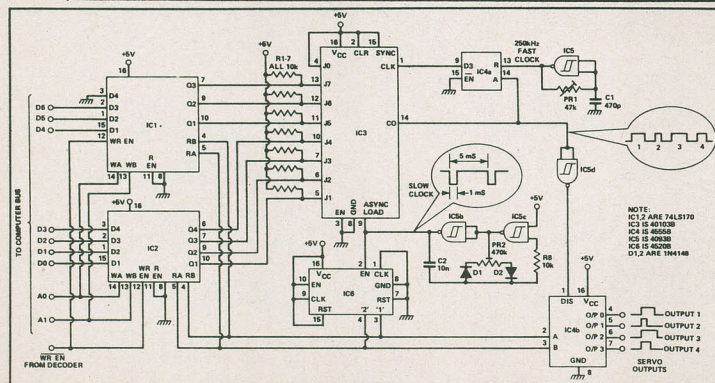


Fig. 6. Circuit diagram of the address decoder block.

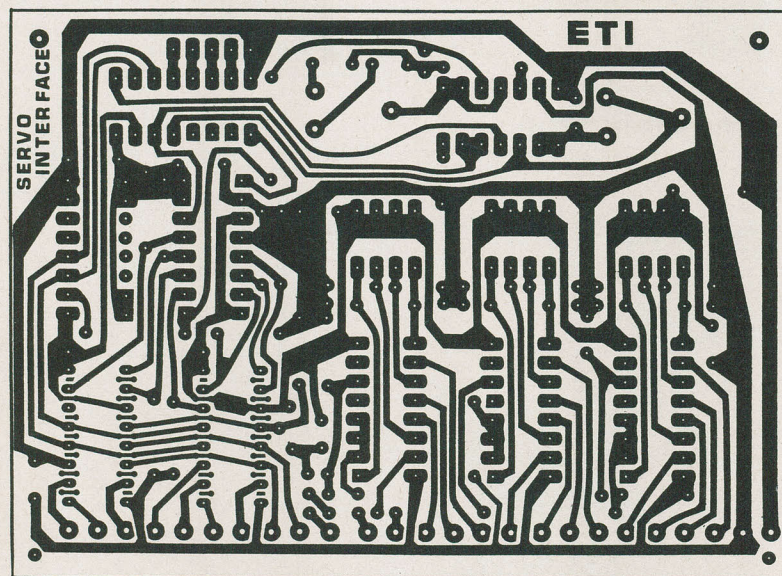

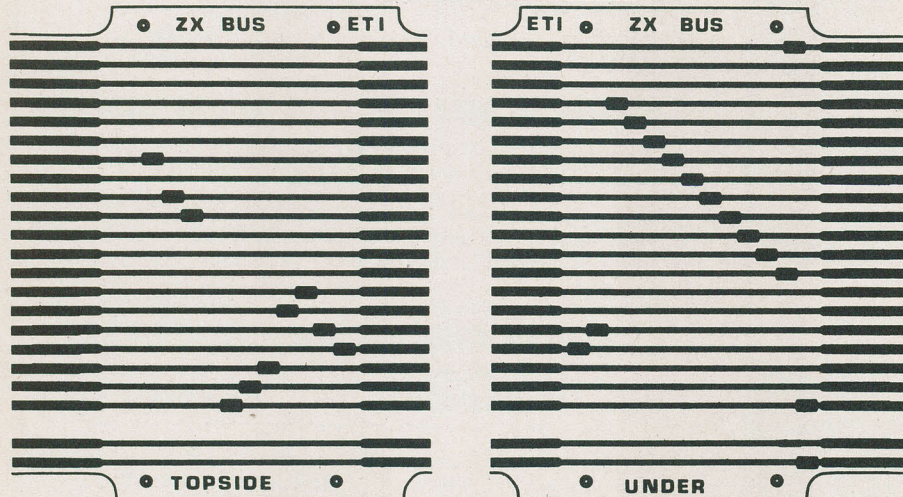

# The Digital vs. Analog battle is over.

**\$125\*** buys you the new champion. **The new Fluke 70 Series.**

They combine digital and analog displays for an unbeatable two-punch combination.

Now, digital users get the extra resolution of a 3200-count LCD display.

While analog users get an analog bar graph for quick visual checks of continuity, peaking, nulling and trends.

Plus unparalleled operating ease, instant autoranging, 2,000+ hour battery life and a 3-year warranty.

All in one meter.

Choose from three new models. The Fluke 73, the ultimate in simplicity. The feature-packed Fluke 75. Or the deluxe Fluke 77, with its own multipurpose protective holster and unique "Touch Hold" function (patent pending) that captures and holds readings, then beeps to alert you.

Each is Fluke-tough to take a beating. American-made, to boot. And priced to be, quite simply, a knockout.

So call for more information.

FROM THE WORLD LEADER  
IN DIGITAL MULTIMETERS.



## Fluke 73

\$125\*  
Analog/digital display  
Volts, ohms, 10A, diode test  
Autorange  
0.7% basic dc accuracy  
2000+ hour battery life  
3-year warranty

## Fluke 75

\$145\*  
Analog/digital display  
Volts, ohms, 10A, mA, diode test  
Audible continuity  
Autorange/range hold  
0.5% basic dc accuracy  
2000+ hour battery life  
3-year warranty

## Fluke 77

\$185\*  
Analog/digital display  
Volts, ohms, 10A, mA, diode test  
Audible continuity  
"Touch Hold" function  
Autorange/range hold  
0.3% basic dc accuracy  
2000+ hour battery life  
3-year warranty  
Multipurpose holster

\*Suggested Canadian price including duty and federal sales tax. Provincial taxes extra.



**"IN STOCK ACROSS CANADA"**

The Fluke 70 Series in Stock right now at the leading distributors listed at left.



# Allan Crawford Associates Ltd.

Test & Measurement Division

Toronto: (416) 678-1500 Montreal: (514) 731-8564 Ottawa: (613) 722-7682  
Halifax: (902) 463-8640 Vancouver: (604) 294-1326 Calgary: (403) 230-1341

Circle No. 11 on Reader Service Card



# Product Mart *Where Buyers Find Sellers*

**INSTRUMENTS** inventory clean up the following are new (n) or reconditioned (r) instruments. 1. Qty 2 triplett 4000 bench multimeter (r) \$169.00. 2. Yaesu YC500E frequency counter (r) \$160.00. 3. Amprobe AMC2 insulation tester (r) \$160.00. 4. Associated research 2204 insulation tester \$299.00 (r). 5. Simpson 378 ACMA meter \$29.00 (r). 6. Eico 150 signal tracer \$149.00 (r). 7. Robinair 14660 volt-wattmeter \$129.00 (n). 8. Tektonix 310A 10 MHz single trace oscilloscope \$125.00 (r). 9. G.E. H-10 halogen leak detector \$99.00 (r). 10 Qty 4 triplett 3525 digi-probe \$83.00 (n). Add 10% P and H, Quebec Res. add 9% P.S.T. Send cheque/ money order to **BRUNELLE INSTRUMENTS**, 826 Belvedere St., Sherbrooke, Que. J1H 4B8 (819) 569-1408.

**NEW Software** ... A 100 question quiz to tune-up your Z80 assembly language know-how. Use it as a fast review, a serious study, or as a game. Makes learning easy. Self-prompting. Choice answer questions. Keeps track of your score. On 8" SSSD floppy disk. Runs on 64K CP/M computers. \$64.25 Money-orders only. Man. res. add 6% tax. **Z-QUIZ**, P.O. Box 3775, Stn. B., Winnipeg, Man. R2W 3R6.

**AUTODIAL-CARD** for Apple II+//IIe. Features pulse dialing and software supplied on modem. \$49.95 VISA/MASTER-CARD. **W.H.S. ENTERPRISES**, 34 Epsom Cres., Winnipeg, Manitoba, R3R 0X2.

**MUSIC SYNTHESIZER** & accessories for your Apple - digital oscillator, interface card; hardware & software compatible with Soundchaser & alphaSyntauri systems. 61N keyboards from \$325. Write for list. Dealer inquiries invited. **CLASS ORGAN CO.**, 300-12 Don Park Road, Markham, Ont. L3R 3A1 (416) 475-1263.

**PORTABLE AM and FM BOOSTER ANTENNAS.** Compact audio mixers. Surplus tubes, speakers and other radio parts. List/Data from **ELDON ELECTRONIC ENTERPRISES**, Suite 200, 811 - 12th Avenue Southwest, Calgary, Alberta T2R 0J1.

**SATELLITE T.V. PROJECT**, July 83 ETI Hard to get parts, GAAS, Fets, Chip capacitors, LNA kits, etc. Also commercial LNA's receivers, polarizers. Trackers, dishes etc. At factory prices. Send S.A.S.E. for price list. **COLESAT SYSTEMS**, RR#2 Tantallon, N.S. B0J 3J0.

**Z80 MICRO-CONTROLLER** ... parallel I/O ports. Runs XYZ motors with encoders via keypad commands. An introduction to automation. Schematics, X-Y grid wiring lists, and software monitor in ROM, \$110.00 Source and doc on 8" SSSD disk for further software customizing via your 64K CPM computer, \$84.00. Do-it-yourself. Money-orders only. Man. res. add 6% tax, **Z80-CONTROLLER**, P.O. Box 3775, Stn. B., Winnipeg, Man., R2W 3R6.

**C64 assembler** \$9.95, disk version \$15.95. Low cost R5232 interface coming soon. VIC 20 8k Battery Powered RAM Cartridge clearance \$49.95 RAM/ROM board \$6.95. Free information. **CANADIAN MICRO PERIPHERALS**, Box 123, Waterloo, Ont. N2J 3Z9.

**AMAZING Space Age Devices** for the homebuilder. Lasers, Hand Phasers, Micro Transmitters, Psychonic, 3-D, Security and much more. Catalogue \$1.00. Mail Order Only. **DUKER ENTERPRISES** 8307 - 160 Street, Edmonton, Alberta T5R 2H2.

**DATA CONVERTER** for APPLE II//IIe//III<sup>TM</sup>, COMMODORE 64<sup>TM</sup>. Use with robots, sensors, science classes. Measure biopotentials, sound waveforms, shutter speeds. \$199. **NALAN**, Dept. ETI, Box 1426, Boone, NC 28607.

**NEW Amazing T.V. Projector Kit.** Engineer Designed. Get comparable reception to commercial projector costing \$2500.00 or more. Only \$24.50 (for portable television only). **QUEEN ENTERPRISES**, P.O. Box 159, Toronto, Ontario M6M 4Z2.

**FREE COMPUTER SOFTWARE CATALOGUE.** Save \$\$\$\$ by Direct Mail on Flight Simulation, Games, Trivia, Educational and Home/Business Software for your Apple, Atari, Commodore-64, VIC-20, IBM. **THE SOFT WAREHOUSE**, Dept. 14, P.O. Box 1983, Winnipeg, Man. R3C 3R3.

**DIGITAL Logic kits.** Each one builds on previous. Introductory package includes wire-wrap tool, wiring board, IC's, hardware, manual and more. Send \$37.95 + \$3.00 P&H for package or \$1.00 for more info. **LAMANTIA PRODUCTS**, P.O. Box 690, Lindsay, Ont. K9V 4W9

**1984 WORLD RADIO-TV HANDBOOKS** \$23 + \$2 S&H, WSI 1984 Catalogue \$2.00, **WSI RADIO**, Box 400, Kitchener, Ontario N2G 3Y9.

**WE DON'T SELL WORDSTAR!** — Just the most reasonably priced utilities, programming tools and applications in Canada. Write for FREE summer catalogue. **THE ALLIANCE**, 16 Alpha Ave., Toronto, Ontario M4X 1J3.

**SOFTWARE** at discount prices. Brand name software for Apple, Commodore, IBM, TRS-80, Wang, Atari, etc. Send for FREE catalogue. **LB ENTERPRISES**, Box 184, Newmarket, Ont. L3Y 4X1.

**AUDIO Kits:** graphic equalizers, 12-24 bands/channel \$89-200 (U.S.); noise filters, many others — **SSS 856T** Lynnrose, Santa Rosa, CA 95404, U.S.A.

## DID YOU KNOW?

That **HOBBILT ELECTRONICS** is the only truly Canadian company devoted to serving hobbyists and student?

Did you know that **HOBBILT** gives student discounts all year round whether in store or by mail?

Did you know that **HOBBILT** doesn't offer wholesale prices?

We're just better priced!

Did you know that \$1.00 and your name and address gets you the new 1984 catalogue? Well, now you know!

**HOBBILT ELECTRONICS**, 7454 Langelier, St. Leonard (Mtl), Quebec H1S 3B7

## DOSDIAL

### The Apple Terminal Package

There are plenty of terminal programs for the Apple II and its emulators. Some dial, some download, some even nurse your poor motherless wombats when they're lonely and scared at two in the morning. However, only **DOSDIAL** is this splendidly cheap.

**DOSDIAL** is a hybrid Applesoft and machine code package for fast operation and easy modification. It features a phone number library and automatic dialing. It operates on any fruit with a PDA 232C serial card and an autodial modem. A complete source file of the assembler code is included to allow it to be quickly patched for other serial cards.

Only  
**\$16.95**

Ontario residents add seven percent  
Computing Now! Software  
25 Overlea Boulevard, Suite 601  
Toronto, Ontario  
M4H 1B1

Advertising in the **Product Mart** section allows you to reach over 30,000 Canadian readers nation wide for \$1.00 per word (minimum 25 words). Please contact us for further details on the various sizes and styles available. Moorshead Publications, Suite 601, 25 Overlea Blvd., Toronto, Ontario M4H 1B1, (416) 423-3262



# EXCELTRONIX (416) 921-8941 1-800-268-3798

**Bulletin Bd. (416) 624-5574 Telex 065-24218**

**319 College St., (416) 293-1796 Toronto, Ont. M5T 1S2**

Catalogue shipping rates are incorrect. Please call us for correct charges. Prices in catalogue are fluctuating. Use as guideline.

## TWO NEW EXCELTRONIX LOCATIONS!

**NOW OPEN**

Ottawa  
217 Bank Street  
(613) 230-9000

Hamilton  
72 James St. North

Store hours 9:30 to 6:00 Monday-Saturday: to 9:00 p.m. Friday.

### PRINTERS

Star Gemini 10X	\$359
Gemini 15X	\$599
Delta 10 (160 cps)	\$739
Epson MX100	\$995
Epson RX80 (Replaces MX80)	\$495
Epson FX80 (New)	\$798
Epson FX100 (New)	\$1069
TTX (Daisy Wheel)	\$649
Microtek	\$139

### APPLE CARDS

16K card - Multiflex	\$58.00
128K card	\$210.00
Proto Board	\$15.00
80-Column Card	\$84.00
Z80 Card	\$59.00
EPROM Programmer	from \$69.00
(for 2716, 2732, 2732A, 2764, with software) Parallel Printer Card with cable	\$69.00
Wizard Parallel Card	\$95.00
Serial Card	\$99.00

### MONITORS

Zenith ZVM-122 Amber	\$139
Amdek Green	\$129
Zenith ZVM-123 Green	\$129
Amdek Colour 1	\$445
Roll and DG	\$419

New Macintosh with printer	\$4,295
Apple 2C with monitor	\$1,885
New Macintosh, based on 68000 with 3" Disk Drive (smaller version of Lisa™). Diskette Software now available	\$3,195

### Memory Chips

4164-150ns (1x64K single + 5V)	
Motorola	\$9.95
T.I.	\$7.95
4116-200ns (1x16K)	\$1.74
4116-150ns (1x16K)	\$1.99
2114L-200 ns (1Kx4 static)	\$2.49
6116-150 ns (2Kx8 static RAM)	\$8.94
(Pin compatible with 2716 uses negligible amount of power)	
2016-150 ns (2Kx8 static)	\$8.74
2102L-200 ns (1Kx1 static)	\$1.94
5101-CMOS RAM	\$3.84
2708-(1Kx8 EPROM)	\$6.74
2716-(2Kx8 EPROM single + 5V)	\$5.50
2732-(4Kx8 EPROM single + 5V)	\$8.95
2532-(4Kx8 EPROM single 5V)	\$8.74
2764-(8Kx8 EPROM single 5V)	\$12.95

**HUGE STOCK OF LS**

### Diskettes

5 1/4" Diskettes. Boxes of 10	
Maxell MD1	\$34.00
Maxell MD2	\$52.95
Verbatim	\$34.00
CDC	\$26.95
3M	\$32.95
Accutrak	\$26.95
2 Ectype Diskettes in a plastic binder sheet	\$5.89
Flip N File 50	\$44.95
Diskminder (75)	\$33.95
Dysan	\$39.00
BASF	\$34.00
BASF with case	\$35.00

**Special!**

## Featuring the Multiflex Apple™ Compatible Drive only \$249



Package Deals:	
A1 Drive & Controller	\$310
B2 Drives & Controller	\$549
Controller only	\$69
with software	\$119
VISTA DRIVE	\$299
QUENTIN DRIVE	\$299

**1 year warranty**

**Controller \$89**  
**With Apple™ Software \$119**

UNIVERSITY OF TORONTO/MULTIFLEX 6809 Board, great for learning about 6809 and computing in general with A & T \$499.00  
Economy Terminal ..... A&T \$369.00  
Package Deal ..... A&T \$849.00

### PRICE POLICY

Remember that at Exceltronix all prices are negotiable for quantity purchases. If you cannot afford large quantities on your own how about starting a Co-op.

**CHARGE**

### MAIL ORDERS

Send a certified cheque or money order (do not send cash). Minimum order is \$10 plus \$3 minimum for shipping. Ontario residents must add 7% provincial sales tax. Visa, Mastercard and American Express accepted: send card No., signature, expiry date and name of bank.



**NEW**  
Smith-Corona Printer  
L1000  
Bi-directional daisy-wheel  
Serial/Parallel port  
\$599


### Joysticks

Economodel	\$19.95	TG Joystick	
Wico Red Ball	\$42.95	Deluxe Model	\$75.00
Self-Centering with two adjustable controls.		TG Paddles Deluxe Model	\$64.95
Super offer	\$64.00	Hayes Mach III	\$58.95
Kraft Joystick		Model Deluxe	
(Apple, PC)	\$64.95	Table Top	\$59.00
Kraft Paddles	\$48.95	Hayes Mach II	\$48.95

Siemens 8" disk drives	
S.S.D.D.	\$79.00
Buy 2 for	\$59.00 each
D.S.D.D.	\$89.00 single
Buy 2 for	\$69.00 each
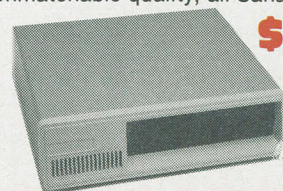
### Super Computer Case


Ideal for 8088 or 6502 boards  
Unmatchable quality, all-Canadian made



**\$87.00!**

**IBM Compatible Keyboard \$189.00**

**Maxiswitch or cherry**

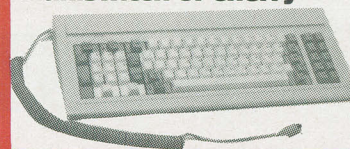

### Superb Power Supply

Uncased Dual 12V:  
(one at 2.8A, one at 2A).  
—12V at 0.5A, +5V at 5A plus

**\$69.00!**

Cased model, with fan, cord and switch

**\$139.00!**

These supplies are ideal for IBM compatibles, they fit beautifully into IBM compatible cases.


IBM is registered trade mark of IBM Canada Limited.

Check our catalogue for far, far more than you see here. If you didn't get it in your May copy of ETI or CN1, send for your free copy.

Head Office: 319 COLLEGE STREET, TORONTO, ONTARIO, CANADA. M5T 1S2 (416) 921-8941

Circle No. 27 on Reader Service Card.



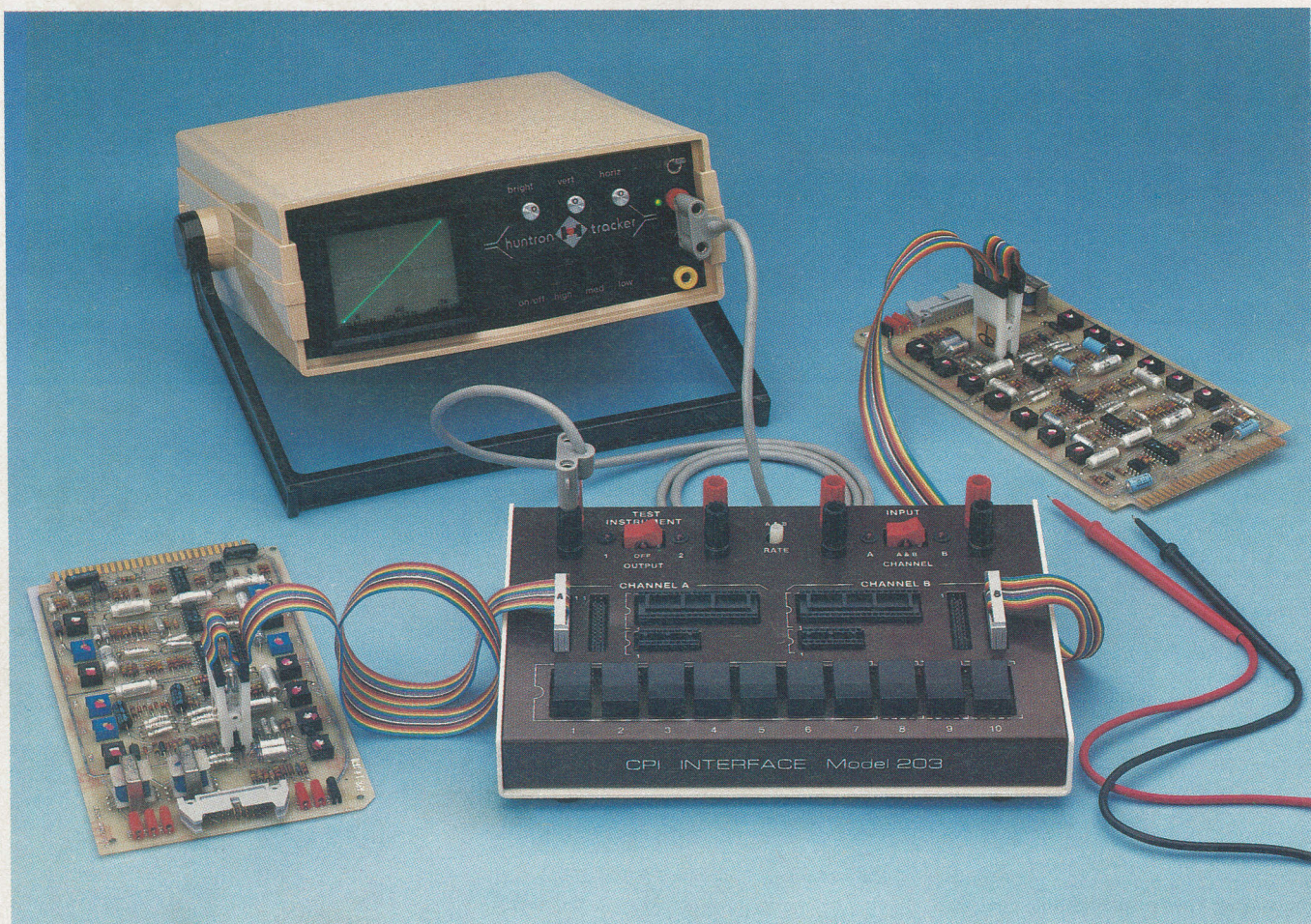

# FAST AND EASY

For a number of years the Huntron Tracker has proven to be an effective service instrument with the ability to troubleshoot electronic circuits to the component level without circuit power applied. The patented Microprobes with their insulated, needle-sharp stainless steel tips have been ideal for point to point testing.

Now the task of troubleshooting PC boards and DIP ICs has been greatly simplified. We have developed the CPI Interface, a test instrument accessory to make it faster and easier to troubleshoot DIP ICs and PC boards, IC by IC, instead of one pin at a time.

The two input channels of the Interface provide good-bad comparison testing capability while two independent, switch selectable output channels allow a choice of test instruments.

## Comparison Testing

In-circuit ICs may be tested using ribbon cables and IC clips to connect directly to the ICs on circuit boards. Out-of-circuit ICs may be tested using sockets mounted on the Interface. In either case, test signals from the device under test and a known good device are routed through the Interface to the desired test instrument.

Comparisons and measurements are made by connecting one IC clip to a known good IC and the other clip to the suspect device. Pins to be examined are selected one at a time by activating the appropriate pin-select switch. The Interface will then automatically alternate between input channels connecting first one IC and then the other into the test circuit. This short interval switching between input channels instantly reveals even minor differences between the devices being compared. The length of time each channel is activated is operator adjustable. The operator also has the option of locking on either channel in order to examine a pin more closely.

## For Power-Off Troubleshooting

With the Huntron Tracker connected to one output channel, testing or comparison of components and PC boards may be done in an unpowered state. An ohmmeter could be

connected to the other output channel in order to make resistance comparisons.

## For Power-On Troubleshooting

The Interface can also be used with general purpose test equipment such as multimeters or logic probes. This feature is useful when the user wishes to take measurements or make comparisons of voltages, signal levels or logic states in powered circuits.

## Additional Features

The Interface also incorporates jacks for connecting Microprobes so that point to point testing may be done at any time without disconnecting the Interface from either test instrument. This permits the user to leave the Interface connected to test instruments on the service bench at all times and go from "power down" Tracker, or ohmmeter testing to "power up" measurements at the flick of a switch.



Exclusively by:  
**CYPRUS PRODUCTS INC.**

7648 Heather Street Vancouver, B.C. V6P 3R1  
Telephone: (604) 327-8814